

# **ECE 327/627**

# **Digital Hardware Systems**

## **Lecture 7: Pipelining**

Andrew Boutros

[andrew.boutros@uwaterloo.ca](mailto:andrew.boutros@uwaterloo.ca)

# Some Logistics

- Lab 2 was released last Friday
  - Worth **8%** of the ECE 327 course grade
  - Worth **4%** of the ECE 627 course grade
  - Deadline on **Friday, Feb 6 @ 11:59 pm**

## In the Previous Lecture ...

- More FSM design examples:
  - FSM with multiple possible transitions per state – Chess Clock
  - Multiple interacting FSMs – Music Toy
  - FSM + Datapath (FSMD) – Polynomial on a multiply/add ALU


# What is Pipelining?

# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ...

 
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



 
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!


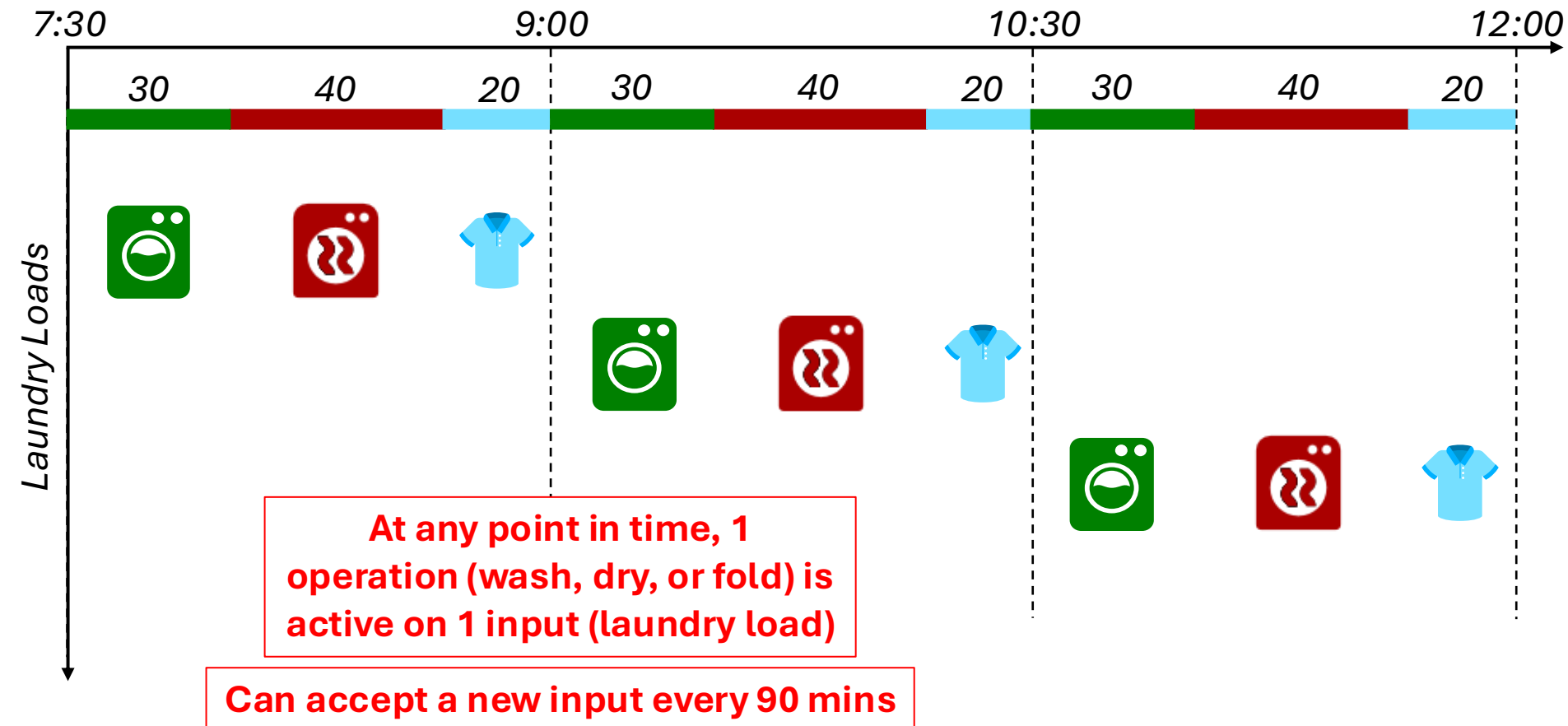
# What is Pipelining?


Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!





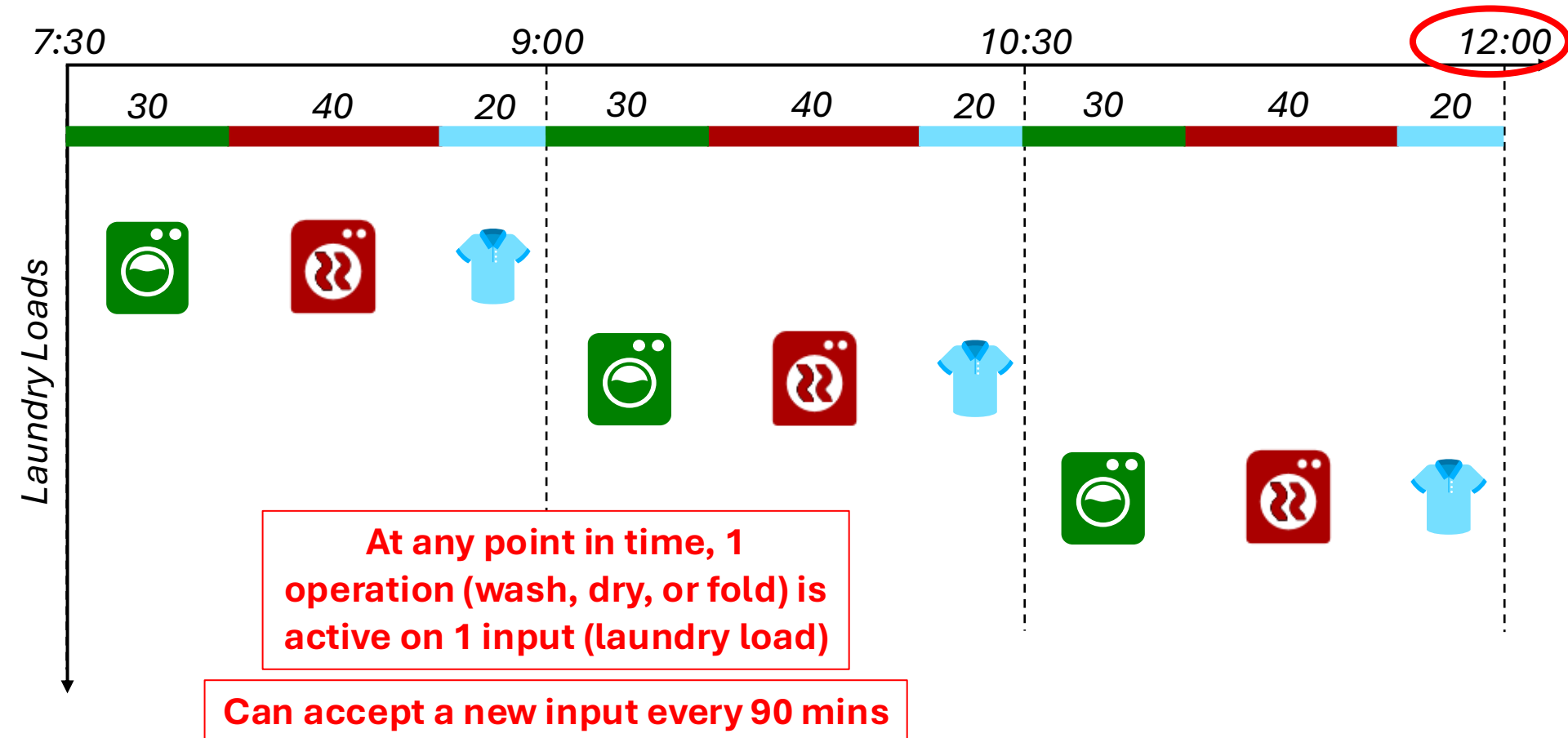
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



 
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



 
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



 
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



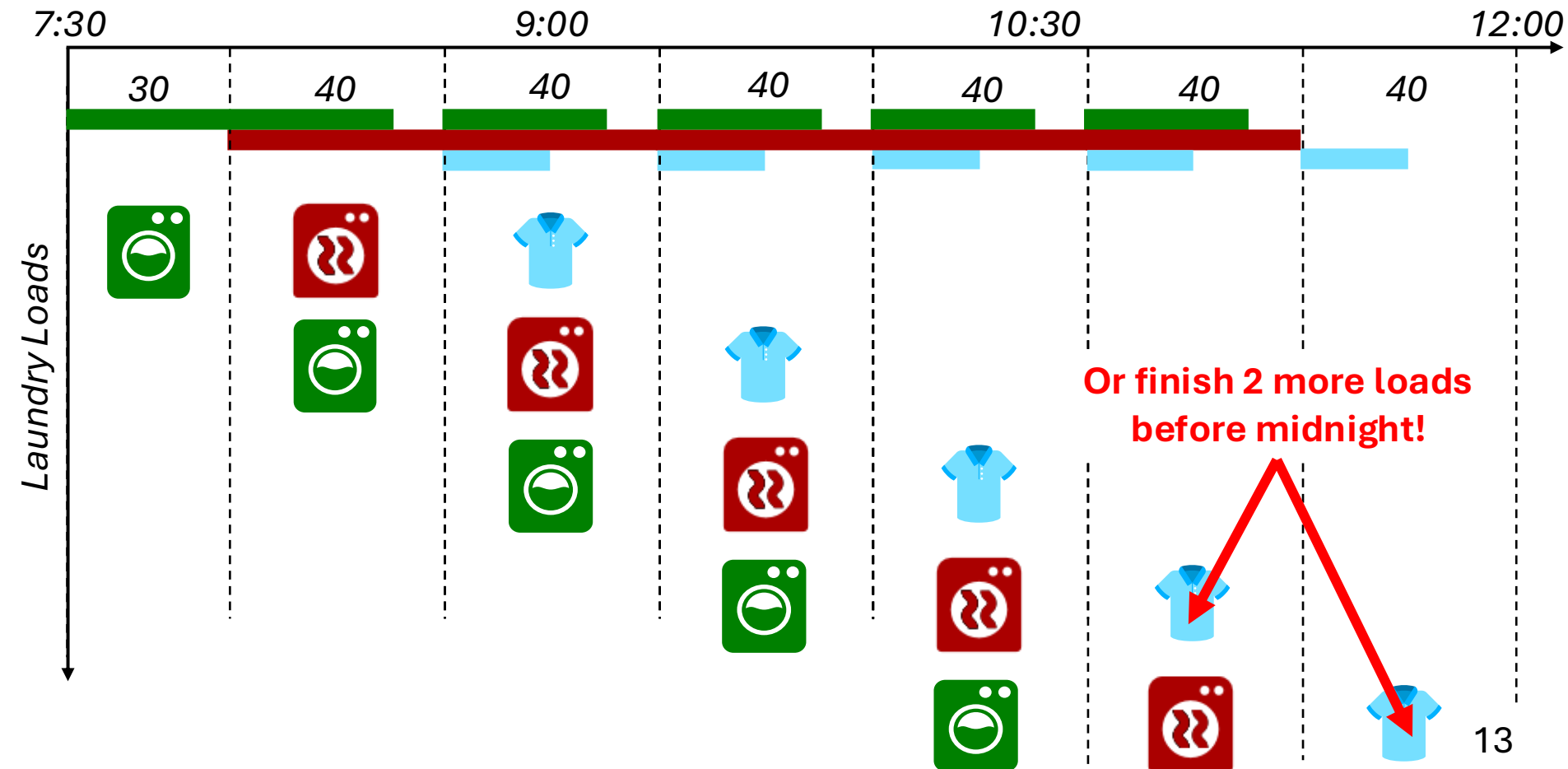
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



 
# What is Pipelining?

Nice analogy to understand pipelining is everyone's favorite activity ... doing laundry!!



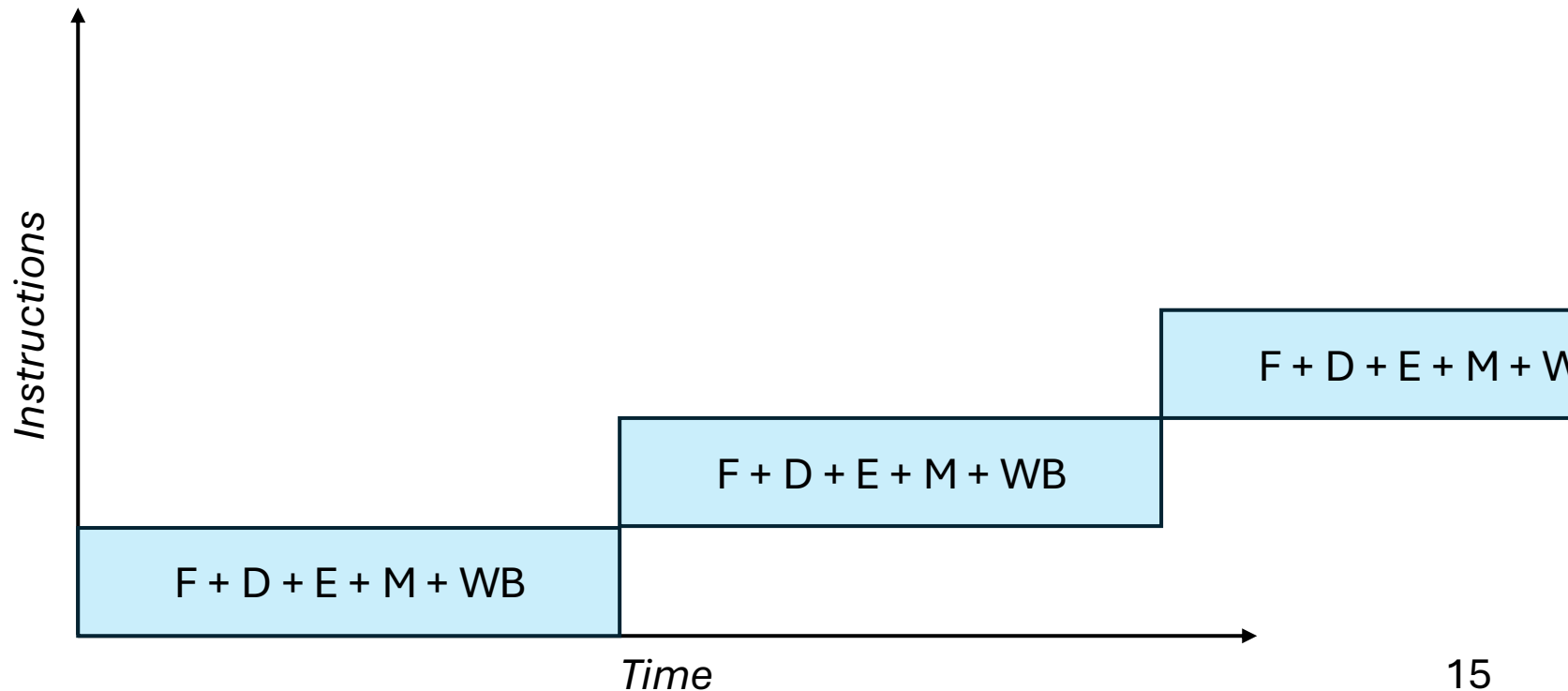
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back


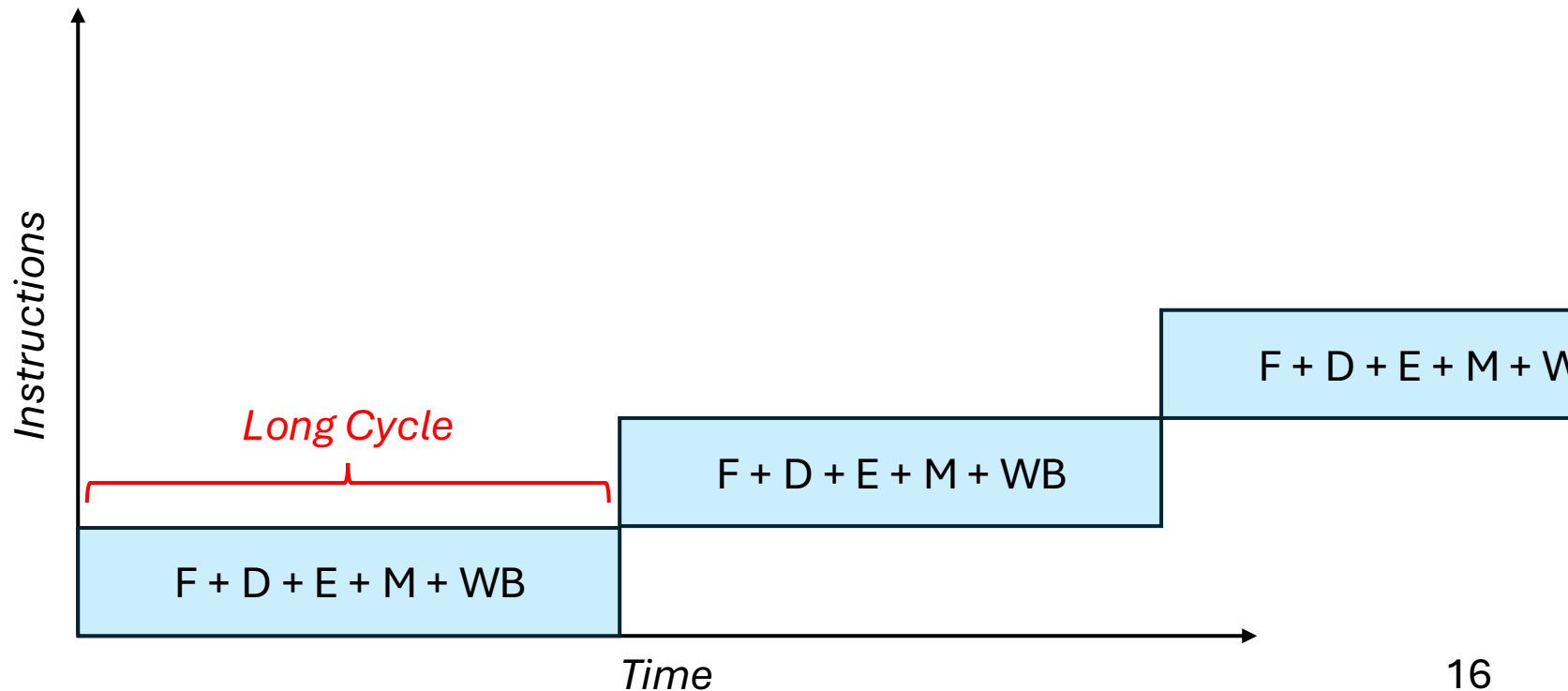
# Pipelining in Modern CPUs


- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back





 
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



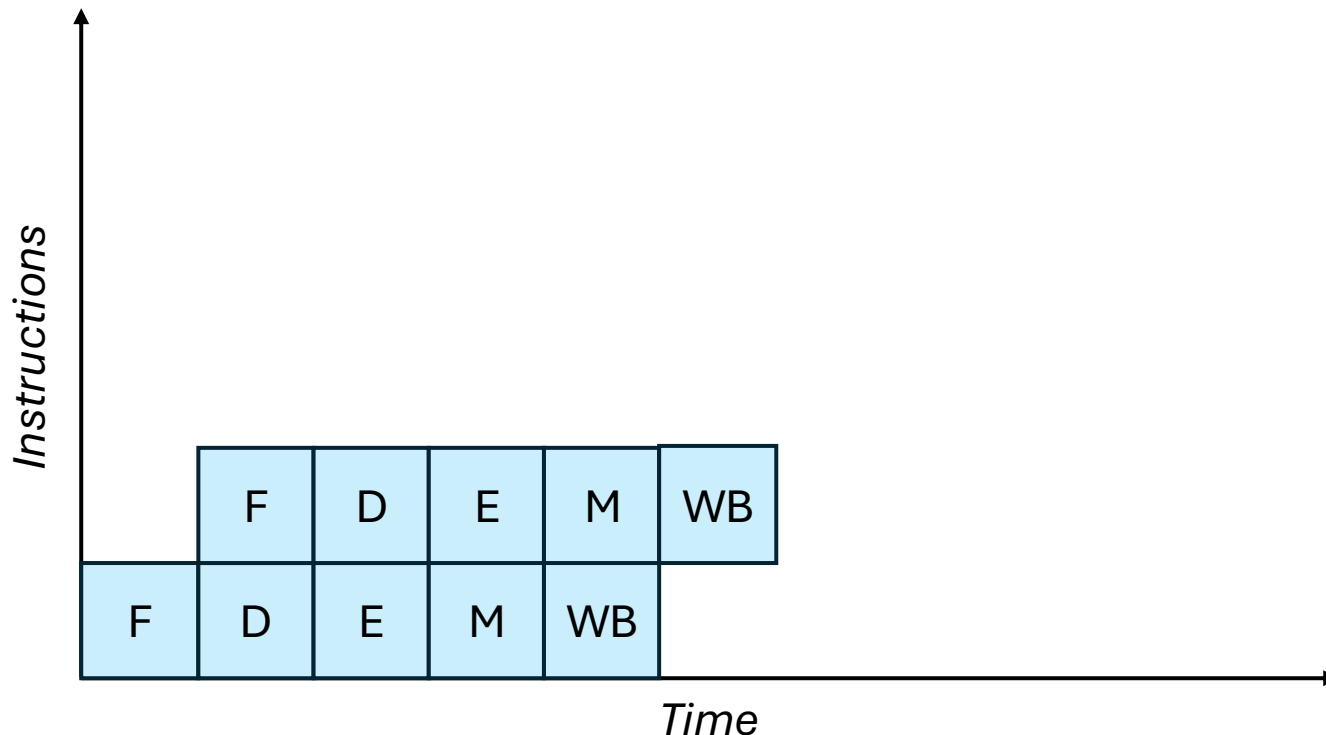
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



 
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



 
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



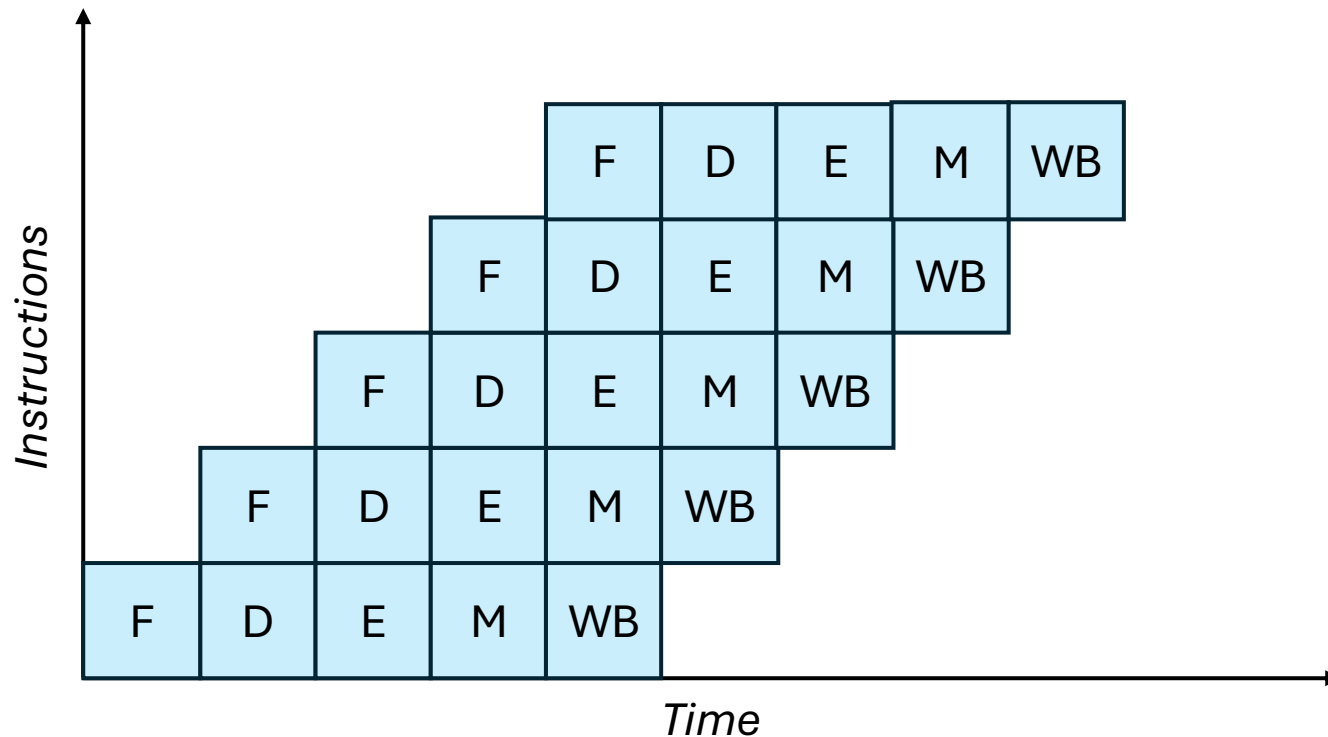
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



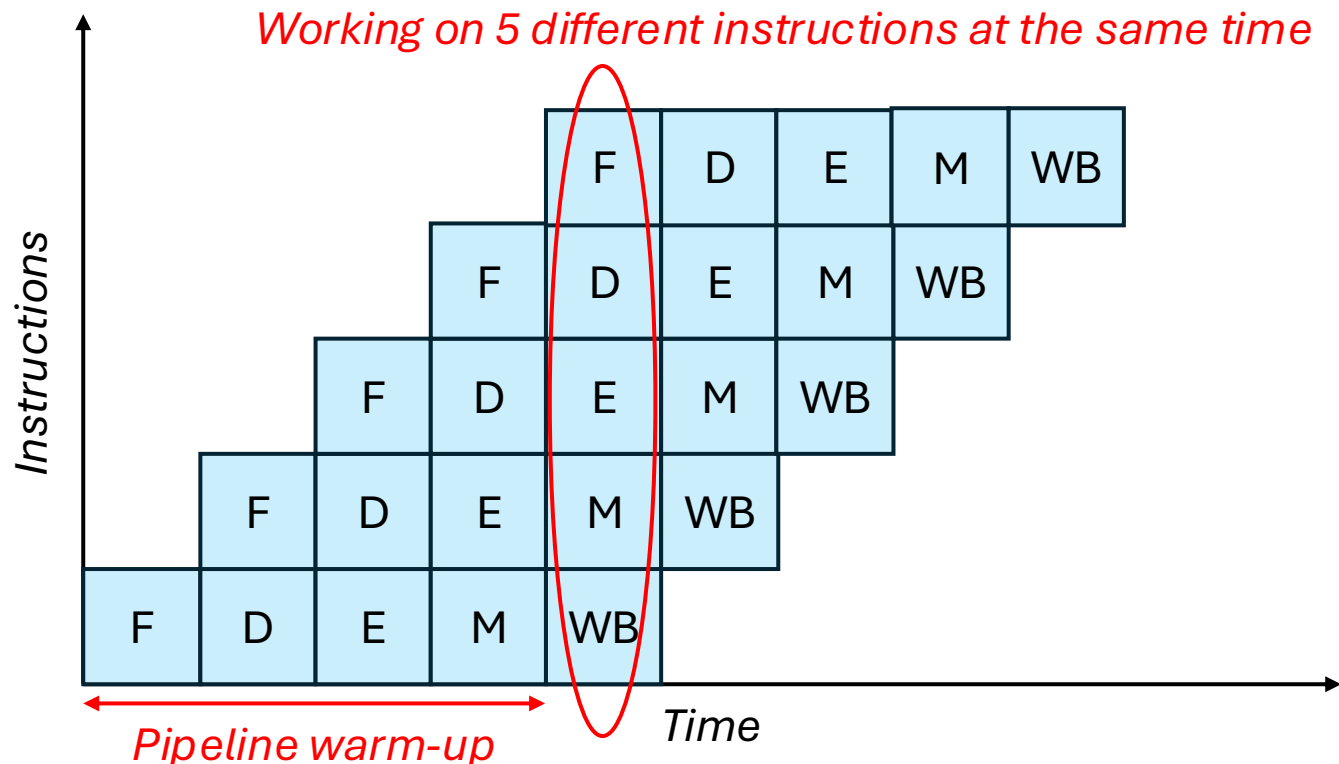
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



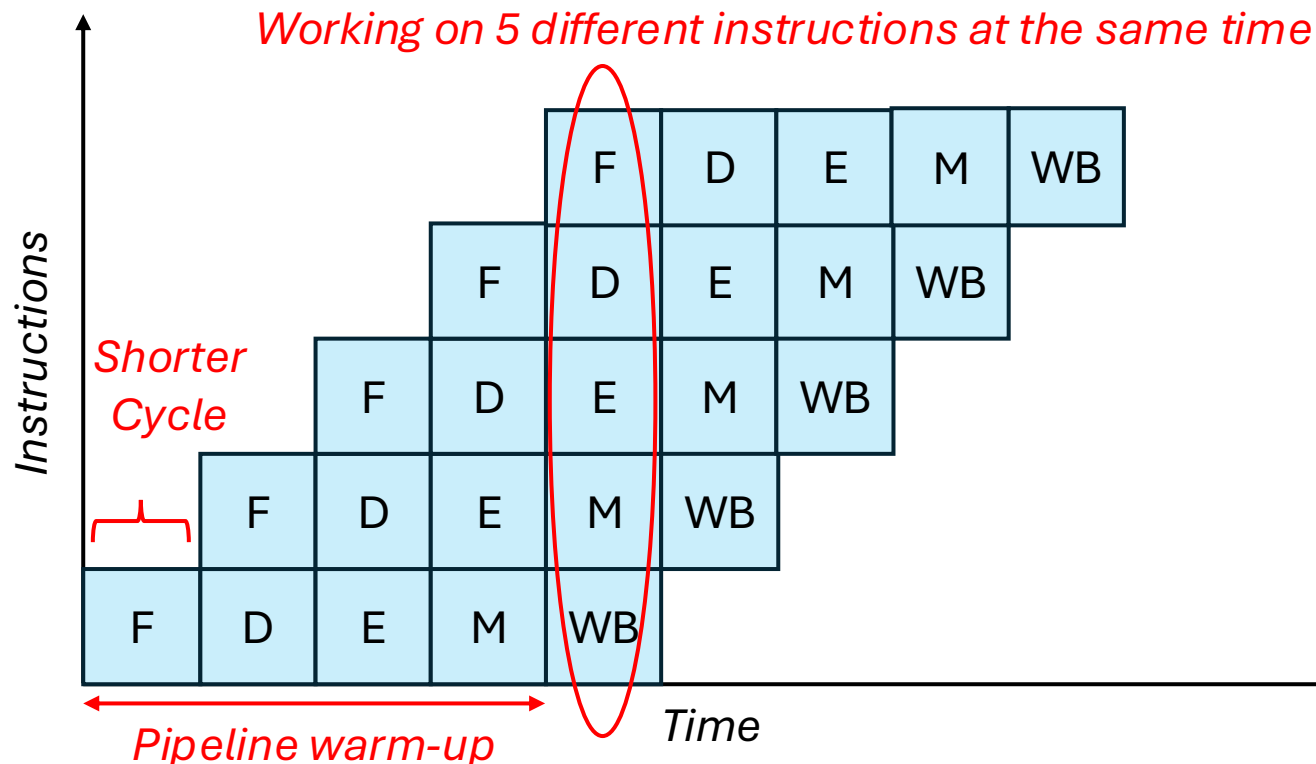
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle


 
# Pipelining in Modern CPUs


- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle





 
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle



 
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle
  - Check for dependencies and stall the pipeline (bubbles)



 
# Pipelining in Modern CPUs

- A simple CPU can execute an entire instruction in 1 cycle
  - Fetch → Decode → Execute → Memory → Write back
- Better CPUs pipeline each state into a cycle
  - Overlap execution of different instructions in the same clock cycle
  - Check for dependencies and stall the pipeline (bubbles)




# Pipelining Digital Circuits

 
 
# Pipelining Digital Circuits


*Registers represented as dashed lines for simplicity*



*Clock period must be  $\geq$  longest path between two registers  
(Critical Path)*
 
# Pipelining Digital Circuits


*Registers represented as dashed lines for simplicity*



*Clock period must be  $\geq$  longest path between two registers  
(Critical Path)*
 
# Pipelining Digital Circuits


*Registers represented as dashed lines for simplicity*



*Clock period must be  $\geq$  longest path between two registers  
(Critical Path)*
 
# Pipelining Digital Circuits

*Registers represented as dashed lines for simplicity*




*Clock period must be  $\geq$  longest path between two registers  
(Critical Path)*


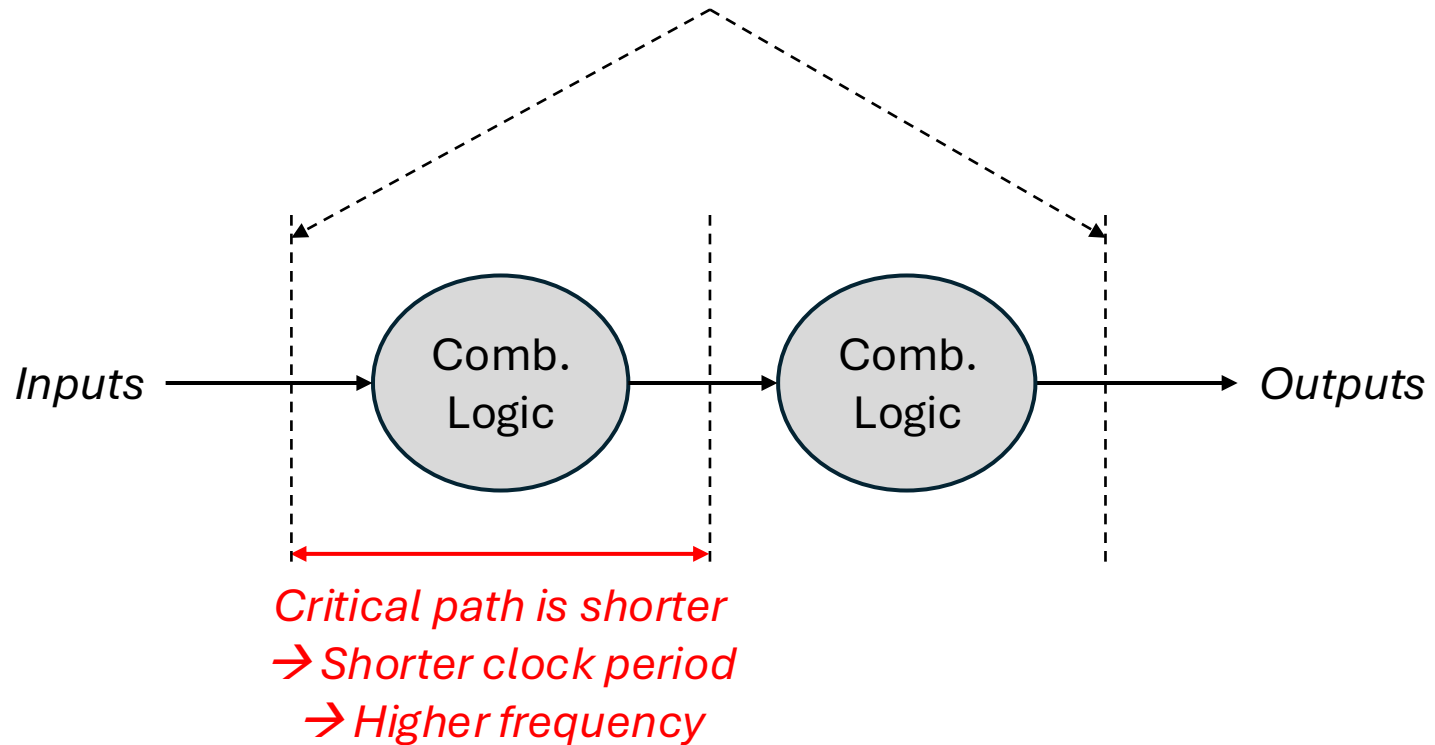
# Pipelining Digital Circuits

*Registers represented as dashed lines for simplicity*



# Pipelining Terminology

- **Throughput:** Operations performed per second (ops/sec)
  - Operations per cycle x cycles per second (frequency)

# Pipelining Terminology

- **Throughput:** Operations performed per second (ops/sec)
  - Operations per cycle x cycles per second (frequency)
- **Latency:** Time taken for an input to propagate through the circuit and produce an output (sec)
  - No. of cycles x clock period

# Pipelining Terminology

- **Throughput:** Operations performed per second (ops/sec)
  - Operations per cycle x cycles per second (frequency)
- **Latency:** Time taken for an input to propagate through the circuit and produce an output (sec)
  - No. of cycles x clock period
- **Clock Period:** Time separation between clock edges
  - Faster clock frequency → smaller clock period
  - Must run the circuit as fast as required by the design specifications

# Pipelining Terminology

- **Throughput:** Operations performed per second (ops/sec)
  - Operations per cycle x cycles per second (frequency)
- **Latency:** Time taken for an input to propagate through the circuit and produce an output (sec)
  - No. of cycles x clock period
- **Clock Period:** Time separation between clock edges
  - Faster clock frequency → smaller clock period
  - Must run the circuit as fast as required by the design specifications
- **Critical Path:** The delay of the longest path between registers
  - Determines the smallest safe clock period to operate at

# Pipelining Effect

For a given circuit, more pipelining means ...

Critical Path ↓

Clock Period ↓

Frequency ↑

No. of Cycles ↑

# Pipelining Effect

For a given circuit, more pipelining means ...

Critical Path ↓

Clock Period ↓

Frequency ↑

No. of Cycles ↑

**Throughput** = Operations per cycle x Frequency

# Pipelining Effect

For a given circuit, more pipelining means ...

Critical Path ↓

Clock Period ↓

Frequency ↑

No. of Cycles ↑

**Throughput** = Operations per cycle x Frequency

**Latency** = No. of Cycles x Clock Period



# Pipelining Effect

For a given circuit, more pipelining means ...

Critical Path ↓

Clock Period ↓

Frequency ↑

No. of Cycles ↑

**Throughput** = Operations per cycle x Frequency

**Latency** = No. of Cycles x Clock Period

*If that's the full  
picture, should we just  
pipeline indefinitely?!*



# Pipelining Effect

For a given circuit, more pipelining means ...

Critical Path ↓

Clock Period ↓

Frequency ↑

No. of Cycles ↑

**Throughput** = Operations per cycle x Frequency

**Latency** = No. of Cycles x Clock Period

*In practice, you typically want  
to optimize one while meeting  
a certain spec on the other*

*If that's the full  
picture, should we just  
pipeline indefinitely?!*



# Pipelining Effect

For a given circuit, more pipelining means ...

Critical Path ↓

Clock Period ↓

Frequency ↑

No. of Cycles ↑

**Throughput** = Operations per cycle x Frequency


**Latency** = No. of Cycles x Clock Period

Silicon Area ↑

Power ↑

Clock Distribution Network Design Complexity ↑



# Example: Polynomial Circuit

 


```
module poly_1stage (  
    input clk,  
    input rst,  
    input [7:0] a,  
    input [7:0] b,  
    input [7:0] c,  
    input [7:0] x,  
    output logic [23:0] y  
);  
  
logic [7:0] r_a, r_b, r_c, r_x;  
  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        r_a <= 0; r_b <= 0;  
        r_c <= 0; r_x <= 0;  
        y <= 0;  
    end else begin  
        // Input registers  
        r_a <= a; r_b <= b;  
        r_c <= c; r_x <= x;  
        // Stage 1  
        y <= ((r_a * r_x) + r_b) * r_x + r_c;  
    end  
end  
  
endmodule
```

# Example: Polynomial Circuit


Clock Period = 11.4ns

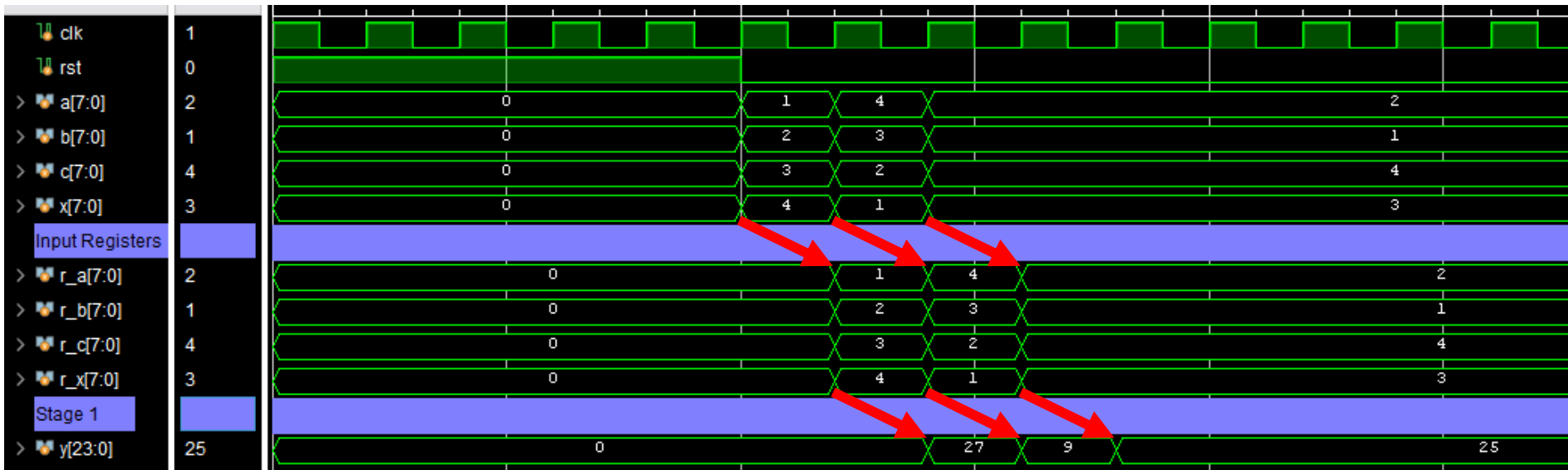 

# Example: Polynomial Circuit

 

# Example: Polynomial Circuit

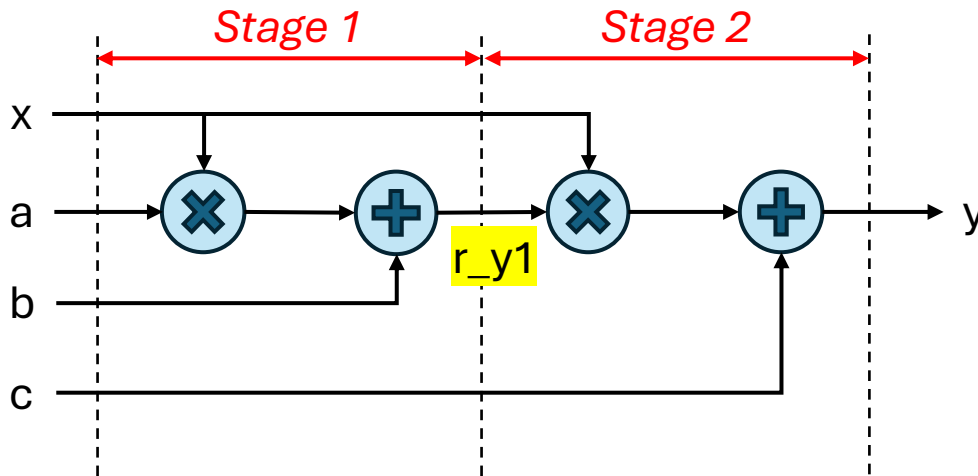

```

module poly_2stage (
    input clk,
    input rst,
    input [7:0] a,
    input [7:0] b,
    input [7:0] c,
    input [7:0] x,
    output logic [23:0] y
);

logic [7:0] r_a, r_b, r_c, r_x;
logic [15:0] r_y1;


always_ff @ (posedge clk) begin
    if (rst) begin
        r_a <= 0; r_b <= 0;
        r_c <= 0; r_x <= 0;
        r_y1 <= 0;
        y <= 0;
    end else begin
        // Input registers
        r_a <= a; r_b <= b;
        r_c <= c; r_x <= x;
        // Stage 1
        r_y1 <= (r_a * r_x) + r_b;

        // Stage 2
        y <= (r_y1 * r_x) + r_c;
    end
end

endmodule

```

# Example: Polynomial Circuit

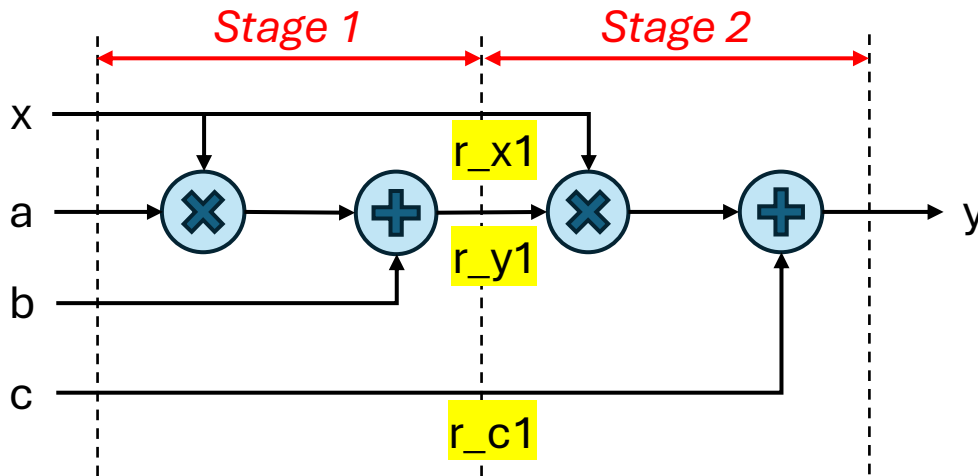

```

module poly_2stage (
    input clk,
    input rst,
    input [7:0] a,
    input [7:0] b,
    input [7:0] c,
    input [7:0] x,
    output logic [23:0] y
);

logic [7:0] r_a, r_b, r_c, r_x;
logic [15:0] r_y1;
logic [7:0] r_x1, r_c1;

always_ff @ (posedge clk) begin
    if (rst) begin
        r_a <= 0; r_b <= 0;
        r_c <= 0; r_x <= 0;
        r_y1 <= 0; r_x1 <= 0; r_c1 <= 0;
        y <= 0;
    end else begin
        // Input registers
        r_a <= a; r_b <= b;
        r_c <= c; r_x <= x;
        // Stage 1
        r_y1 <= (r_a * r_x) + r_b;
        r_x1 <= r_x; r_c1 <= r_c;
        // Stage 2
        y <= (r_y1 * r_x1) + r_c1;
    end
end



endmodule

```




# Example: Polynomial Circuit


Clock Period = 6.9ns

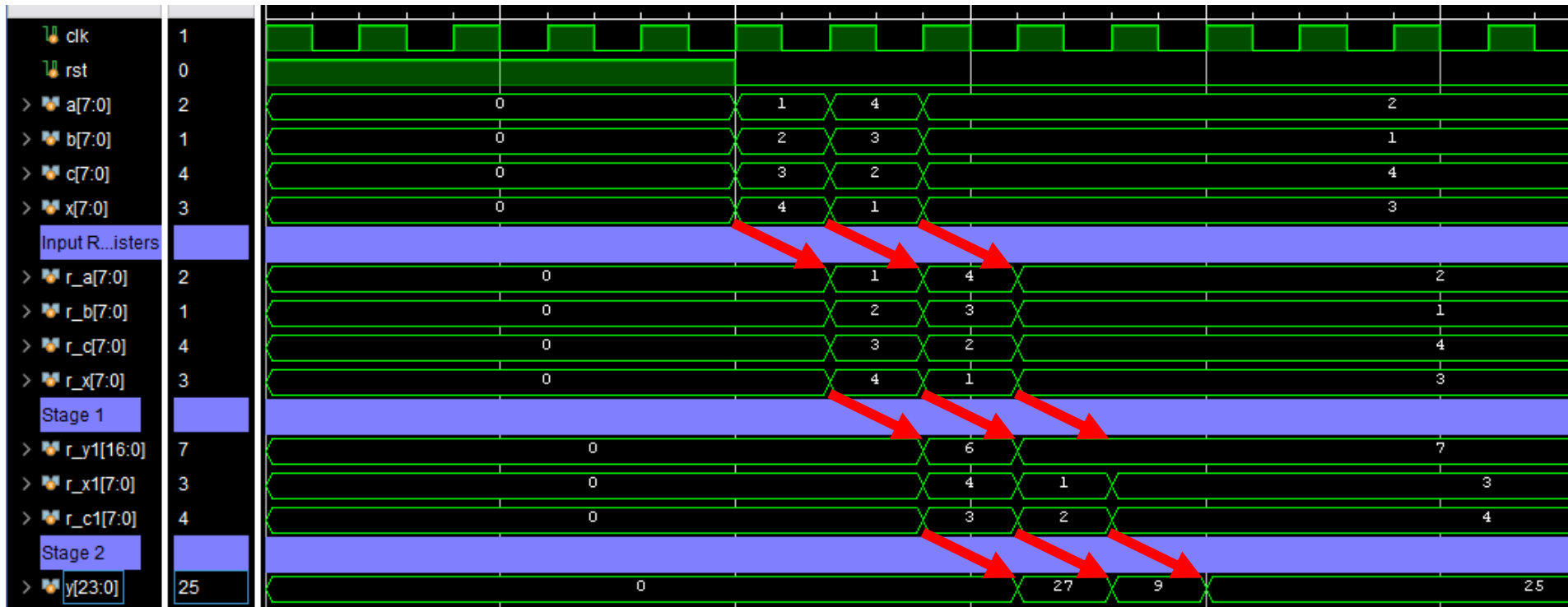 


# Example: Polynomial Circuit

 

# Example: Polynomial Circuit

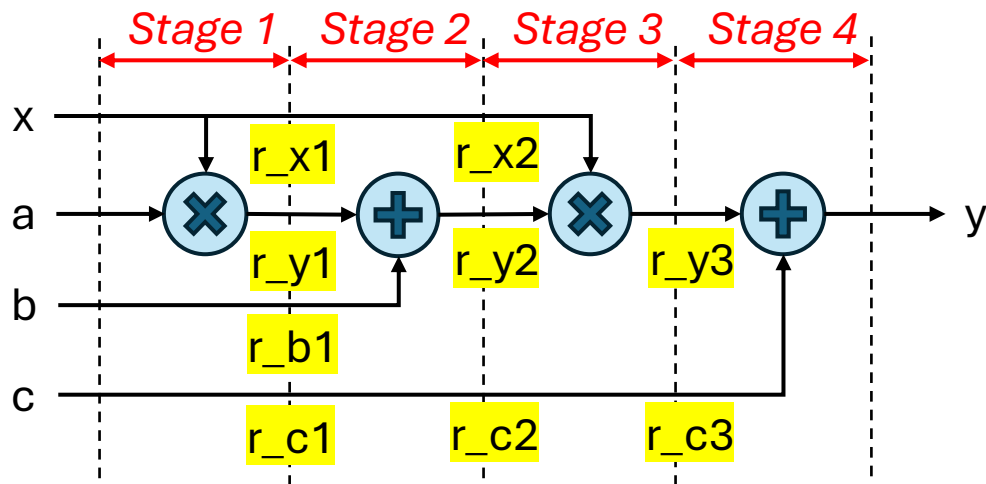

# Example: Polynomial Circuit

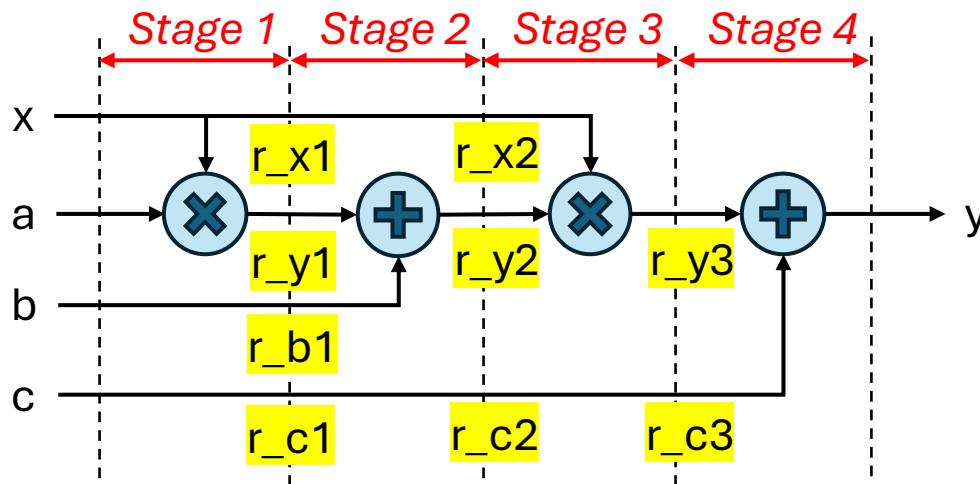

```

module poly_4stage (
    input clk,
    input rst,
    input [7:0] a,
    input [7:0] b,
    input [7:0] c,
    input [7:0] x,
    output logic [23:0] y
);

    logic [7:0] r_a, r_b, r_c, r_x;
    logic [15:0] r_y1;
    logic [7:0] r_x1, r_b1, r_c1;
    logic [15:0] r_y2;
    logic [7:0] r_x2, r_c2;
    logic [23:0] r_y3;
    logic [7:0] r_c3;

```

```



always_ff @ (posedge clk) begin
    if (rst) begin
        r_a <= 0; r_b <= 0;
        r_c <= 0; r_x <= 0;
        r_y1 <= 0; r_y2 <= 0; r_y3 <= 0;
        r_x1 <= 0; r_b1 <= 0; r_c1 <= 0;
        r_x2 <= 0; r_c2 <= 0;
        r_c3 <= 0;
        y <= 0;
    end else begin
        // Input registers
        r_a <= a; r_b <= b;
        r_c <= c; r_x <= x;
        // Stage 1
        r_y1 <= (r_a * r_x);
        r_x1 <= r_x; r_b1 <= r_b; r_c1 <= r_c;
        // Stage 2
        r_y2 <= r_y1 + r_b1;
        r_x2 <= r_x1; r_c2 <= r_c1;
        // Stage 3
        r_y3 <= r_y2 * r_x2;
        r_c3 <= r_c2;
        // Stage 4
        y <= r_y3 + r_c3;
    end
end

endmodule

```

# Example: Polynomial Circuit

Clock Period = 5.4ns

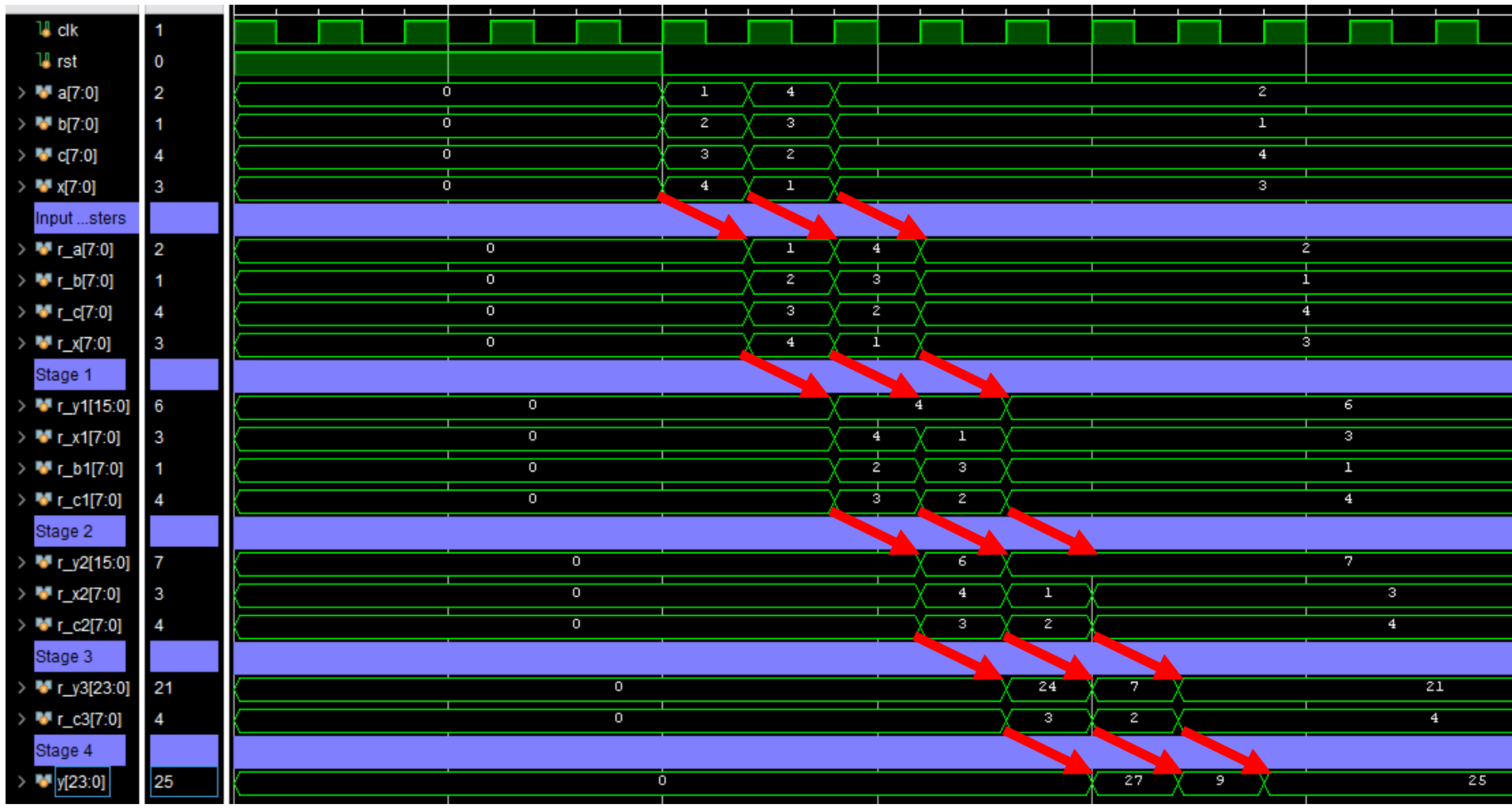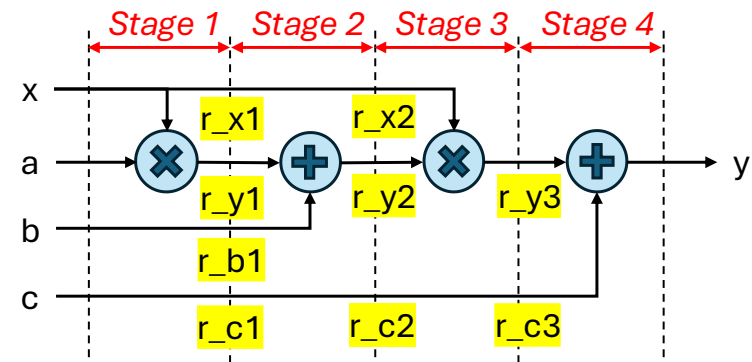

# Pipelined Polynomial Circuit Analysis

## 1 Stage

Clock Period = 11.4ns

Frequency = 88 MHz

No. of Ops = 4

Throughput = 352 MOPS

Latency =  $2 \times 11.4\text{ns} = 22.8\text{ns}$

Registers =  
 $(4 \times 8) + 24 = 56$

## 2 Stages

Clock Period = 6.9ns

Frequency = 145 MHz

No. of Ops = 4

Throughput = 580 MOPS

Latency =  $3 \times 6.9\text{ns} = 20.7\text{ns}$

Registers =  
 $(6 \times 8) + 16 + 24 = 88$

## 4 Stages

Clock Period = 5.4ns

Frequency = 185 MHz

No. of Ops = 4


Throughput = 740 MOPS

Latency =  $5 \times 5.4\text{ns} = 27\text{ns}$

Registers =  
 $(10 \times 8) + (2 \times 16) + (2 \times 24) = 160$

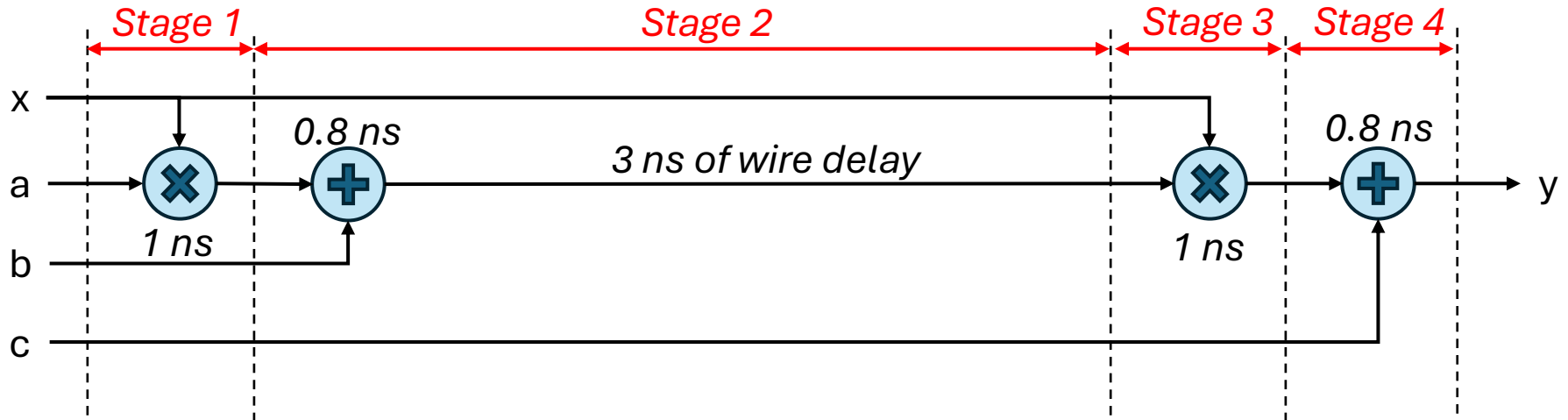
# Wire Pipelining

- Remember that wires do not have zero delay
- In modern semiconductor process nodes, most of the delay is in the wires and not the logic


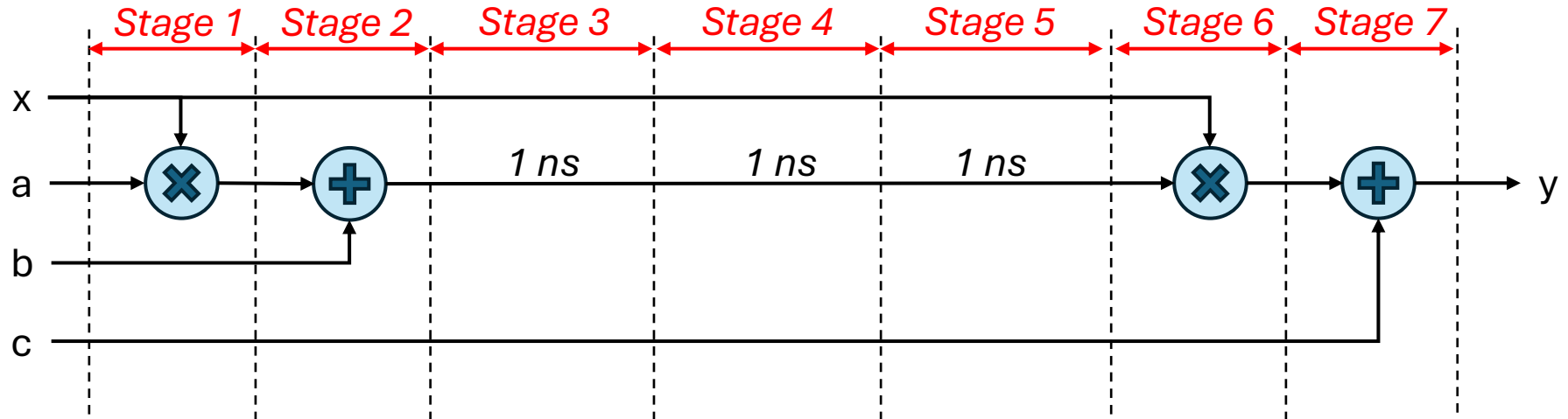
# Wire Pipelining


- Remember that wires do not have zero delay
- In modern semiconductor process nodes, most of the delay is in the wires and not the logic
- Sometimes we need to pipeline wires to improve frequency




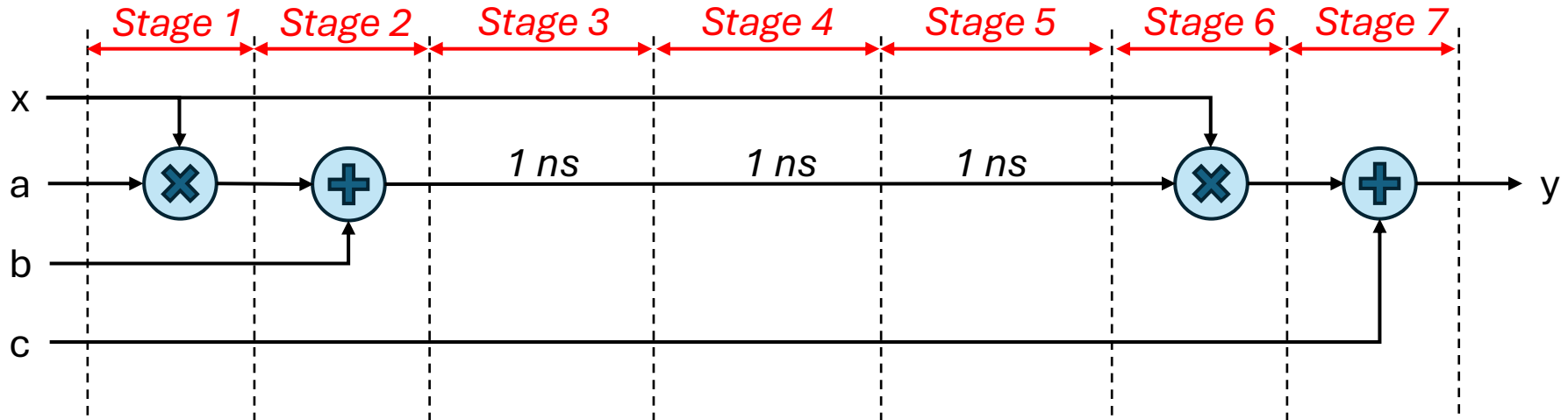
# Wire Pipelining

- Remember that wires do not have zero delay
- In modern semiconductor process nodes, most of the delay is in the wires and not the logic
- Sometimes we need to pipeline wires to improve frequency



*How do I know which wires  
to add pipeline registers to?*




# Wire Pipelining

- To avoid frequent code changes when experimenting with different wire pipelining depths, we can implement a parameterizable wire pipelining “module”
- Instantiate between design modules and change NUM\_STAGES parameter to experiment with different pipeline depths

```
module wire_pipeline # (  
    parameter DATAW = 8,  
    parameter NUM_STAGES = 3  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] data_in,  
    output [DATAW-1:0] data_out  
);  
  
    logic [DATAW-1:0] r_data [0:NUM_STAGES-1];  
    integer i;  
  
    always_ff @ (posedge clk) begin  
        if (rst) begin  
            for (i=0; i<NUM_STAGES; i=i+1) begin  
                r_data[i] <= 0;  
            end  
        end else begin  
            r_data[0] <= data_in;  
            for (i=1; i<NUM_STAGES; i=i+1) begin  
                r_data[i] <= r_data[i-1];  
            end  
        end  
    end  
    assign data_out = r_data[NUM_STAGES-1];  
endmodule
```


 
# Pipeline Bubbles Revisited

- In a CPU processing pipeline, bubbles are injected due to stalls caused by data dependencies



  
# Pipeline Bubbles Revisited

- In a CPU processing pipeline, bubbles are injected due to stalls caused by data dependencies
- In custom datapaths (e.g., our polynomial circuit), bubbles can be injected due to absence of input data
  - We implicitly assume that new inputs will arrive every cycle
  - This is not necessarily the case in many designs
  - Data arrival uncertainty is not known at design time



 
# Handling Bubbles in Custom Datapaths

- When no new inputs, **invalid** data is injected in the pipeline
- We need to know the output corresponding to invalid inputs such that downstream modules can ignore it:
  - Add new input and output “valid” ports
  - Each input arrives coupled with a valid tag
  - Valid tag propagates through the circuit from the input valid port to the output valid port with a delay matching the datapath pipeline latency



 
# Handling Bubbles in Custom Datapaths

- When no new inputs, **invalid** data is injected in the pipeline
- We need to know the output corresponding to invalid inputs such that downstream modules can ignore it:
  - Add new input and output “valid” ports
  - Each input arrives coupled with a valid tag
  - Valid tag propagates through the circuit from the input valid port to the output valid port with a delay matching the datapath pipeline latency



 
# Handling Bubbles in Custom Datapaths

- When no new inputs, **invalid** data is injected in the pipeline
- We need to know the output corresponding to invalid inputs such that downstream modules can ignore it:
  - Add new input and output “valid” ports
  - Each input arrives coupled with a valid tag
  - Valid tag propagates through the circuit from the input valid port to the output valid port with a delay matching the datapath pipeline latency


 
# Handling Bubbles in Custom Datapaths


- When no new inputs, **invalid** data is injected in the pipeline
- We need to know the output corresponding to invalid inputs such that downstream modules can ignore it:
  - Add new input and output “valid” ports
  - Each input arrives coupled with a valid tag
  - Valid tag propagates through the circuit from the input valid port to the output valid port with a delay matching the datapath pipeline latency





 
# Handling Bubbles in Custom Datapaths

- When no new inputs, **invalid** data is injected in the pipeline
- We need to know the output corresponding to invalid inputs such that downstream modules can ignore it:
  - Add new input and output “valid” ports
  - Each input arrives coupled with a valid tag
  - Valid tag propagates through the circuit from the input valid port to the output valid port with a delay matching the datapath pipeline latency


 
# Handling Bubbles in Custom Datapaths

- When no new inputs, **invalid** data is injected in the pipeline
- We need to know the output corresponding to invalid inputs such that downstream modules can ignore it:
  - Add new input and output “valid” ports
  - Each input arrives coupled with a valid tag
  - Valid tag propagates through the circuit from the input valid port to the output valid port with a delay matching the datapath pipeline latency



# Handling Bubbles in Custom Datapaths


```
module poly_4stage_bubbles (  
    input  clk,  
    input  rst,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    input  i_valid,  
    output [23:0] y,  
    output o_valid  
);
```

```
poly_4stage poly_inst (  
    .clk(clk),  
    .rst(rst),  
    .a(a),  
    .b(b),  
    .c(c),  
    .x(x),  
    .y(y)  
);
```

```
wire_pipeline # (  
    .DATAW(1),  
    .NUM_STAGES(5)  
) valid_pipeline (  
    .clk(clk),  
    .rst(rst),  
    .data_in(i_valid),  
    .data_out(o_valid)  
);
```


```
endmodule
```

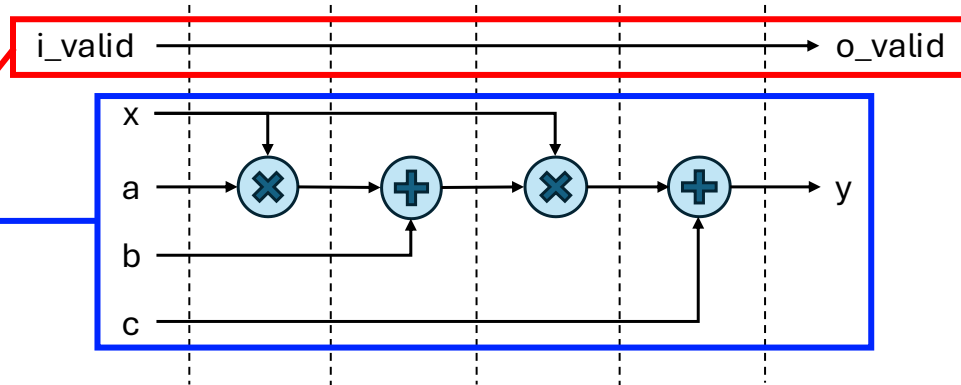**This is just a wire pipeline with 1-bit data and 5 pipeline registers on the path**



**This is the same 4-stage polynomial circuit we implemented before**

# Handling Bubbles in Custom Datapaths

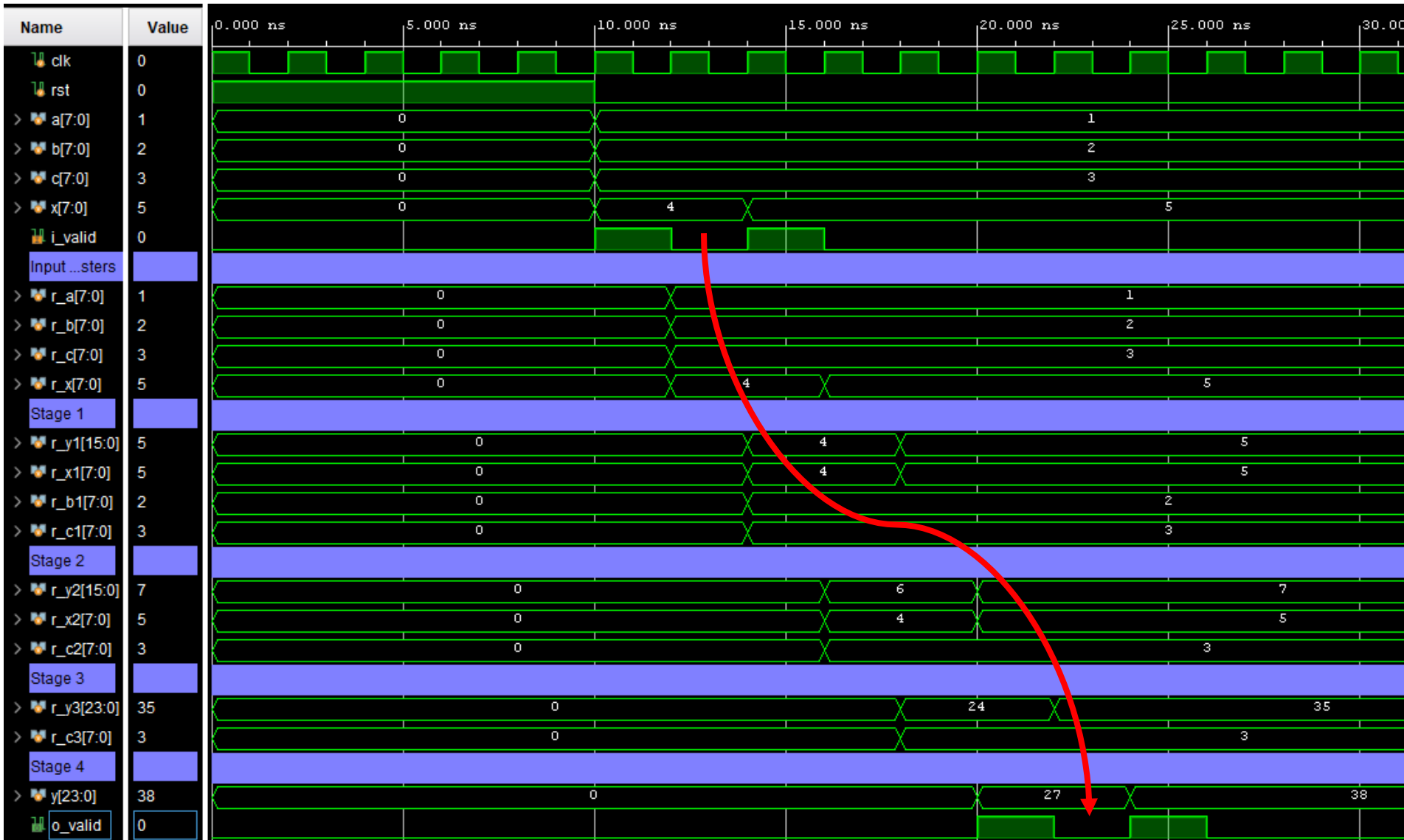

# Next Lecture

Can we pipeline any circuit?!