


**ECE 327/627**

**Digital Hardware Systems**

**Tutorial 1 Solutions**
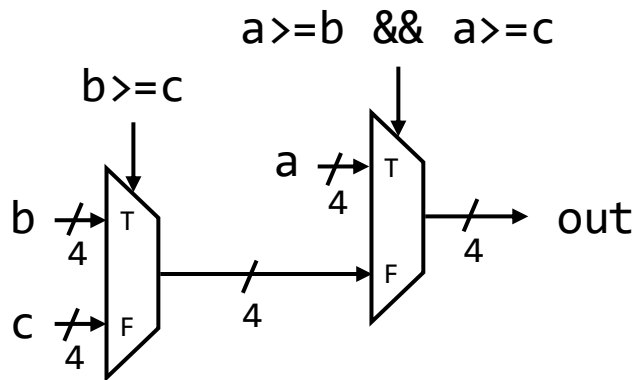
# Q1

What hardware circuit is synthesized from this code?



**Step 1:** Determine input & output interfaces

**Step 2:** *always\_comb* means it's a combinational circuit and output is not registered


**Step 3:** Nested if-else translates to a chain of multiplexers

**Step 4:** Priority of nested ifs determines the order of multiplexers. Highest priority (i.e., first if statement) is the multiplexer closest to the output

```
module q1 (  
    input [3:0] a,  
    input [3:0] b,  
    input [3:0] c,  
    output logic [3:0] out  
);  
  
always_comb begin  
    if (a>=b && a>=c) begin  
        out = a;  
    end else if (b>=c) begin  
        out = b;  
    end else begin  
        out = c;  
    end  
end  
  
endmodule
```
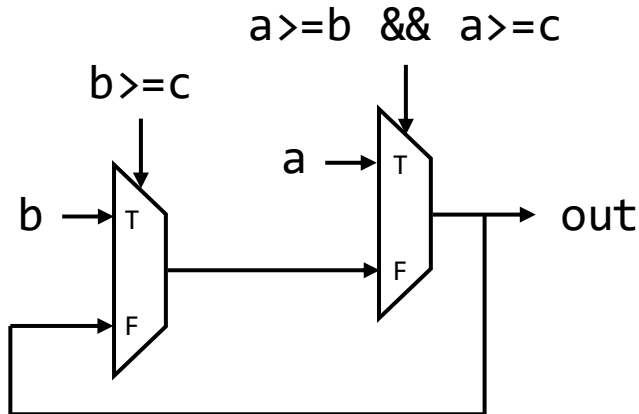
## Q2

Write the SystemVerilog code that is synthesized into the following circuit.




```
module q2 (  
    input [3:0] a,  
    input [3:0] b,  
    input [3:0] c,  
    output logic [3:0] out  
);  
  
always_comb begin  
    if (a>=b && a>=c) begin  
        out = a;  
    end else if (b>=c) begin  
        out = b;  
    end  
end  
  
endmodule
```

Incomplete definitions of if-else statements in always blocks results in a combinational feedback from output to input. This is the logical representation of an inferred latch at the output. Almost always you do not mean to have latches in your design. Designing circuits with latches is tricky and needs careful consideration to avoid metastability.
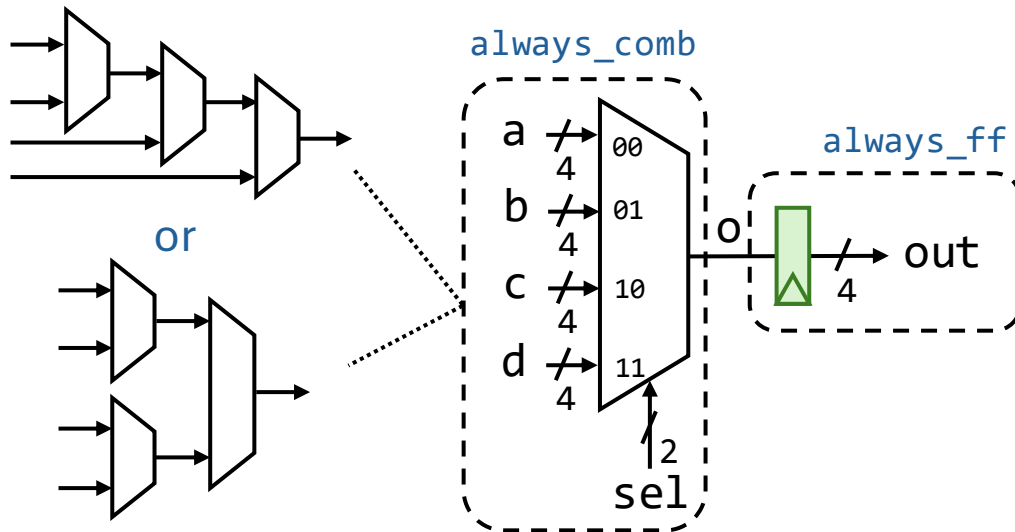
## Q3

What hardware circuit is synthesized from this code?




This circuit has an `always_ff` and an `always_comb` blocks. We can reason about each block separately and translate it to hardware, then stitch them together. Since the order of the if-else statement doesn't matter in this case (mutually exclusive – using `==` and not relational operators), you can think of it as a flat 4:1 multiplexer. This multiplexer can be implemented using three 2:1 multiplexers organized in a chain or a tree.

```
module q3 (  
    input [3:0] a,  
    input [3:0] b,  
    input [3:0] c,  
    input [3:0] d,  
    input [1:0] sel,  
    input clk,  
    input rst,  
    output logic [3:0] out  
);  
  
logic [3:0] o;  
  
always_comb begin  
    if (sel == 2'b00) o <= a;  
    else if (sel == 2'b01) o <= b;  
    else if (sel == 2'b10) o <= c;  
    else o <= d;  
end  
  
always_ff @ (posedge clk) begin  
    if (rst) out <= 4'd0;  
    else out <= o;  
end  
  
endmodule
```
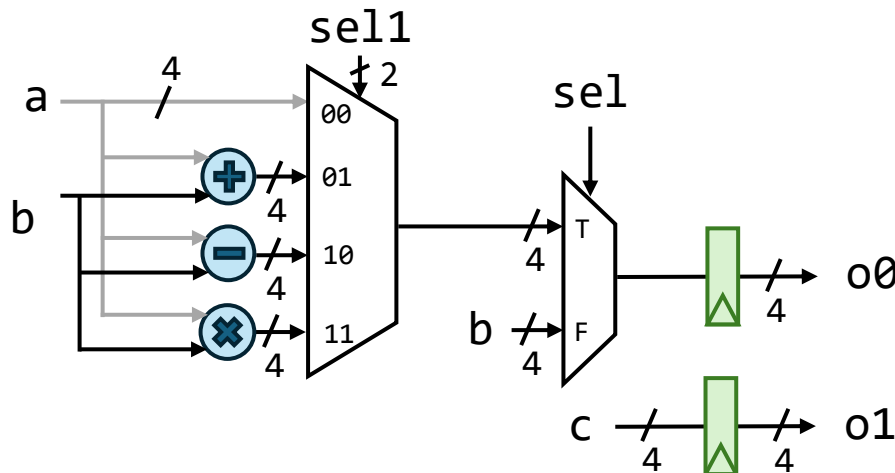
# Q4

What hardware circuit is synthesized from this code?



Having an `always_ff` means that both outputs `o0` and `o1` are registered. This code can be refactored as:

```
o0 <= b;
if (sel) o0 <= // some value depending on case
if (!sel) o1 <= b;
o1 <= c;
```

An assignment before an if with a missing else represents the false (default) branch. An assignment after an if-else condition results in all previous assignments to be ignored. Finally, the case statement is translated to a flat 4:1 multiplexer. Remember, in SystemVerilog, last assignment wins!

```
module q4 (
    input [3:0] a,
    input [3:0] b,
    input [3:0] c,
    input sel,
    input [1:0] sel1,
    input clk,
    output logic [3:0] o0,
    output logic [3:0] o1
);

always_ff @ (posedge clk) begin
    o0 <= b;
    if (sel) begin
        case (sel1)
            2'b00: o0 <= a;
            2'b01: o0 <= a+b;
            2'b10: o0 <= a-b;
            2'b11: o0 <= a*b;
            default: o0 <= 0;
        endcase
    end else if (!sel) begin
        o1 <= b;
    end
    o1 <= c;
end

endmodule
```

## Q5

Draw the diagram of the circuit generated when elaborating this SystemVerilog code. What should be the values of M & L for this circuit to be functionally correct?

```
module q5 # (  
    parameter K = 4,  
    parameter N = 8,  
    parameter M = ...,  
    parameter L = ...  
)(  
    input clk,  
    input rst,  
    input [N-1:0] a [0:K-1],  
    input [N-1:0] b [0:K-1],  
    output logic [M-1:0] c  
);  
  
logic [L-1:0] tmp1 [0:K-1];  
logic [M-1:0] tmp2;  
  
integer i, j;
```

```
always_comb begin  
    for (i=0; i<K; i=i+1) begin  
        tmp1[i] = a[i] * b[i];  
    end  
end  
  
always_comb begin  
    tmp2 = 0;  
    for (j=0; j<K; j=j+1) begin  
        tmp2 = tmp2 + tmp1[j];  
    end  
end  
  
always_ff @ (posedge clk) begin  
    if (rst) c <= 'd0;  
    else c <= tmp2;  
end  
  
endmodule
```

## Q5

Draw the diagram of the circuit generated when elaborating this SystemVerilog code. What should be the values of M & L for this circuit to be functionally correct?

