

**ECE 327/627**

**Digital Hardware Systems**

**Tutorial 2**

# Q1

Write the SystemVerilog code for a combinational circuit that sorts two inputs (a, b) into two outputs (o1, o2) such that  $o1 \geq o2$ . Assume both inputs are 4-bit numbers.

```
module q1 (  
    input  [3:0] a,  
    input  [3:0] b,  
    output [3:0] o1,  
    output [3:0] o2  
);  
  
assign o1 = (a>=b)? a : b;  
assign o2 = (a>=b)? b : a;  
  
endmodule
```


*(Simple) purely  
combinational circuits can  
be described using  
continuous assignments or  
always\_comb blocks.*

```
module q1 (  
    input  [3:0] a,  
    input  [3:0] b,  
    output [3:0] o1,  
    output [3:0] o2  
);  
  
logic [3:0] out1, out2;  
  
always_comb begin  
    if (a>=b) begin  
        out1 = a; out2 = b;  
    end else begin  
        out1 = b; out2 = a;  
    end  
end  
  
assign o1 = out1;  
assign o2 = out2;  
  
endmodule
```


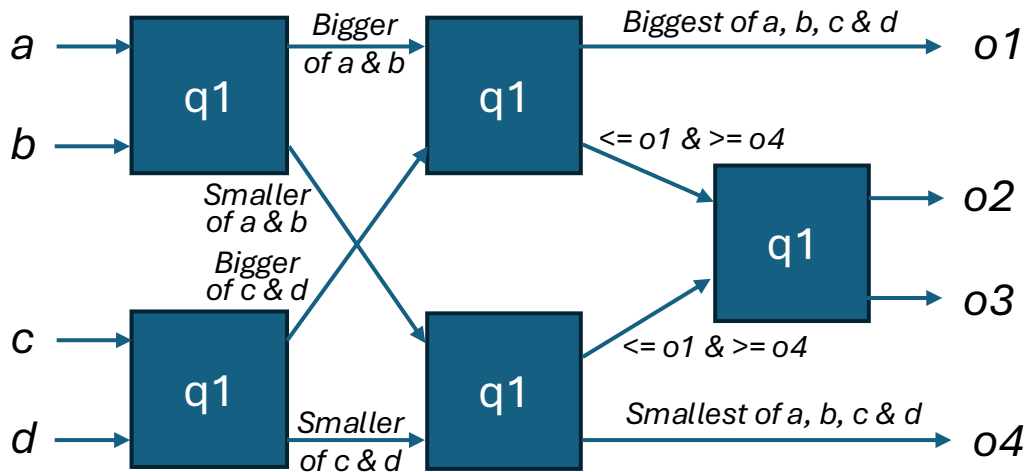
## Q2

Using the circuit you implemented in Q1, design a circuit to sort four inputs (a,b,c,d) into four outputs (o1,o2,o3,o4) such that  $o1 \geq o2 \geq o3 \geq o4$ .



```
module q2 (  
    input  [3:0] a,  
    input  [3:0] b,  
    input  [3:0] c,  
    input  [3:0] d,  
    output [3:0] o1,  
    output [3:0] o2,  
    output [3:0] o3,  
    output [3:0] o4  
);  
  
    logic [3:0] t1,t2,t3,t4,t5,t6;  
  
    q1 q1_inst0(a, b, t1, t2);  
    q1 q1_inst1(c, d, t3, t4);  
  
    q1 q1_inst2(t1, t3, o1, t5);  
    q1 q1_inst3(t2, t4, t6, o4);  
  
    q1 q1_inst4(t5, t6, o2, o3);  
  
endmodule
```

## Q3

Given  $N$  numbers, each is 1-bit wide:

(a) How many bits will be required to represent the sum of these  $N$  numbers?

*The highest value the sum of  $N$  1-bit numbers can be is  $N$ . Therefore, we need  $\lceil \log_2(N) \rceil + 1$  bits to represent this value.*

*For example:*


- *If  $N = 8$ , we need 4 bits*
- *If  $N = 15$ , we need 4 bits*
- *If  $N = 16$ , we need 5 bits*
- *...*

## Q3

Given  $N$  numbers, each is 1-bit wide:

(b) Design hardware to add  $N$  numbers in parallel. You can use as many 2-input adders as you need to compute the sum in 1 clock cycle. How many adders are needed? How many bits each adder will need?

*Showing the circuit for  $N = 8$*

 

*Latency = 1 cycle (to sum  $N$  numbers)*

*# levels ( $L$ ) =  $\text{ceil}(\log_2 N)$*

*Delay =  $L \times t_{\text{adder}}$*

*# adders =  $N - 1$*

*Could be built as a chain instead of a tree*

*Latency = 1 cycle (to sum  $N$  numbers)*

*# levels ( $L$ ) =  $N - 1$*


*Delay =  $L \times t_{\text{adder}}$*

*# adders =  $N - 1$*

## Q3

Given  $N$  numbers, each is 1-bit wide:

 (c) Design hardware to add  $N$  numbers sequentially using a single adder. How many cycles are needed to sum these numbers? How many bits will the adder need?



*Showing the circuit for  $N = 8$  (needs 4 bits to represent the output)*

*Instead of pushing  $N$  inputs at the same time, push them sequentially one at a time over  $N$  cycles.*

*Latency =  $N$  cycle (to sum  $N$  numbers)*

*# levels ( $L$ ) = 1*

*Delay =  $L \times t_{\text{adder}}$*

*# adders = 1 (regardless of  $N$ )*