

ECE 327/627

Digital Hardware Systems

Lecture 6: FSM Examples

Andrew Boutros


andrew.boutros@uwaterloo.ca

Some Logistics

- Lab 1 is due tomorrow!
 - Worth **5%** of the total course grade for ECE 327
 - Worth **3%** of the total course grade for ECE 627
 - Deadline **January 23 @ 11:59 pm**
- Lab 1 assessment quiz in the lab sessions of next week
 - Schedule posted by Maran on Piazza
 - Please be there on time for your assessment slot
- Lab 2 will be released tomorrow ... stay tuned!


In The Previous Lecture ...

 - Introduction to finite state machines (FSMs)
 - What are FSMs?
 - Visual representation of FSMs
 - FSM design recipe
- Simple counter example
 - Free-running
 - Externally enabled
 - Synchronizing outputs and state transitions




Warming Up Example

Counter FSM from last lecture ...

 


Warming Up Example

 Counter FSM from last lecture with external enable signal ...



Warming Up Example

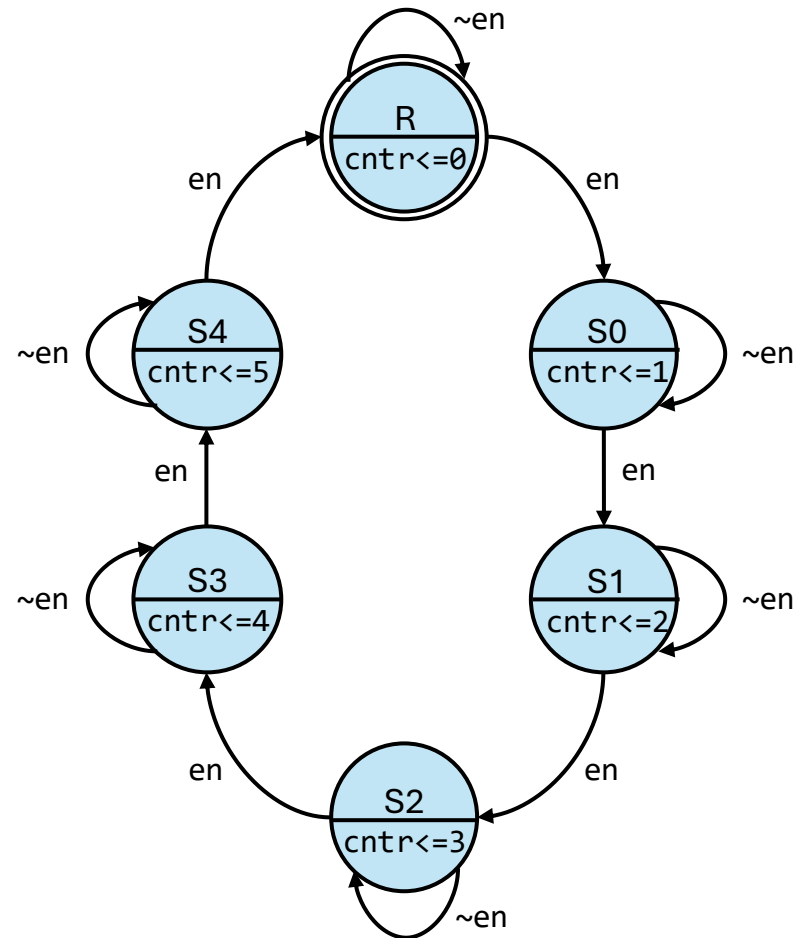What to change to add a count up/down option?



Warming Up Example

```
module cnt5_en (  
    input  clk,  
    input  rst,  
    input  en,  
    output logic [2:0] cnt  
);  
  
enum {R,S0,S1,S2,S3,S4} state, next_state;  
logic [2:0] cnt_val;  
  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        cnt <= 'd0;  
        state <= R;  
    end else begin  
        cnt <= cnt_val;  
        state <= next_state;  
    end  
end
```

```
always_comb begin: state_decoder  
    case (state)  
        R : next_state = (en)? S0 : R;  
        S0: next_state = (en)? S1 : S0;  
        S1: next_state = (en)? S2 : S1;  
        S2: next_state = (en)? S3 : S2;  
        S3: next_state = (en)? S4 : S3;  
        S4: next_state = (en)? R  : S4;  
        default: next_state = R;  
    endcase  
end  
  
always_comb begin: out_decoder  
    case (state)  
        R : cnt_val = 0;  
        S0: cnt_val = 1;  
        S1: cnt_val = 2;  
        S2: cnt_val = 3;  
        S3: cnt_val = 4;  
        S4: cnt_val = 5;  
        default: cnt_val = 0;  
    endcase  
end  
  
endmodule
```

What changes in the SystemVerilog code?




Example: Chess Clock

- Two count down clocks for players $P1$ & $P2$
- Set initial time budget (T_INIT) on both clocks (e.g., 10 mins)
- A player loses when their time counts down to zero
- After $P1$ finishes turn, press the button:
 - Countdown stops for $P1$
 - A time bonus (T_BONUS) is added to $P1$ (e.g., 10 sec)
 - Countdown starts for $P2$
- The two clocks are never running at the same time




Source: digitalgametechnology.com


Example: Chess Clock (FSM Design)

 

Example: Chess Clock (FSM Design)

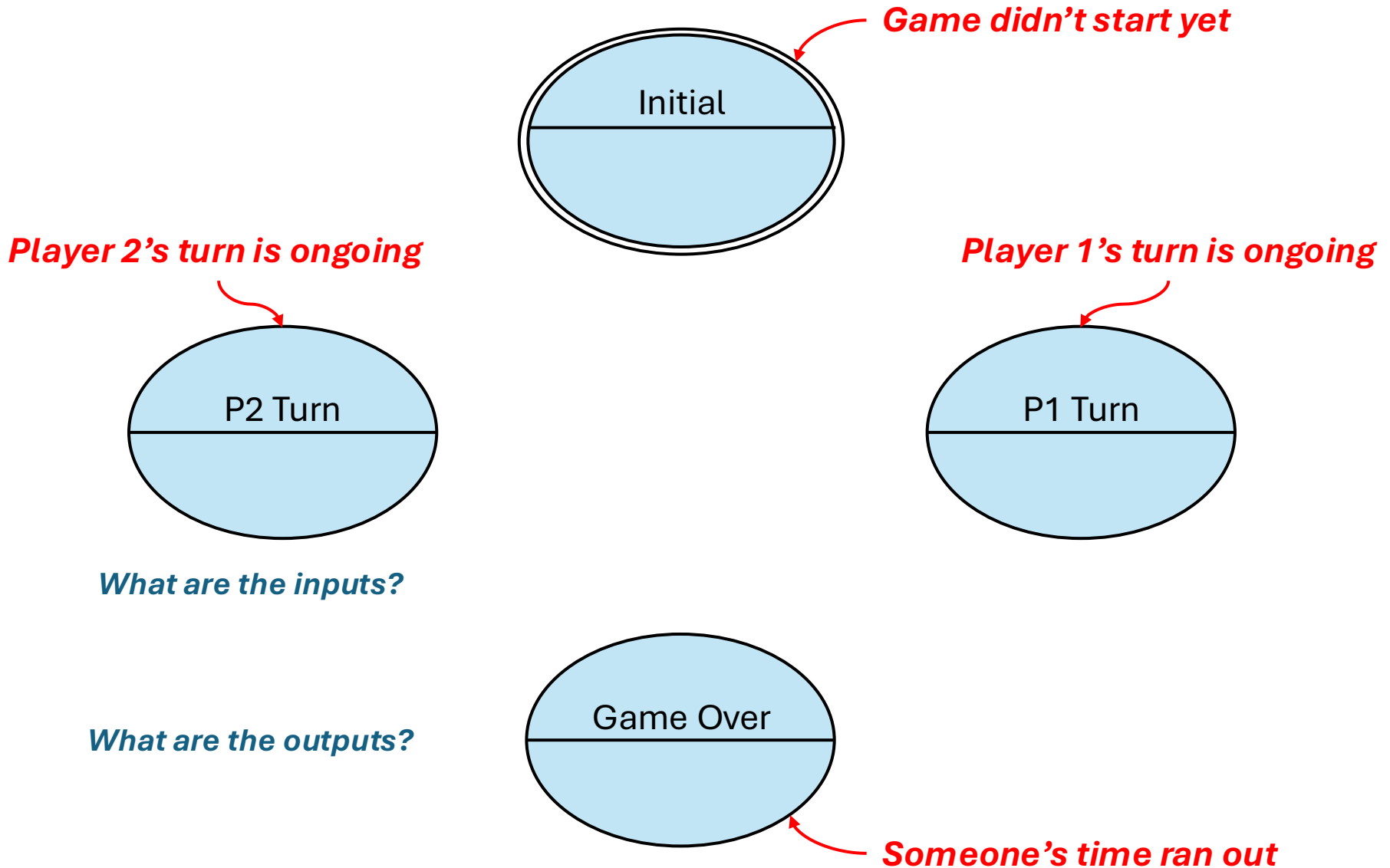

Example: Chess Clock (FSM Design)

 


What are the inputs?

1. input button specifying which player's turn it is (turn)


What are the outputs?

1. time remaining for both players (p1_t, p2_t)
2. flag specifying if a player's time is out (gameover)


Example: Chess Clock (FSM Design)

 


Example: Chess Clock (FSM Design)

 


Example: Chess Clock (FSM Design)

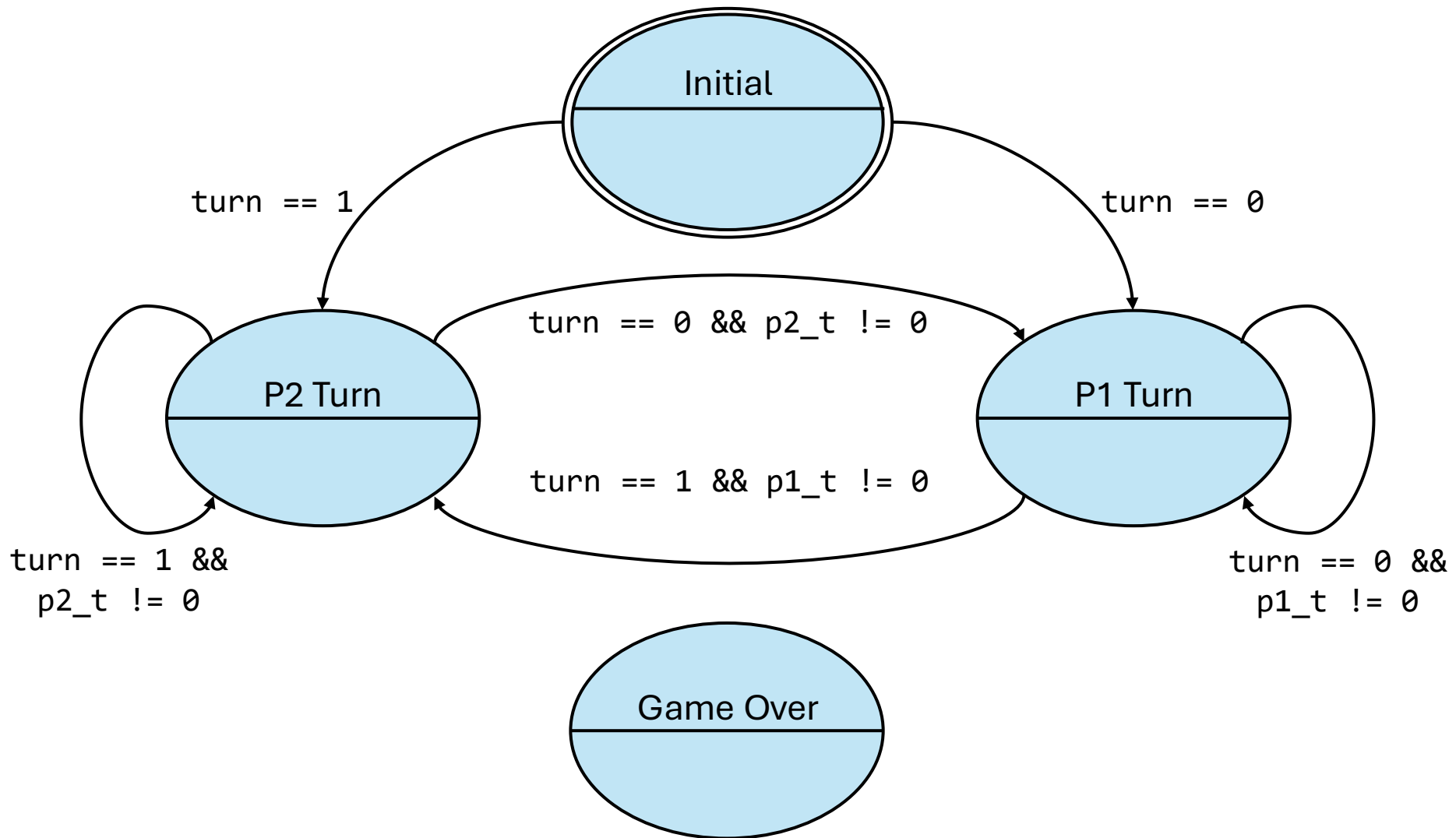


Example: Chess Clock (FSM Design)

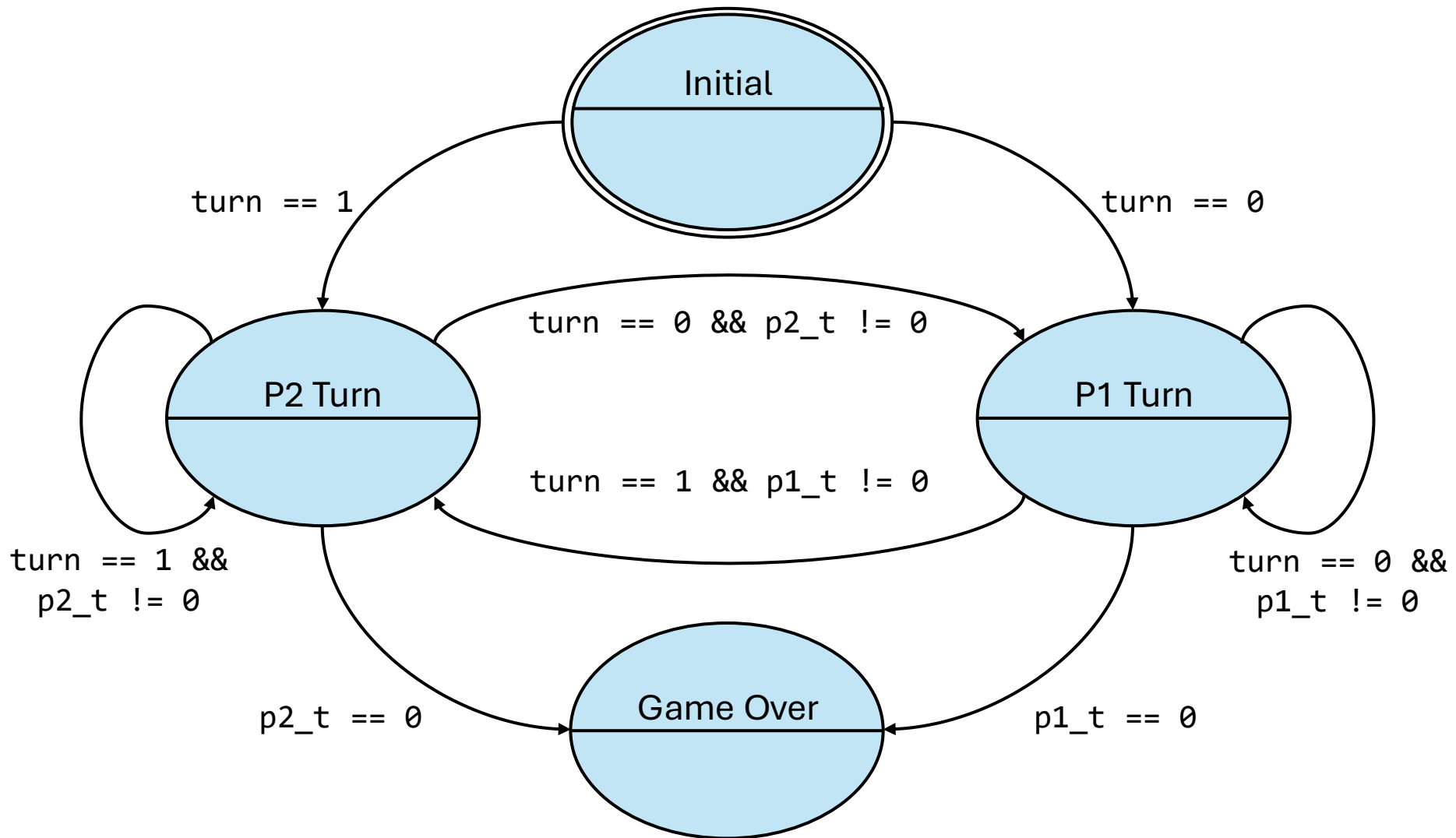


Example: Chess Clock (FSM Design)

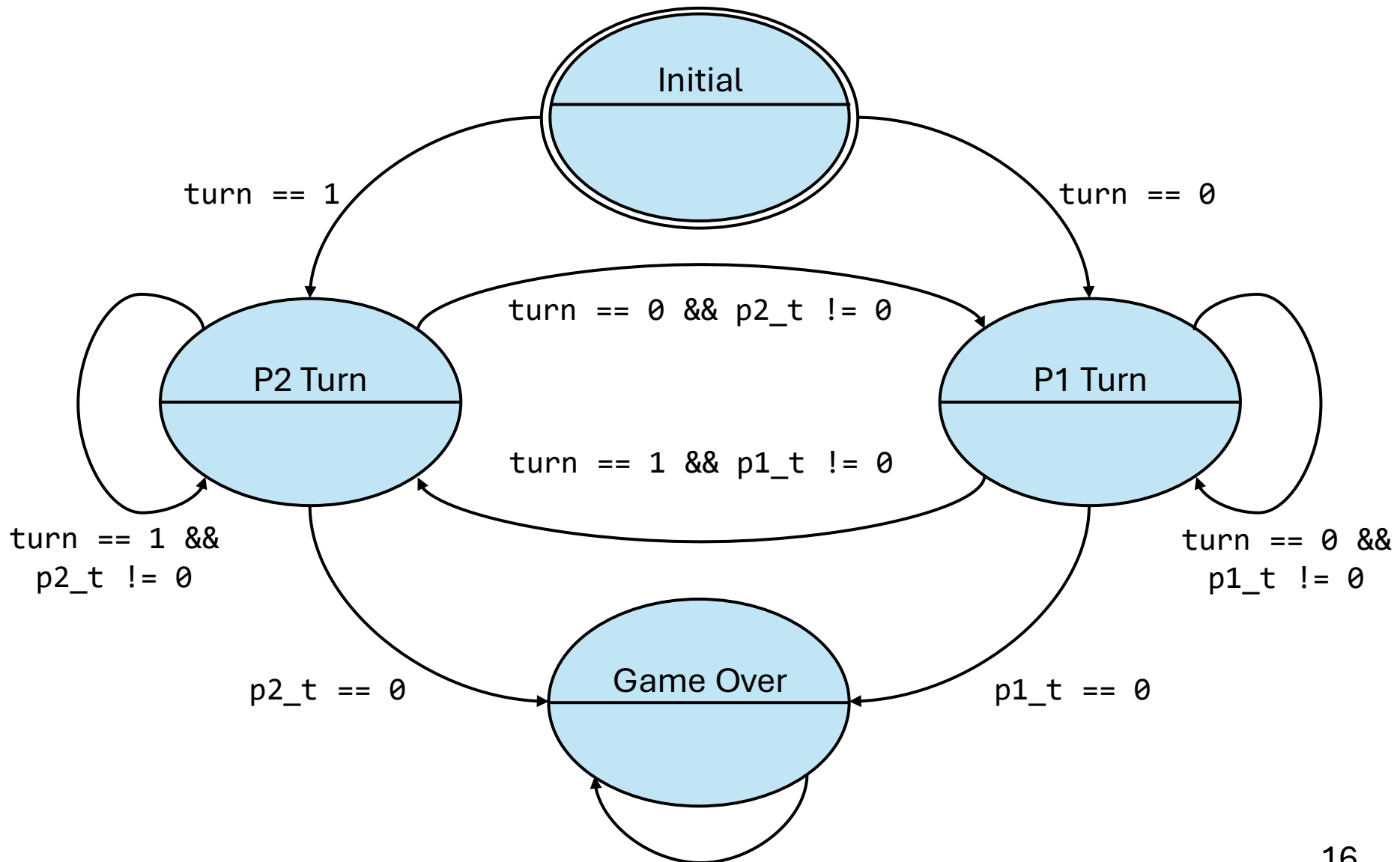


Example: Chess Clock (FSM Design)

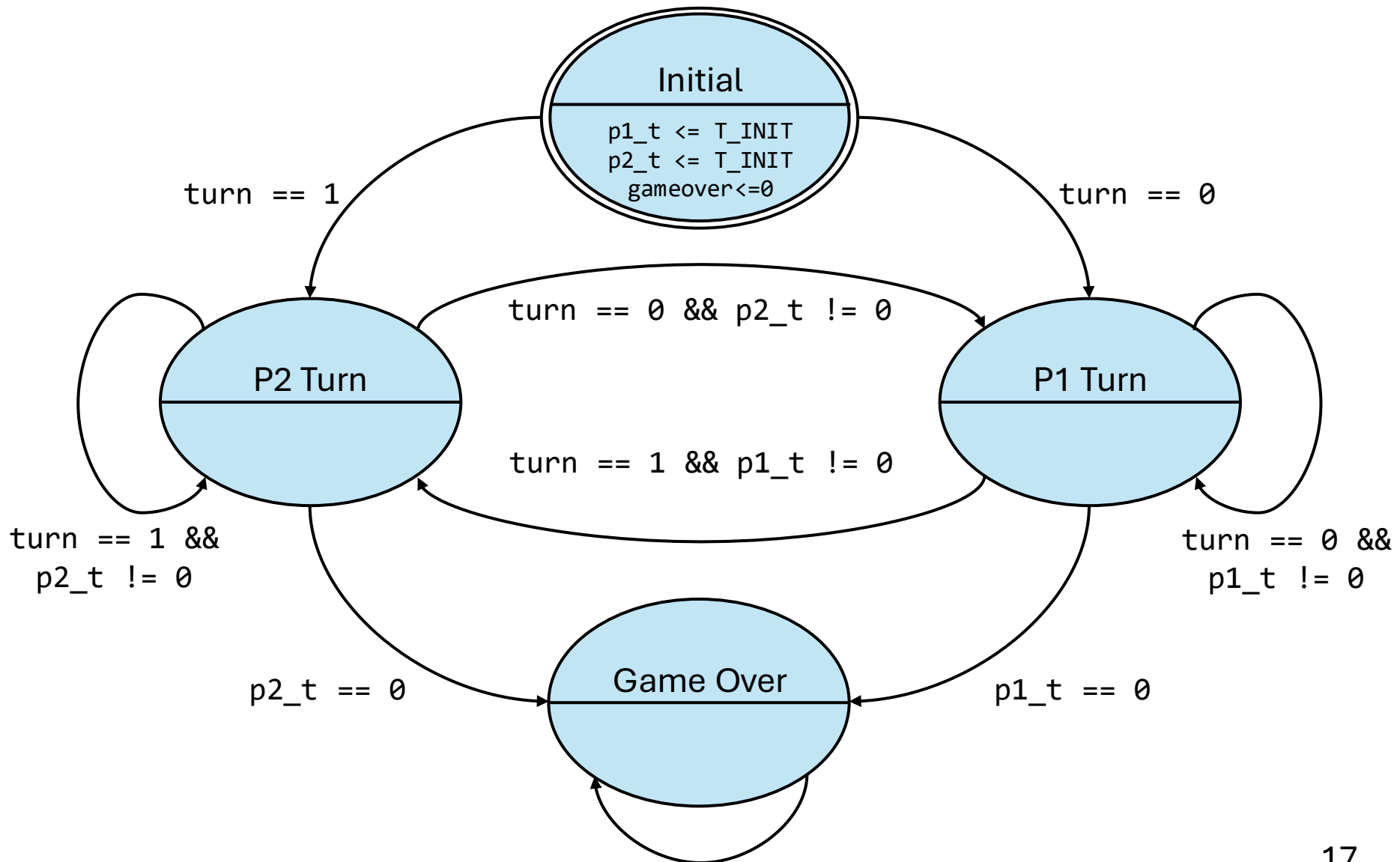


Example: Chess Clock (FSM Design)

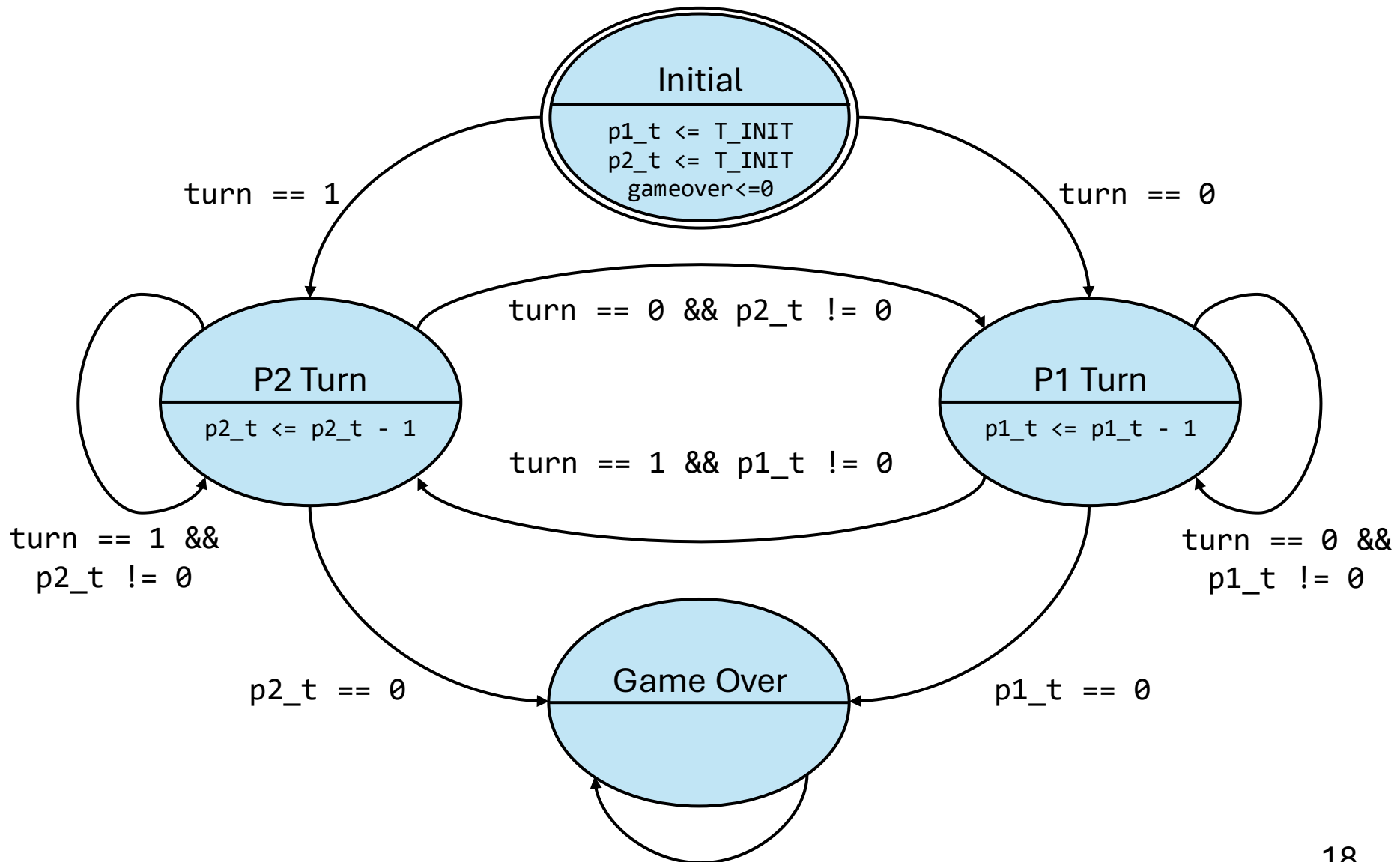

Example: Chess Clock (FSM Design)

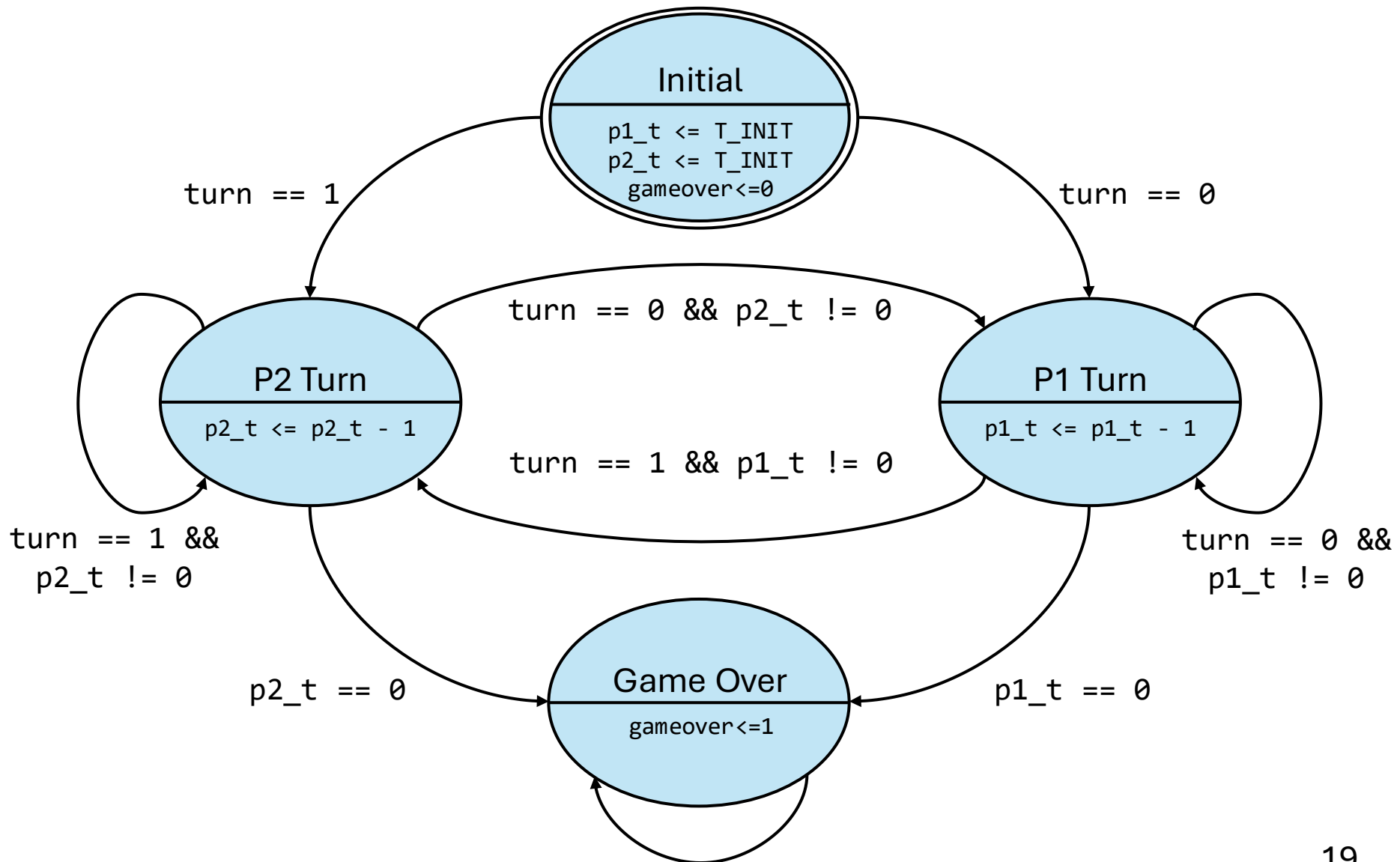

Example: Chess Clock (FSM Design)


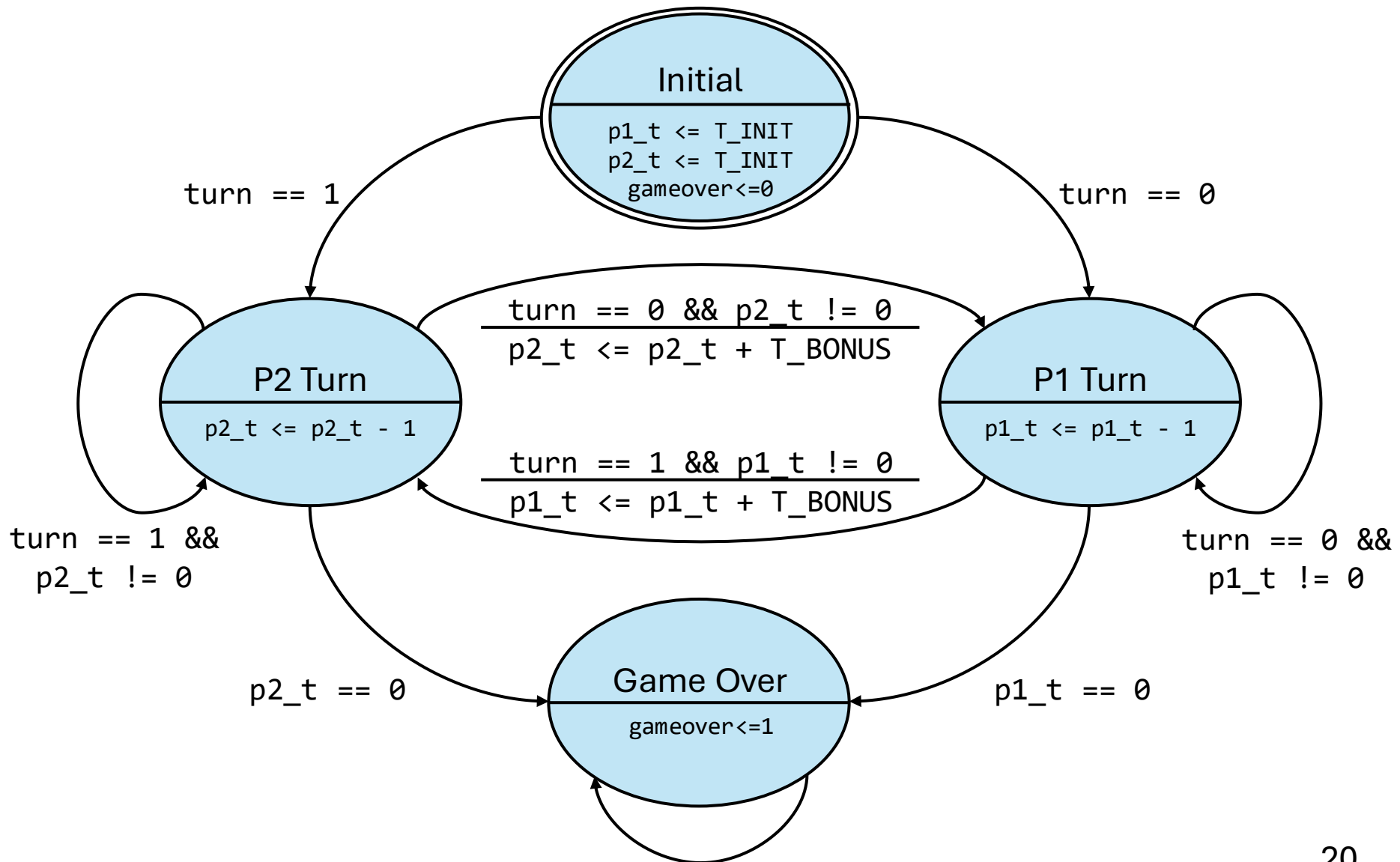


Example: Chess Clock (Code)

```

module chess_clock #(
    parameter T_INIT = 600,
    parameter T_BONUS = 10
)(
    input  clk,
    input  rst,
    input  turn,
    output logic [15:0] p1_t,
    output logic [15:0] p2_t,
    output logic gameover
);

```

 
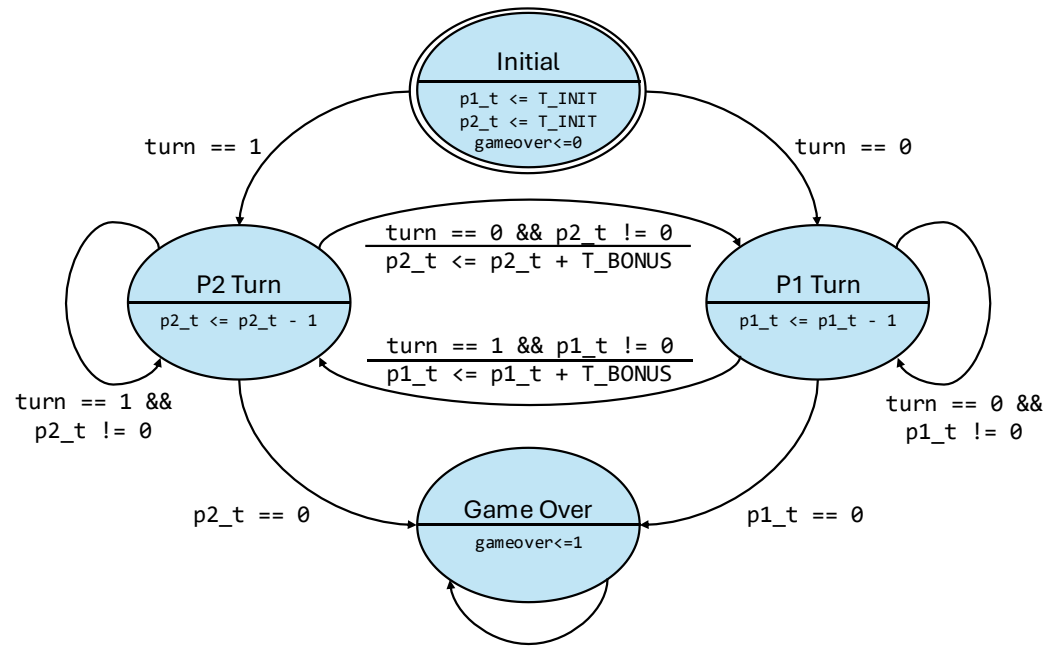


Example: Chess Clock (Code)

```

module chess_clock #(
    parameter T_INIT = 600,
    parameter T_BONUS = 10
)(
    input  clk,
    input  rst,
    input  turn,
    output logic [15:0] p1_t,
    output logic [15:0] p2_t,
    output logic gameover
);

  enum {INIT,P1,P2,GOVER} state, next_state;
logic [15:0] p1_t_val, p2_t_val;
logic gameover_val;
    
```





Example: Chess Clock (Code)

```

module chess_clock #(
    parameter T_INIT = 600,
    parameter T_BONUS = 10
)()
    input  clk,
    input  rst,
    input  turn,
    output logic [15:0] p1_t,
    output logic [15:0] p2_t,
    output logic gameover
);

enum {INIT,P1,P2,GOVER} state, next_state;
logic [15:0] p1_t_val, p2_t_val;
logic gameover_val;

 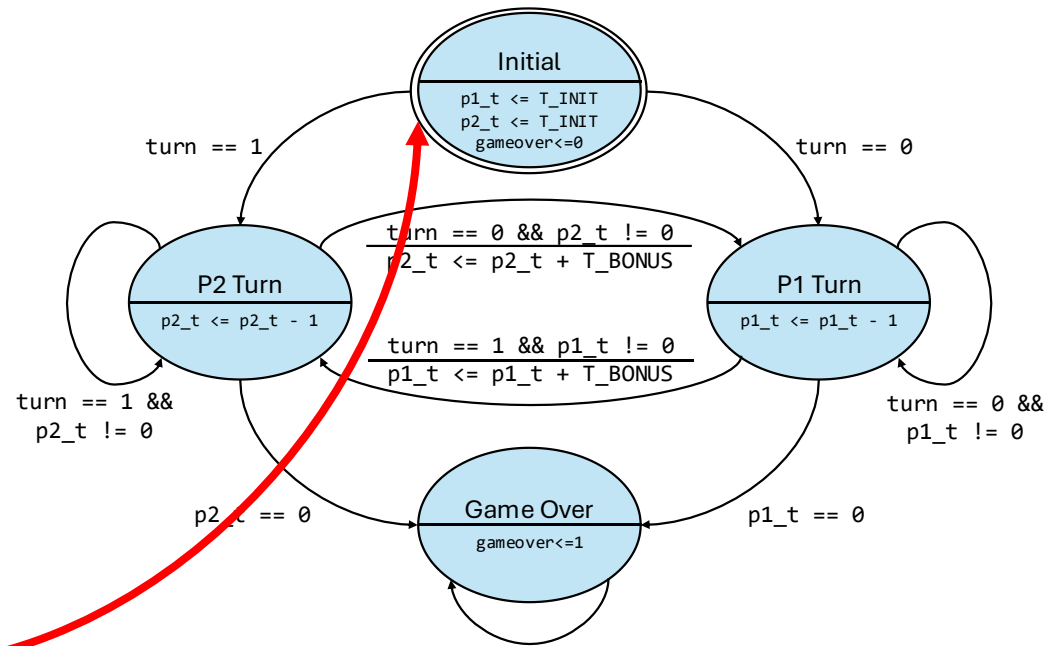always_ff @ (posedge clk) begin
    if (rst) begin
        p1_t <= T_INIT; p2_t <= T_INIT;
        gameover <= 1'b0;
        state <= INIT;
    end else begin
        p1_t <= p1_t_val; p2_t <= p2_t_val;
        gameover <= gameover_val;
        state <= next_state;
    end
end
    
```



Example: Chess Clock (Code)

```

always_comb begin: state_decoder
  case (state)
    INIT : next_state = (turn)? P2 : P1;


    P1: begin
      if (turn && p1_t!=0) next_state = P2;
      else if (p1_t==0) next_state = GOVER;
      else next_state = P1;
    end

    P2: begin
      if (~turn && p2_t!=0) next_state = P1;
      else if (p2_t==0) next_state = GOVER;
      else next_state = P2;
    end

    GOVER: next_state = GOVER;

    default: next_state = INIT;
  endcase
end

```

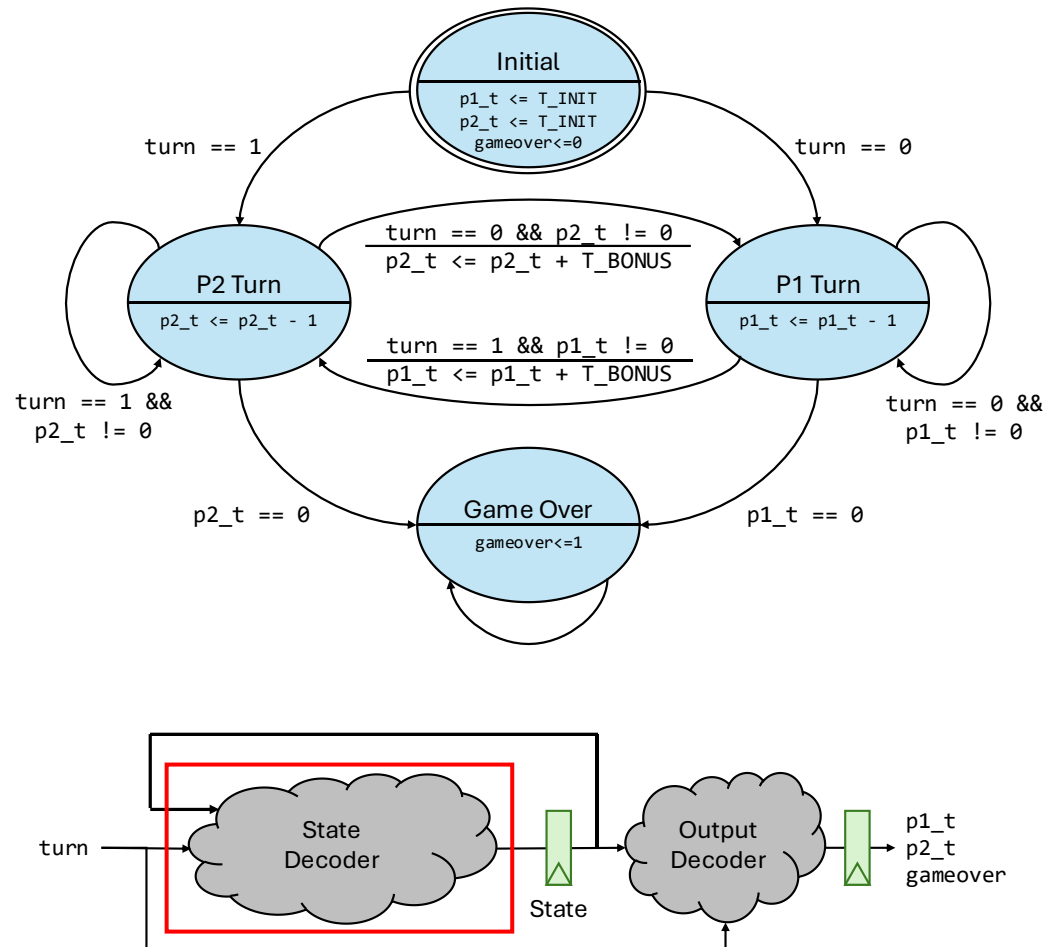

Example: Chess Clock (Code)

```

always_comb begin: out_decoder
  case (state)
    INIT: begin
      p1_t_val = T_INIT; p2_t_val = T_INIT;
      gameover_val = 1'b0;
    end

    P1: begin
      if (turn && p1_t!=0)
        p1_t_val = p1_t + T_BONUS;
      else p1_t_val = p1_t - 1;
    end



    P2: begin
      if (~turn && p2_t!=0)
        p2_t_val = p2_t + T_BONUS;
      else p2_t_val = p2_t - 1;
    end

    GOVER: gameover_val = 1'b1;

  default: begin
    p1_t_val = T_INIT; p2_t_val = T_INIT;
    gameover_val = 1'b0;
  end
endcase
end

endmodule

```

  

Example: Chess Clock (Code)

```

always_comb begin: out_decoder
  case (state)
    INIT: begin
      p1_t_val = T_INIT; p2_t_val = T_INIT;
      gameover_val = 1'b0;
    end

    P1: begin
      if (turn && p1_t!=0)
        p1_t_val = p1_t + T_BONUS;
      else p1_t_val = p1_t - 1;
    end



    P2: begin
      if (~turn && p2_t!=0)
        p2_t_val = p2_t + T_BONUS;
      else p2_t_val = p2_t - 1;
    end

    GOVER: gameover_val = 1'b1;

    default: begin
      p1_t_val = T_INIT; p2_t_val = T_INIT;
      gameover_val = 1'b0;
    end
  endcase
end

endmodule

```

  

Think how to extend to 4 players ...

Example: Music Toy

- Toy gives a sequence of N music tones & waits for user to enter the same sequence correctly
- If correct tones are entered, advance to next level & give a sequence of $N+1$ tones
- If incorrect tones are entered, stay in the same level & give the same sequence of N tones again
- Assume the toy has a total of 3 levels (for simplicity) & the full sequence is hardcoded



My kid's music toy ☺

Example game:

Toy: Re (level 1) → User: Re

Toy: Re, Do (level 2) → User: Fa

Toy: Re, Do (level 2) → User: Re, Do

Toy: Re, Do, Mi (level 3) → User: Re, Do, Mi

Example: Music Toy - Two Interacting FSMs




Prompt FSM

Response FSM


Example: Music Toy - Two Interacting FSMs

 *(1) Based on current level,
generate a sequence of
output tones then raise
flag to indicate waiting for
user response*



Example: Music Toy - Two Interacting FSMs

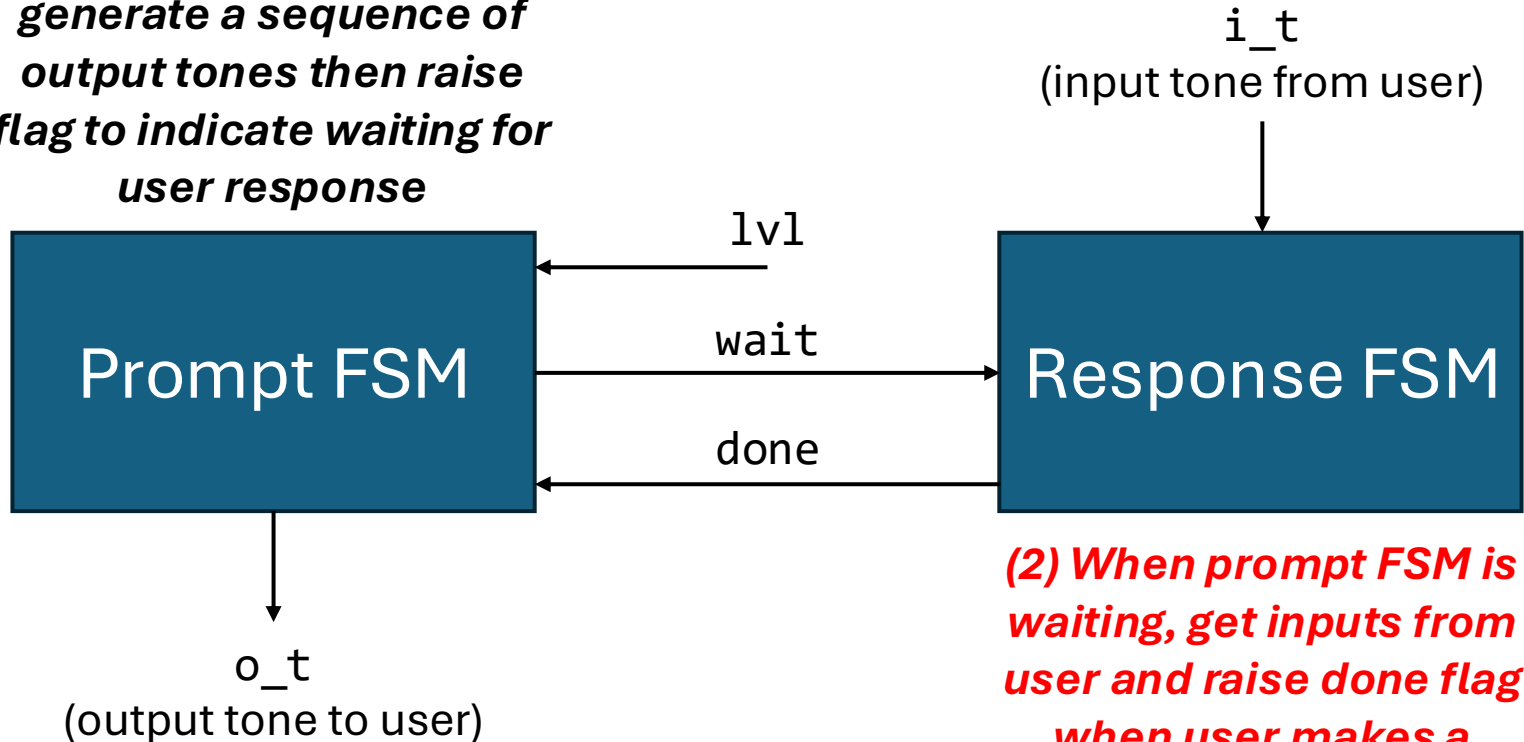
(1) Based on current level, generate a sequence of output tones then raise flag to indicate waiting for user response



(2) When prompt FSM is waiting, get inputs from user and raise done flag when user makes a mistake or enters full sequence correctly

Example: Music Toy - Two Interacting FSMs

 (1) Based on current level, generate a sequence of output tones then raise flag to indicate waiting for user response



o_t
(output tone to user)

(3) Update level accordingly


i_t
(input tone from user)

(2) When prompt FSM is waiting, get inputs from user and raise done flag when user makes a mistake or enters full sequence correctly



Example: Music Toy - Two Interacting FSMs

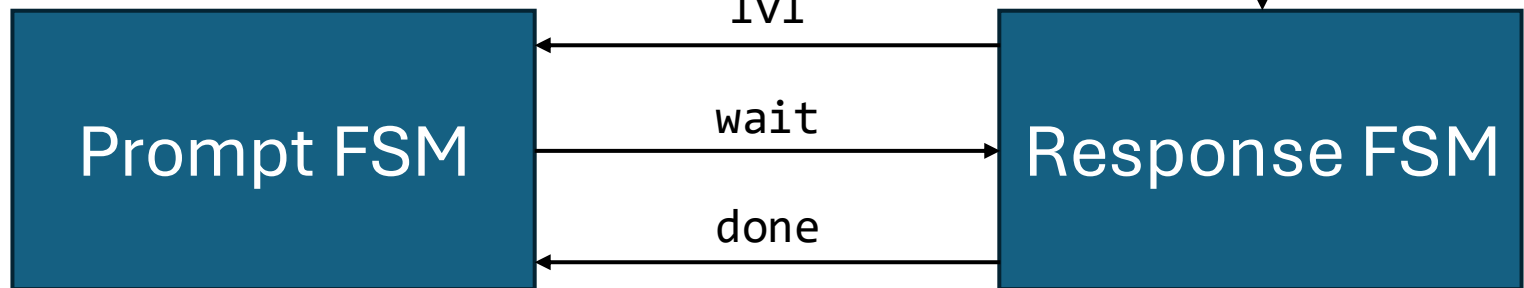
(1) Based on current level, generate a sequence of output tones then raise flag to indicate waiting for user response



(2) When prompt FSM is waiting, get inputs from user and raise done when user makes a mistake or enters full sequence correctly


(4) When response FSM declares done, de-assert wait flag and output tone sequence based on level then raise wait flag ...

Example: Music Toy (Prompt FSM Design)

 


 Example: Music Toy (Prompt FSM Design)

*When reset is de-asserted,
move to state Re and
output the first tone*




Example: Music Toy (Prompt FSM Design)

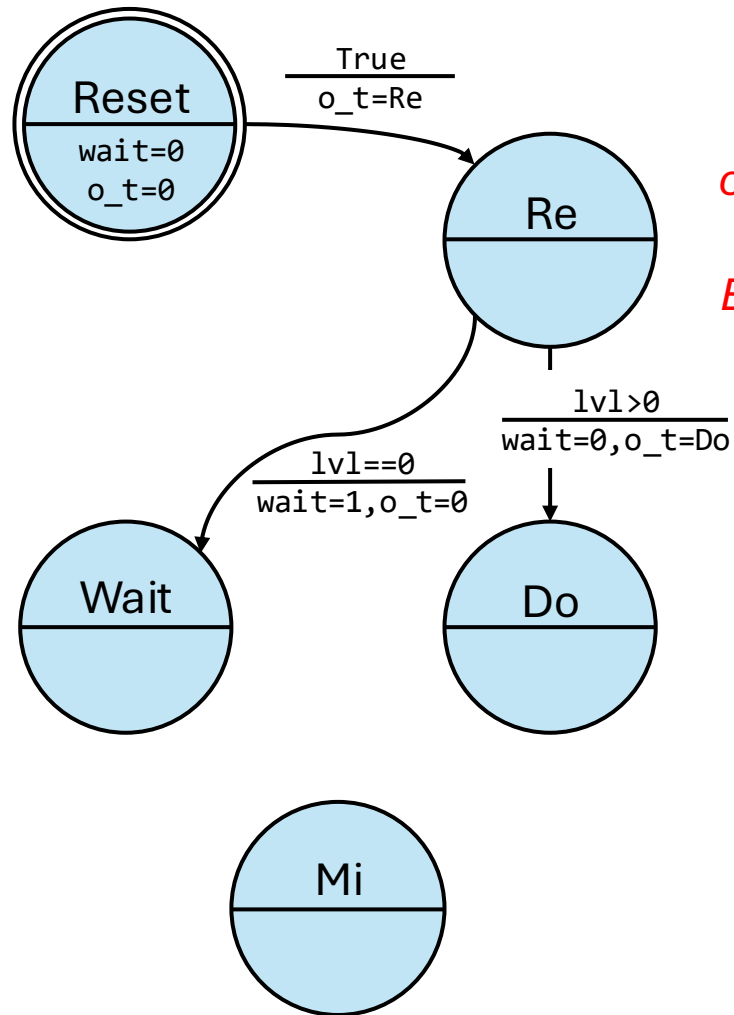


*If this is the first level,
output sequence is done
→ move to wait state
Else, continue sequence*

Example: Music Toy (Prompt FSM Design)

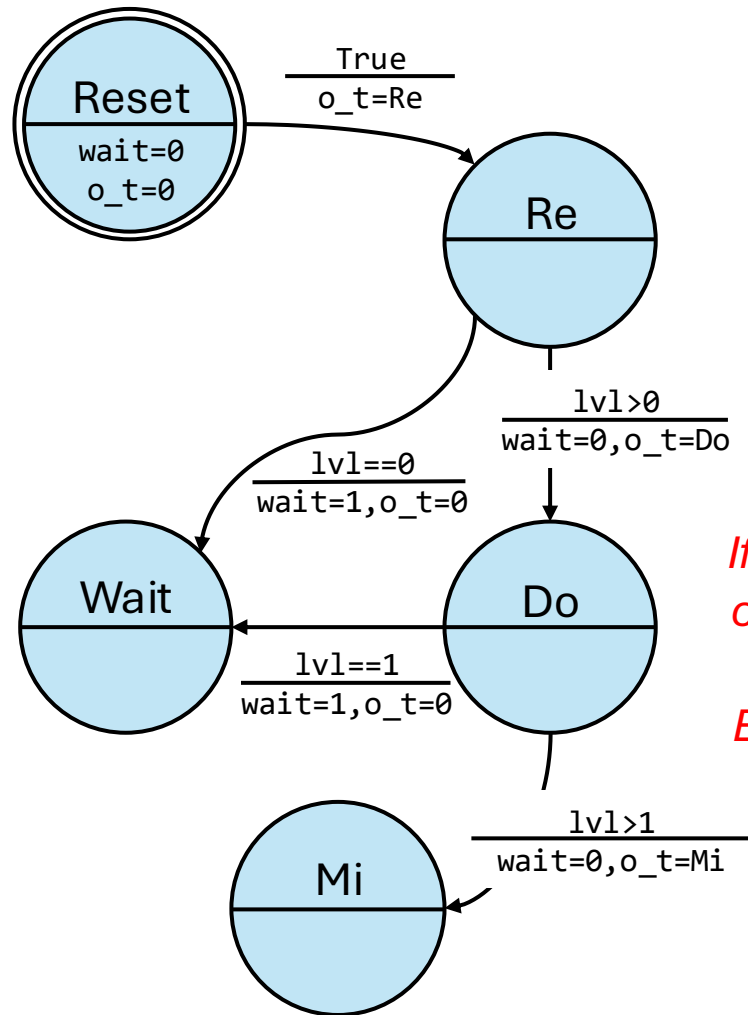


*If this is the second level,
output sequence is done
→ move to wait state
Else, continue sequence*

Example: Music Toy (Prompt FSM Design)

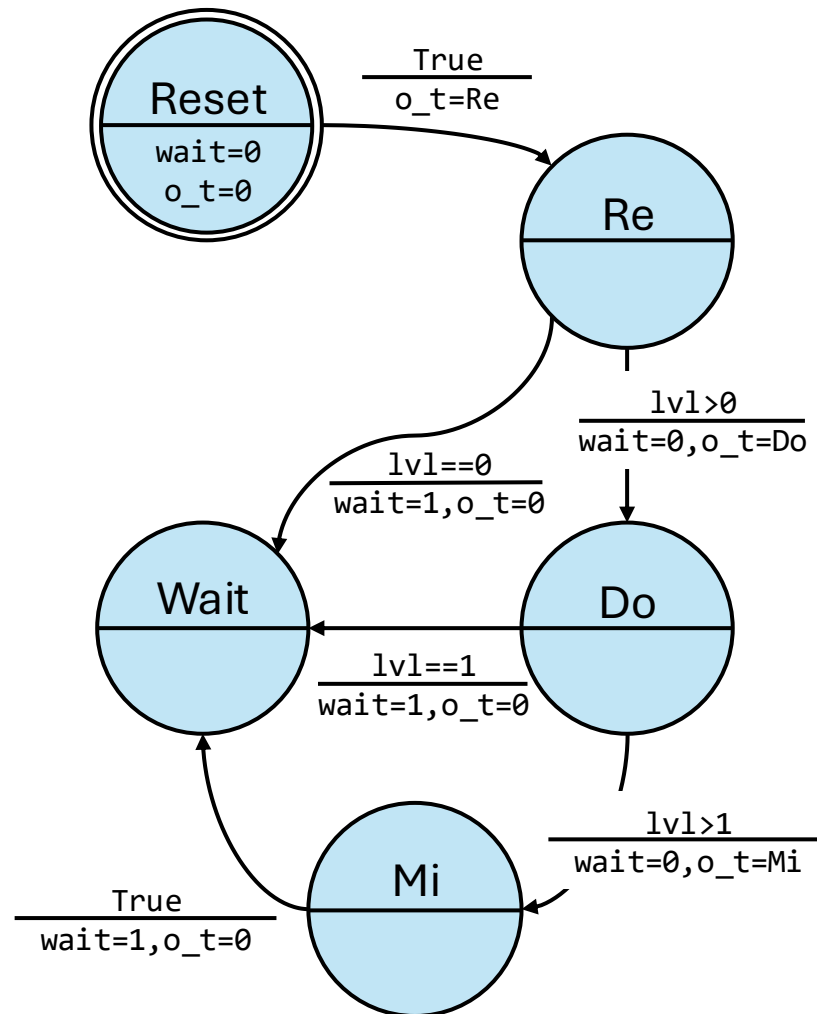

*If this is the third level,
output sequence is done
→ move to wait state*


Example: Music Toy (Prompt FSM Design)

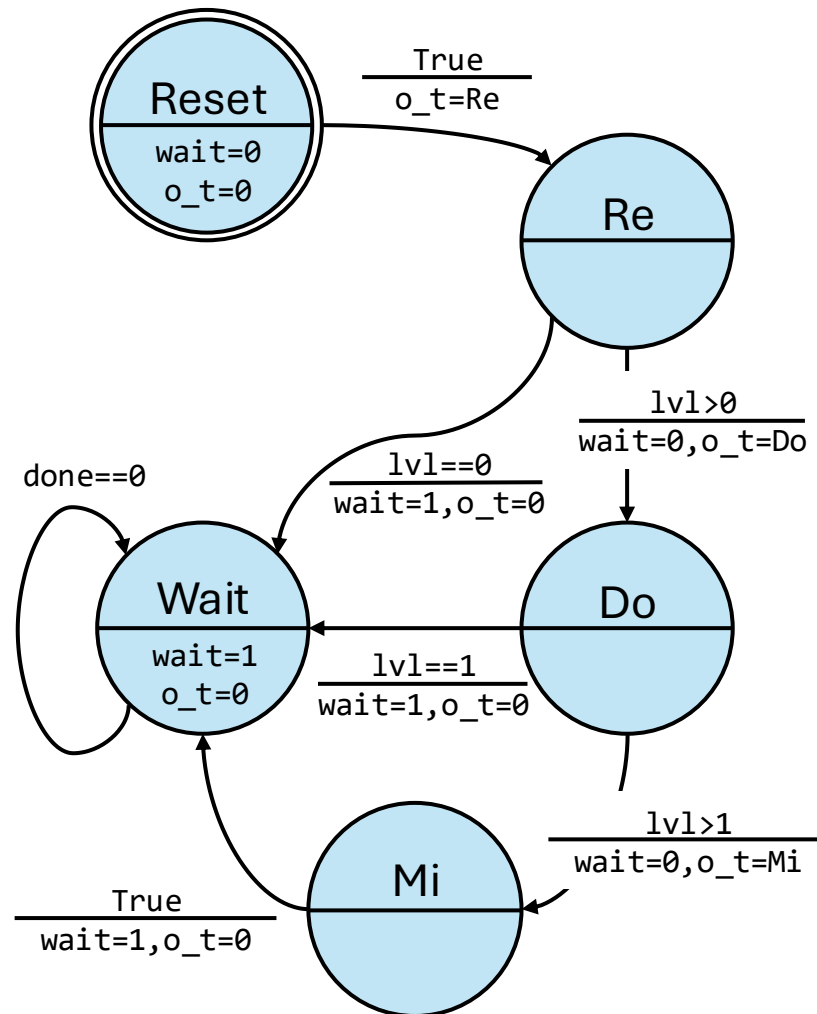






Stay in wait state as long as the response FSM did not indicate that user input is done (mistake or full correct sequence)

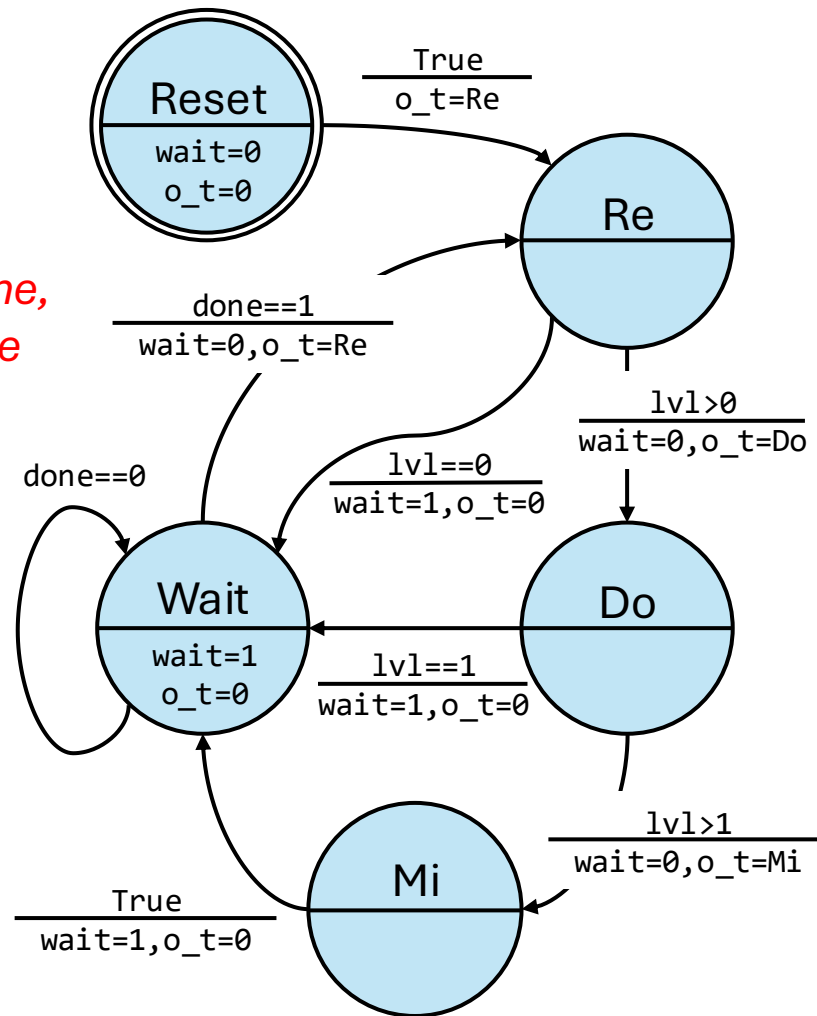Example: Music Toy (Prompt FSM Design)

*Once user input is done,
start a new sequence*




Example: Music Toy (Response FSM Design)

     


 Example: Music Toy (Response FSM Design)


*When reset is
de-asserted,
move to in1 state
when Prompt
FSM starts
waiting*




Example: Music Toy (Response FSM Design)

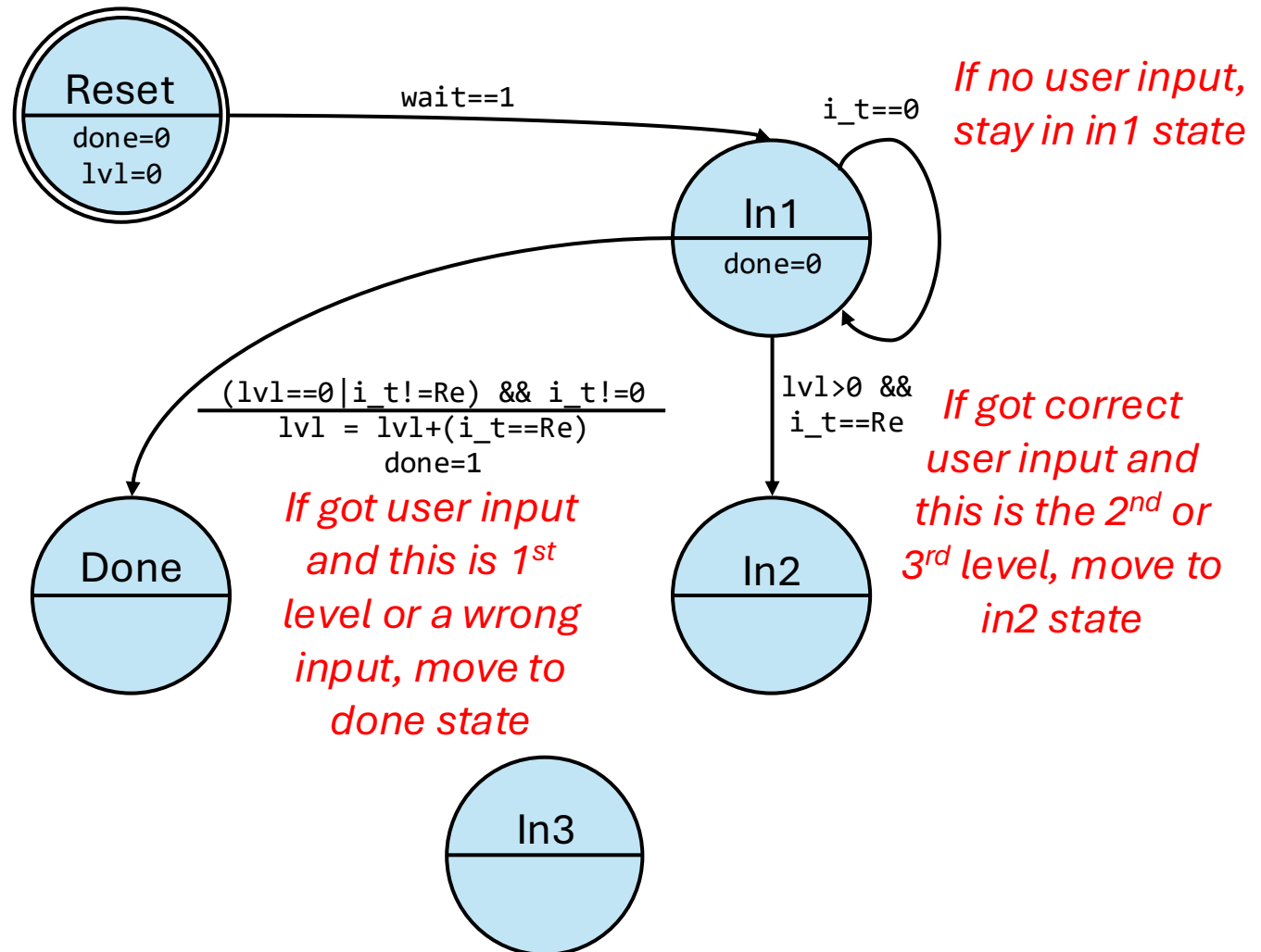


Example: Music Toy (Response FSM Design)

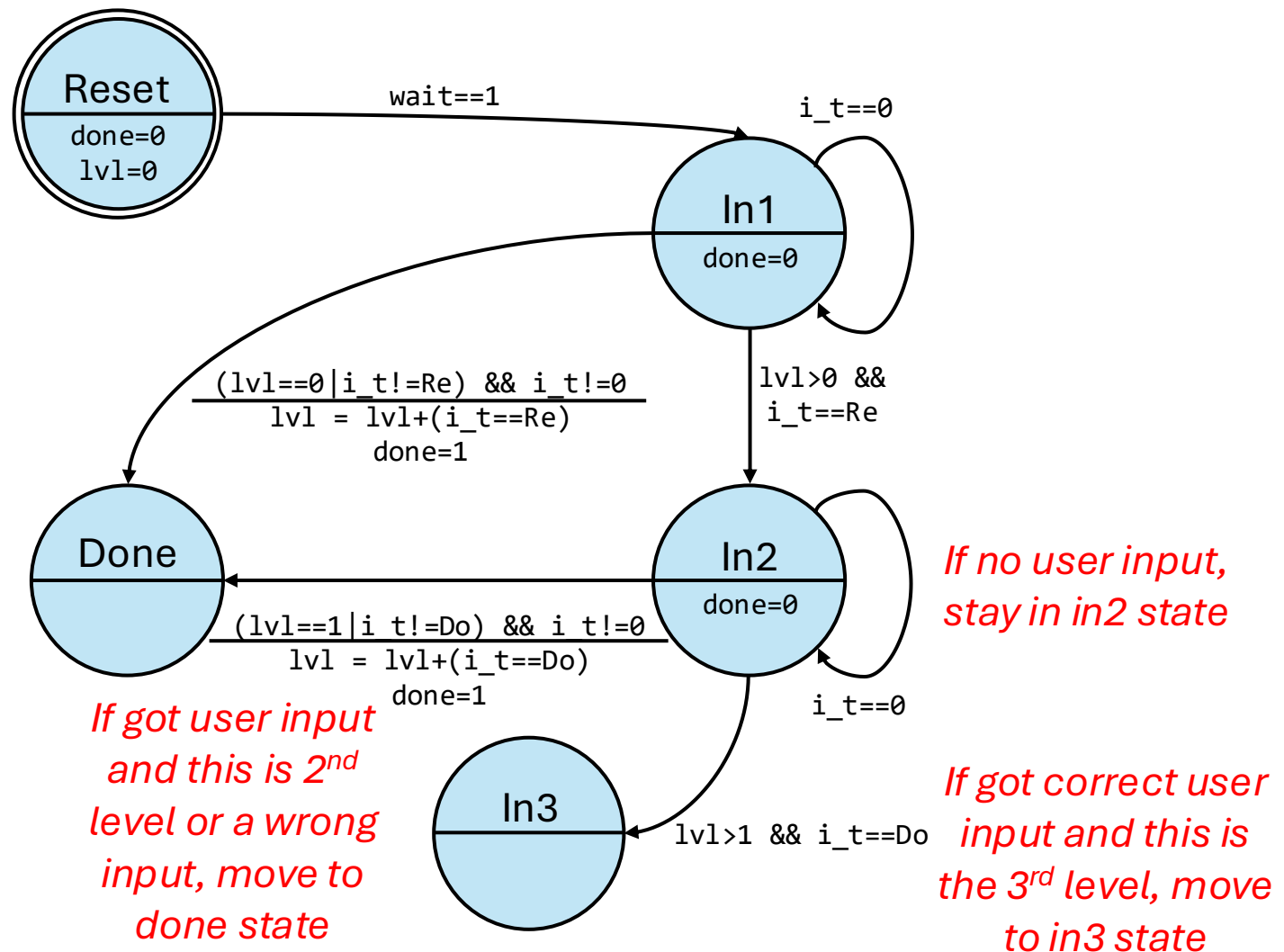

Example: Music Toy (Response FSM Design)

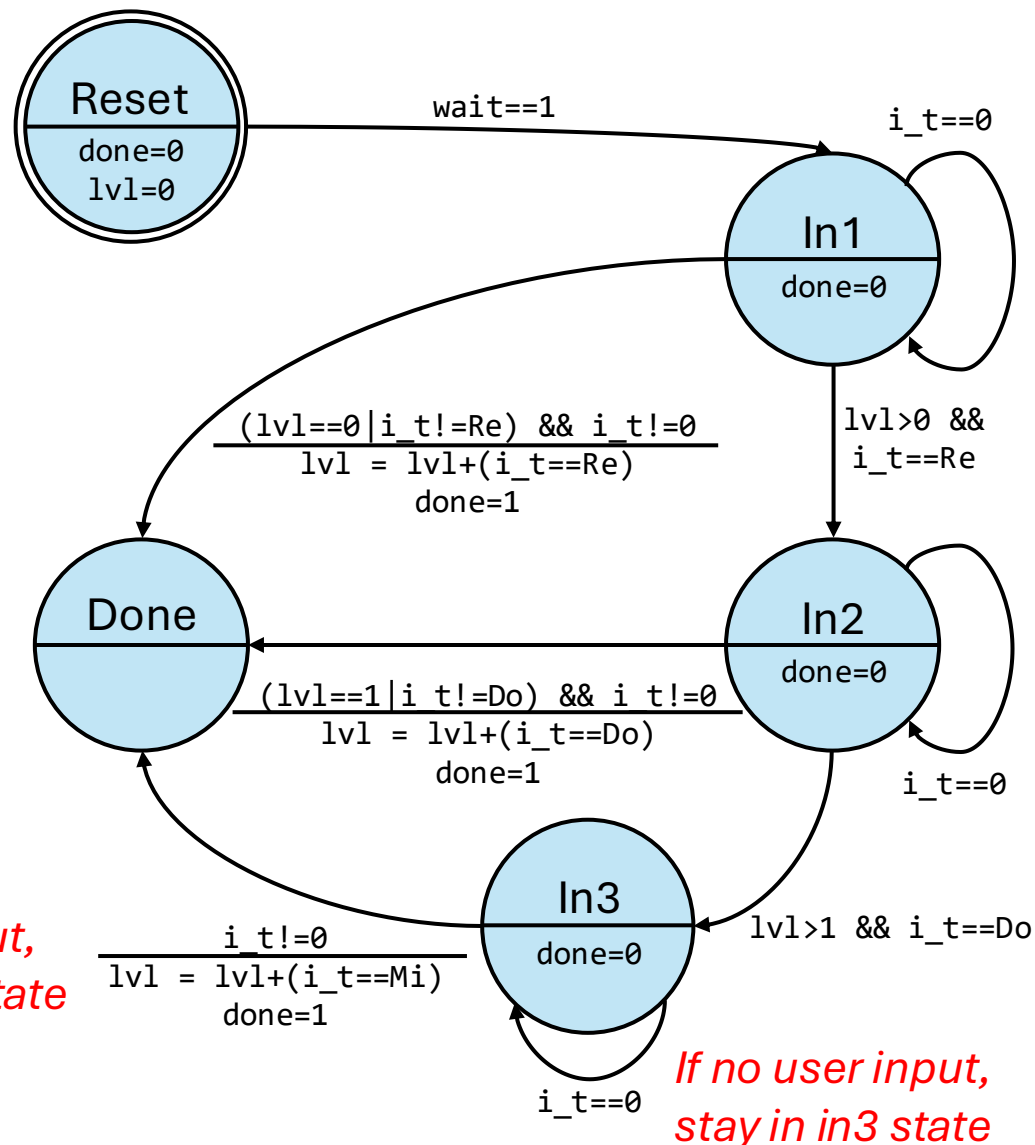


Example: Music Toy (Response FSM Design)

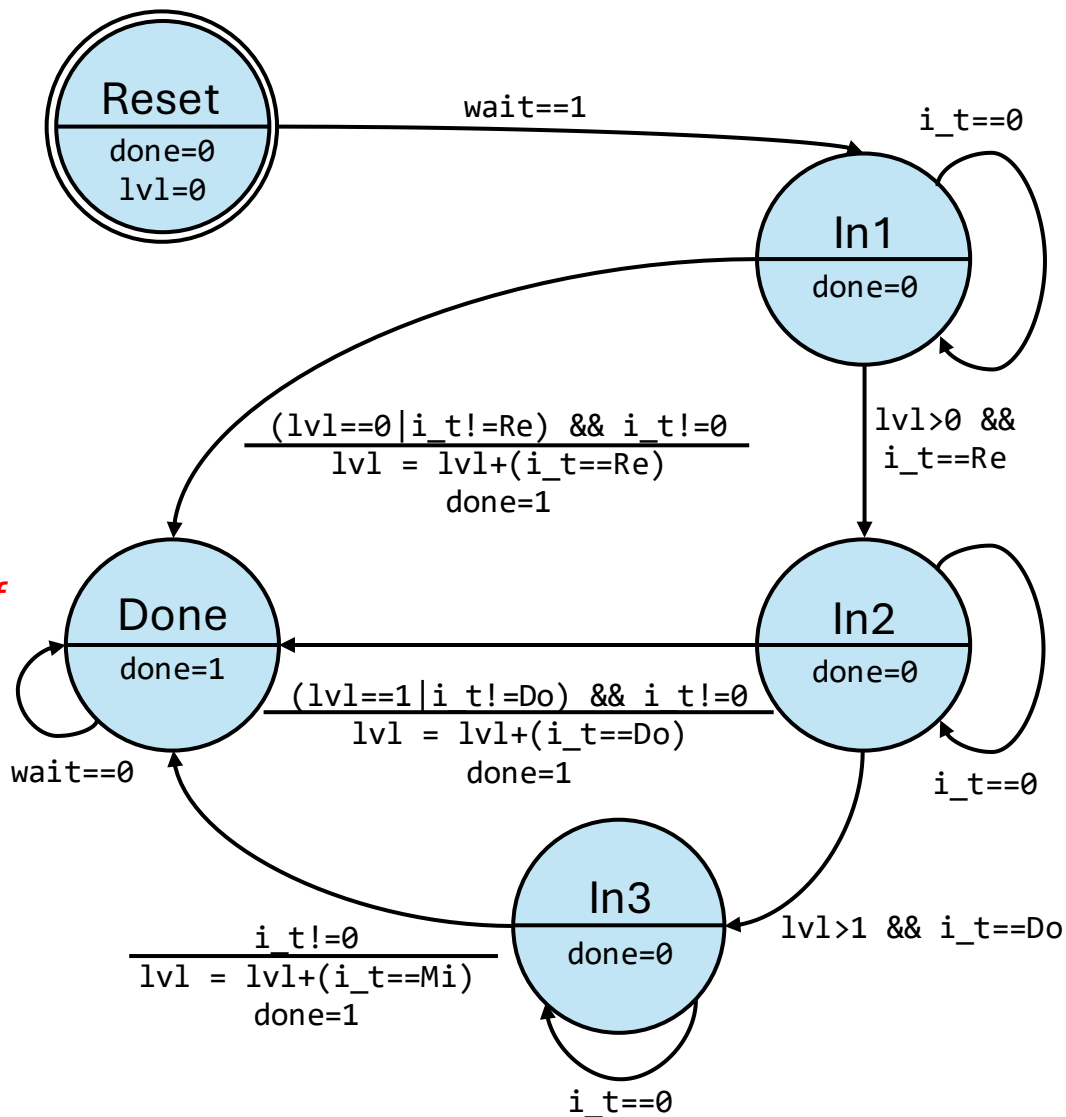



Stay in done state if
Prompt FSM is not
waiting for a user
input sequence

Example: Music Toy (Response FSM Design)

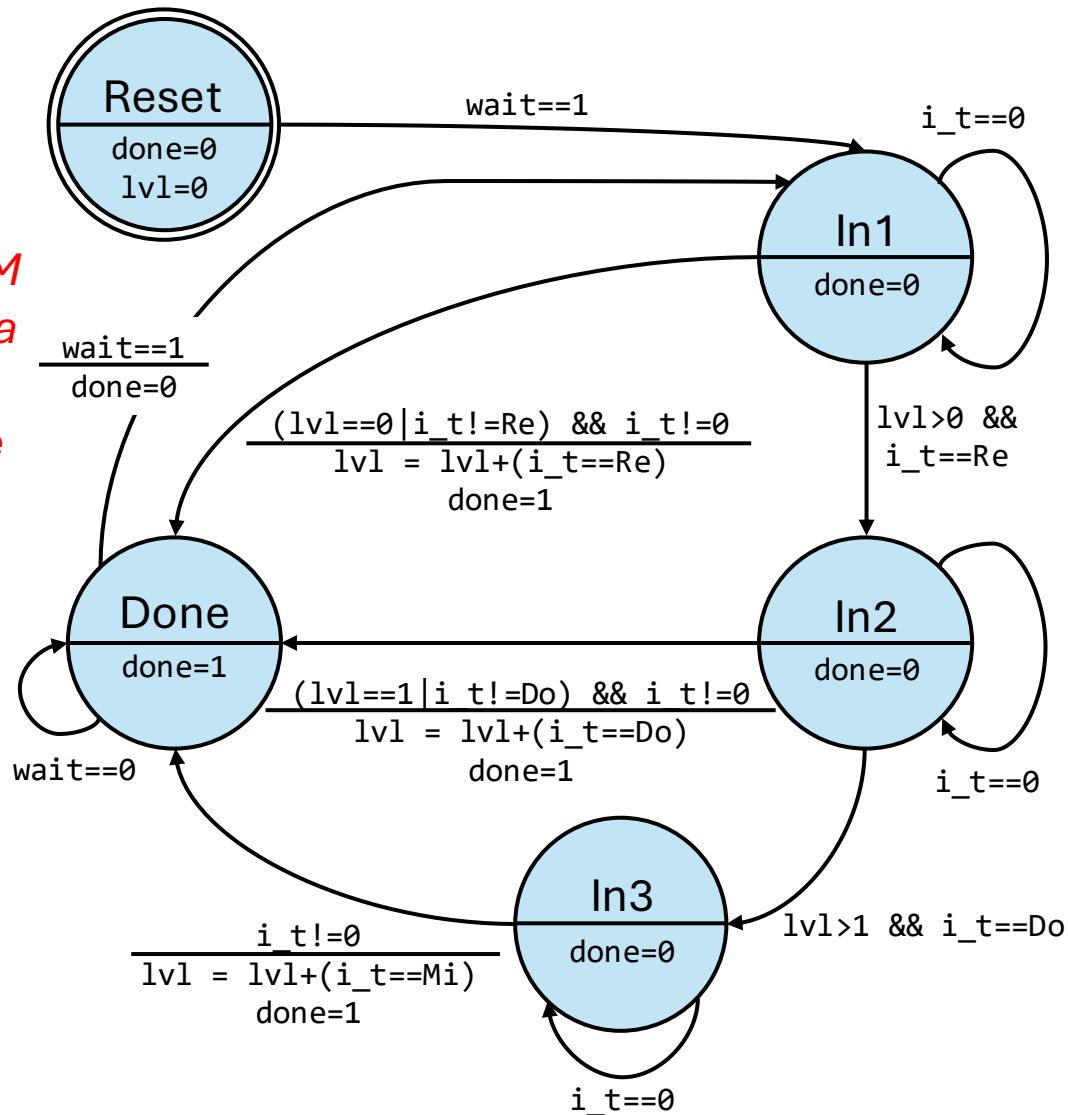


When Prompt FSM starts waiting for a user sequence, move to in1 state

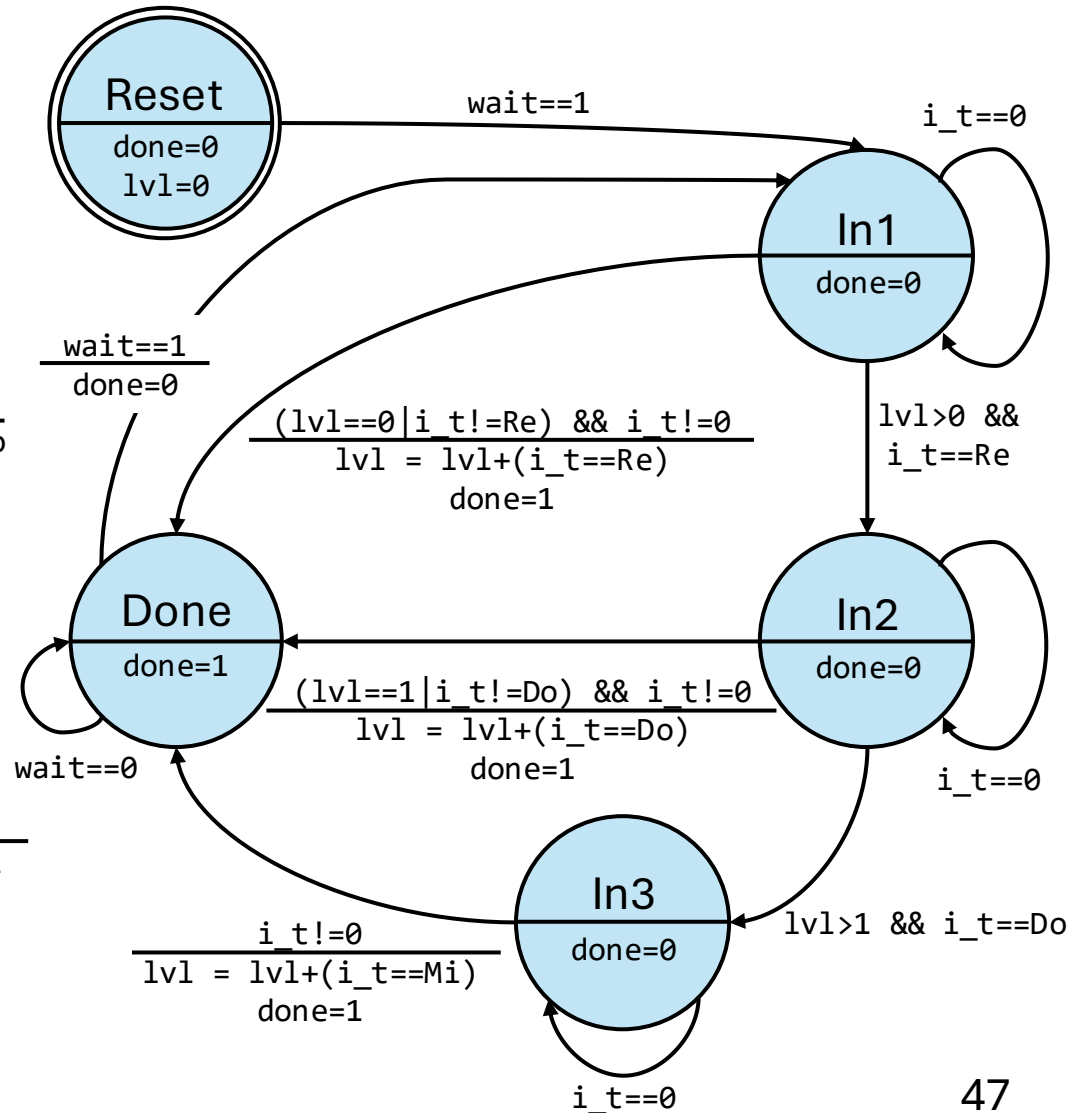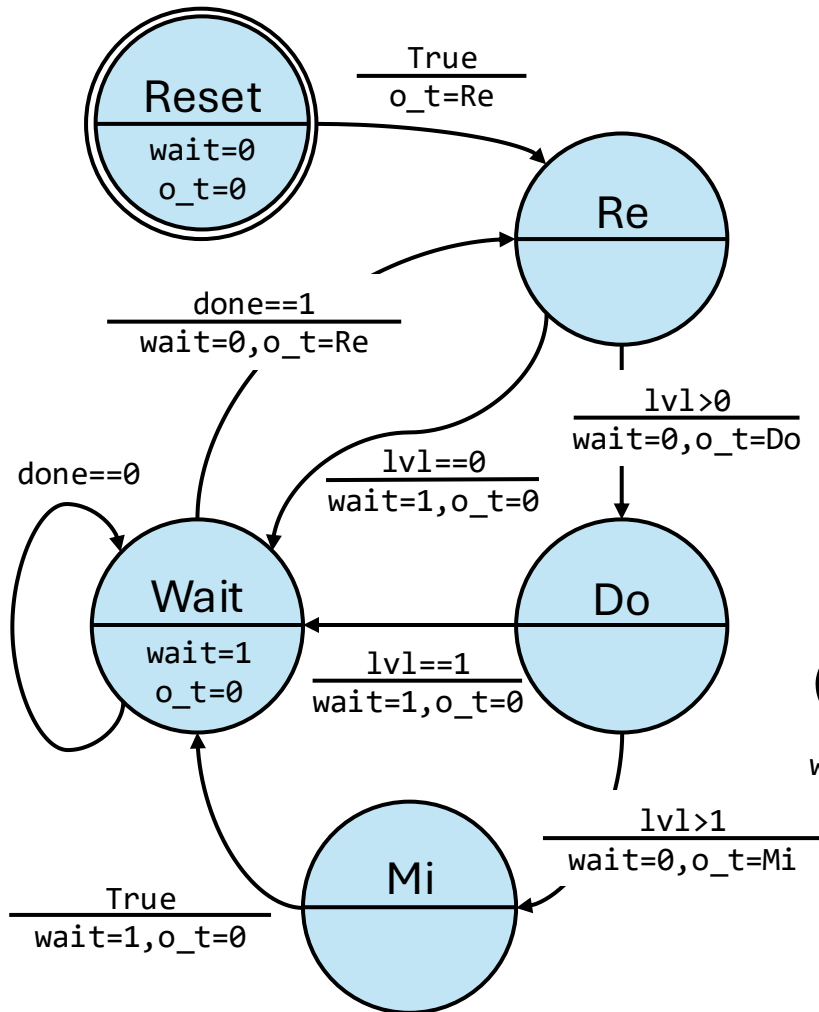
Example: Music Toy (Prompt + Response FSMs)



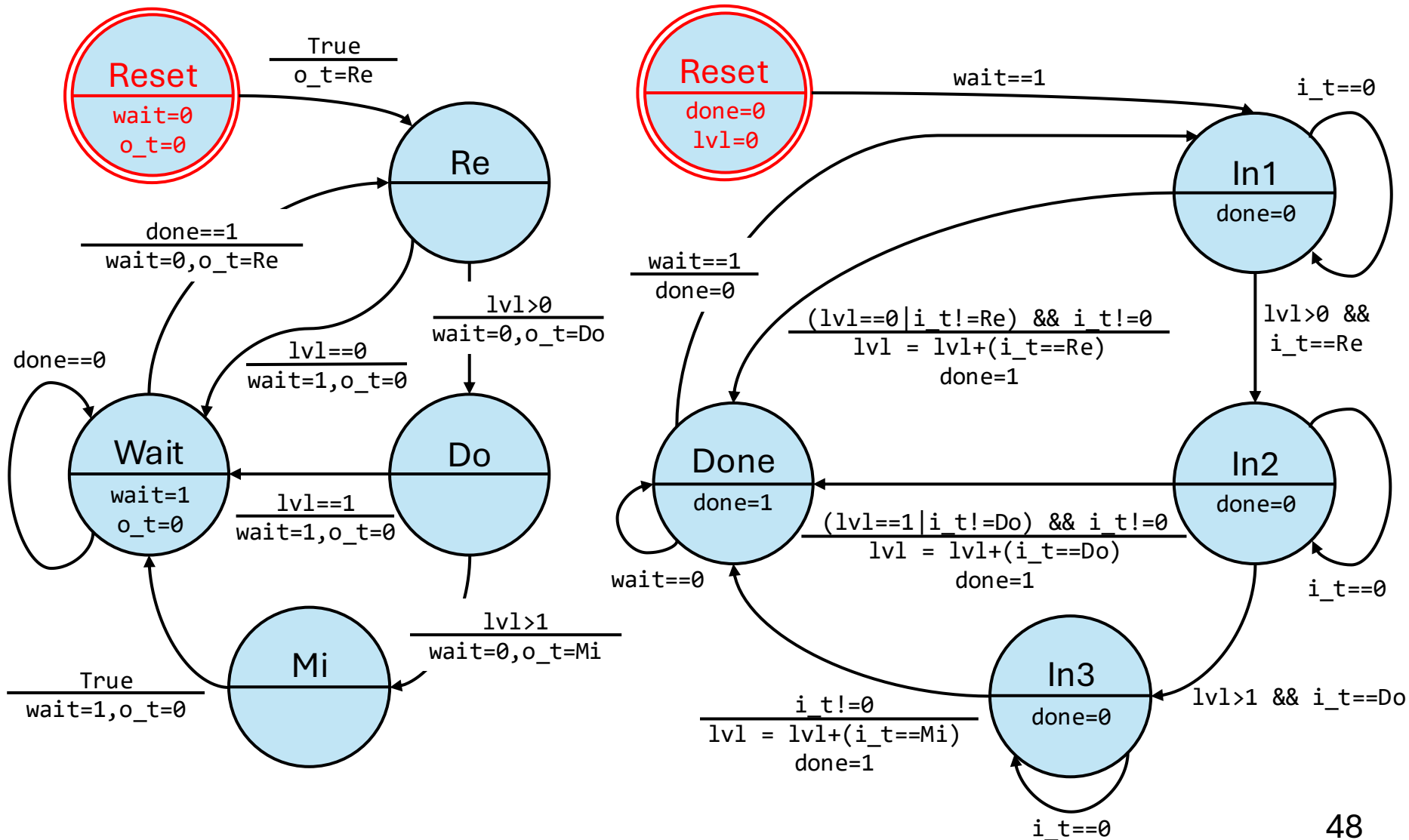
Example: Music Toy (Prompt + Response FSMs)



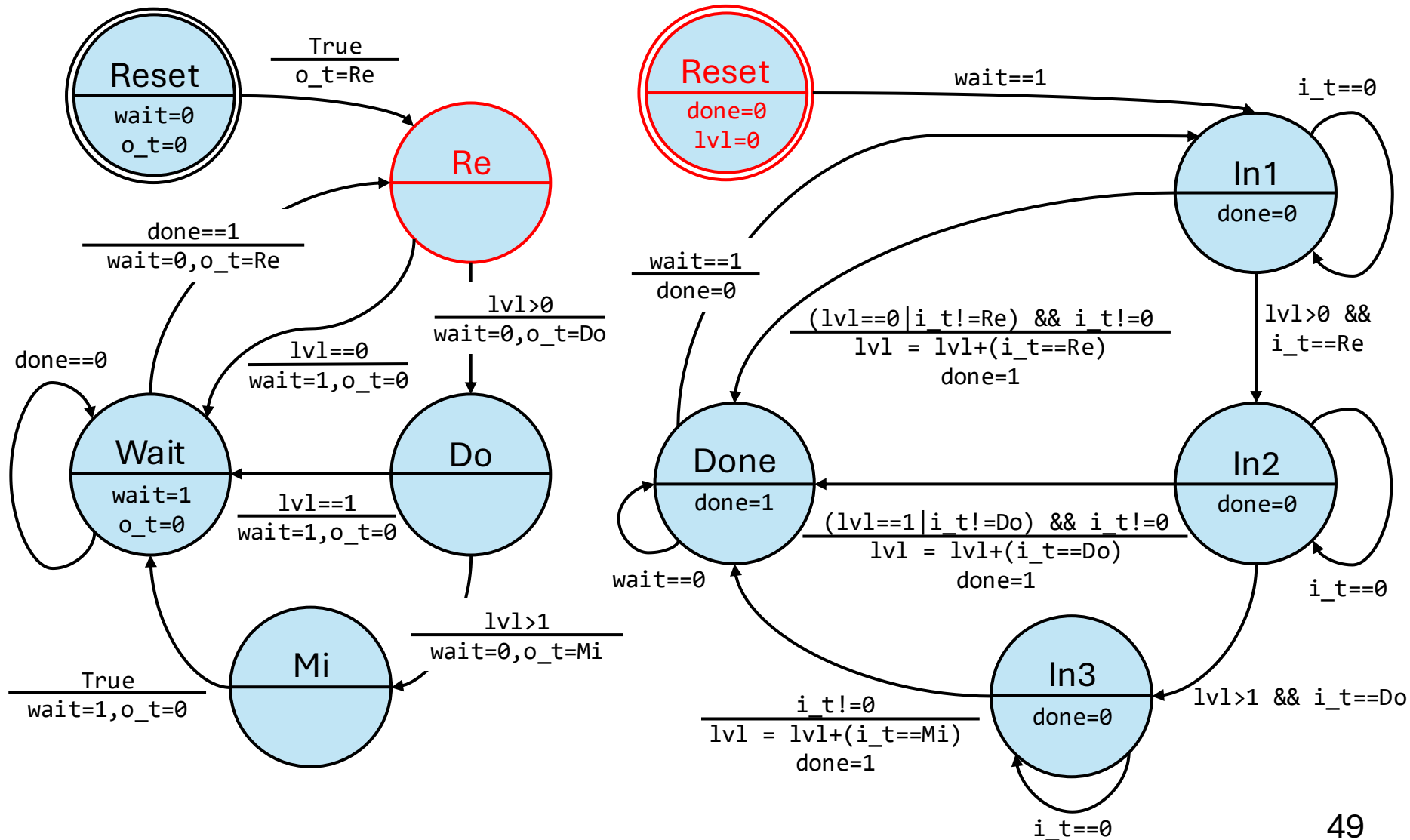
Example: Music Toy (Prompt + Response FSMs)



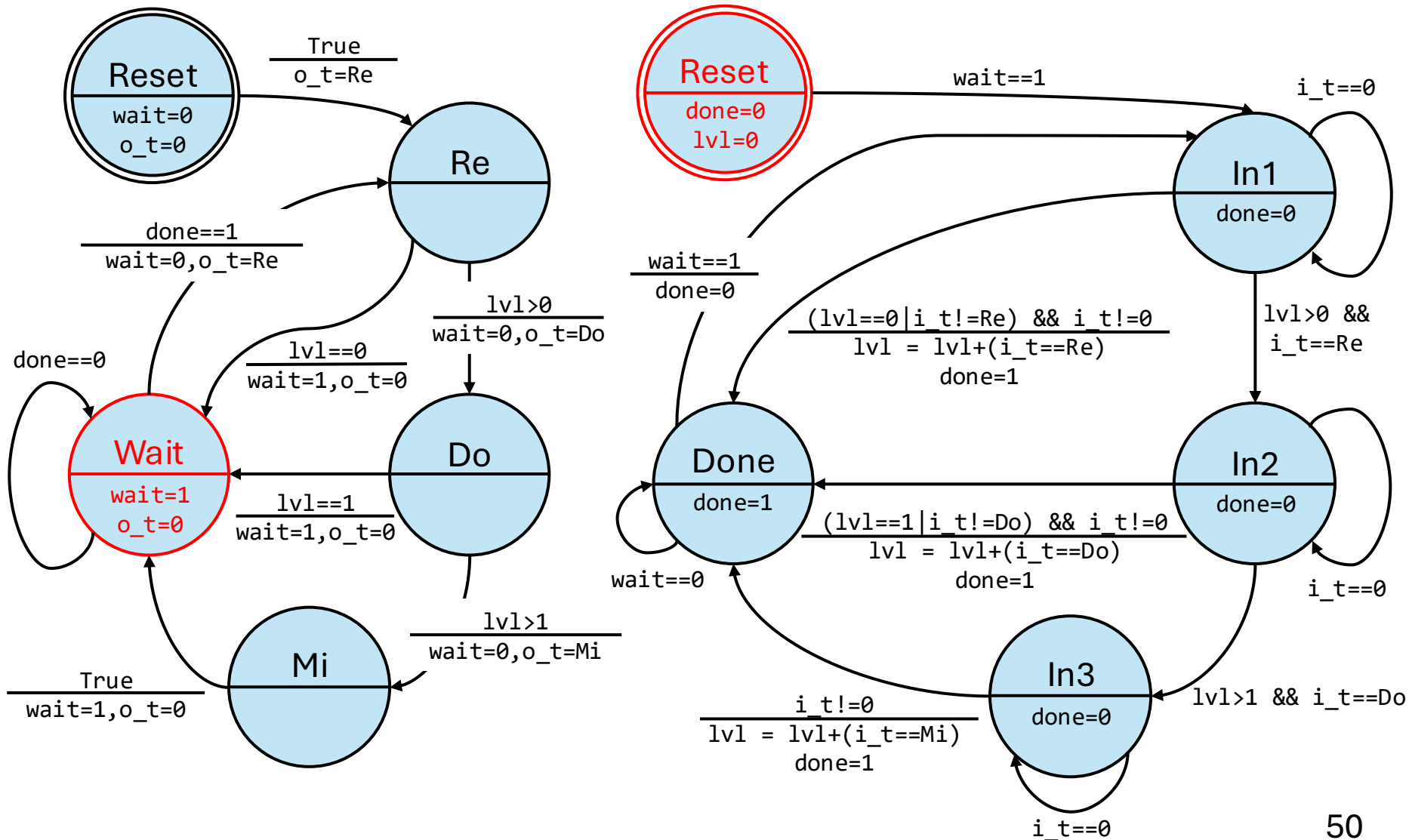
Example: Music Toy (Prompt + Response FSMs)



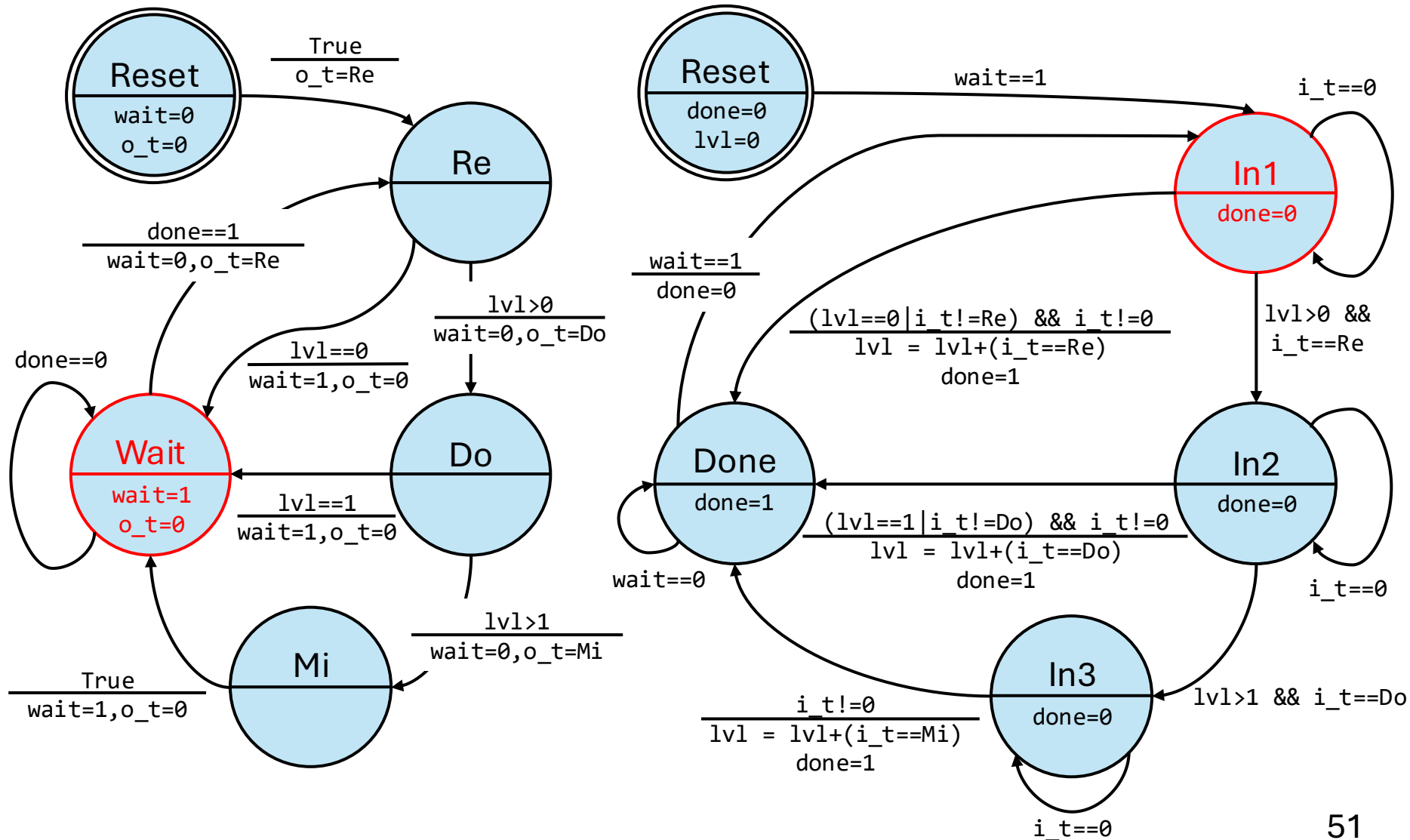
Example: Music Toy (Prompt + Response FSMs)



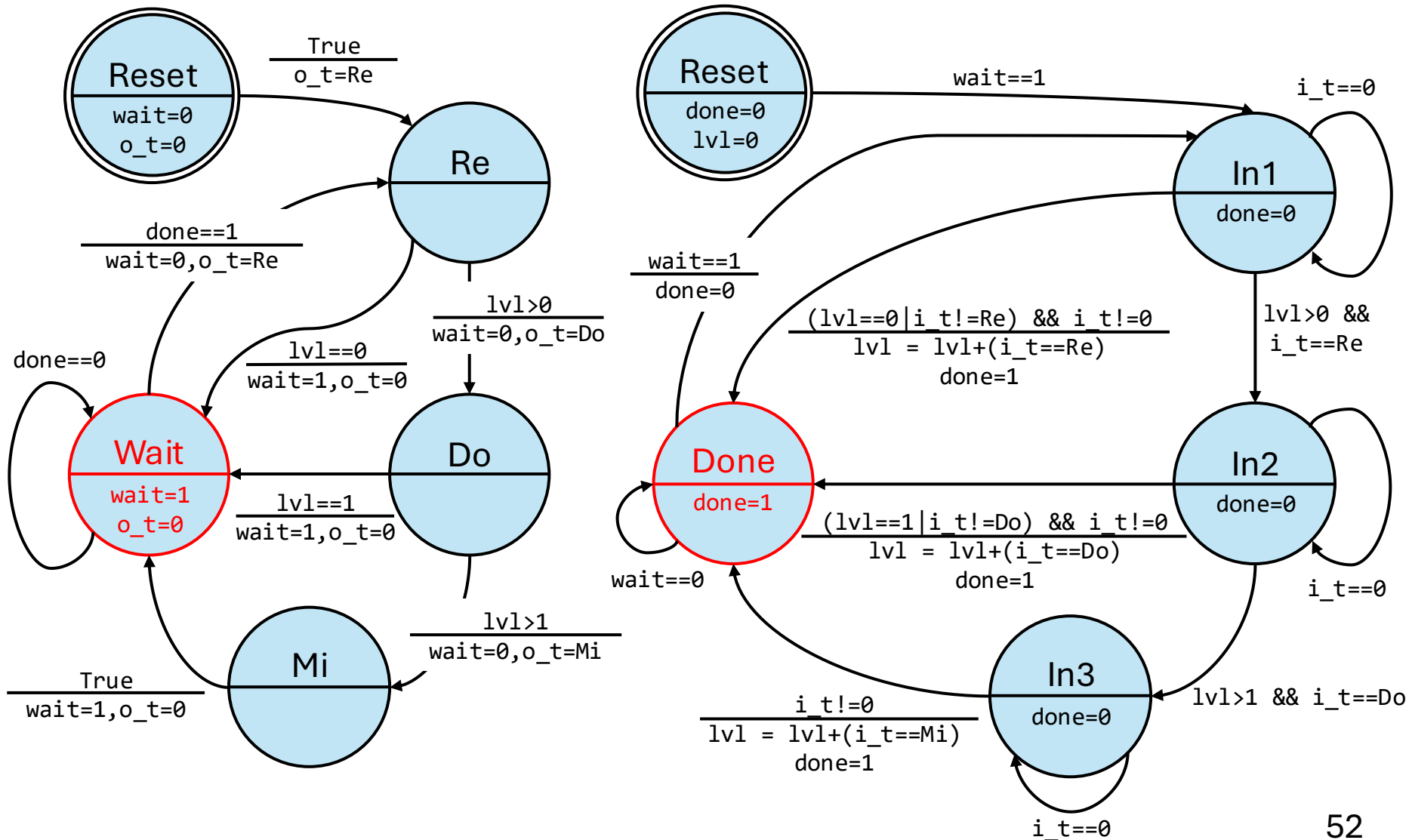
Example: Music Toy (Prompt + Response FSMs)



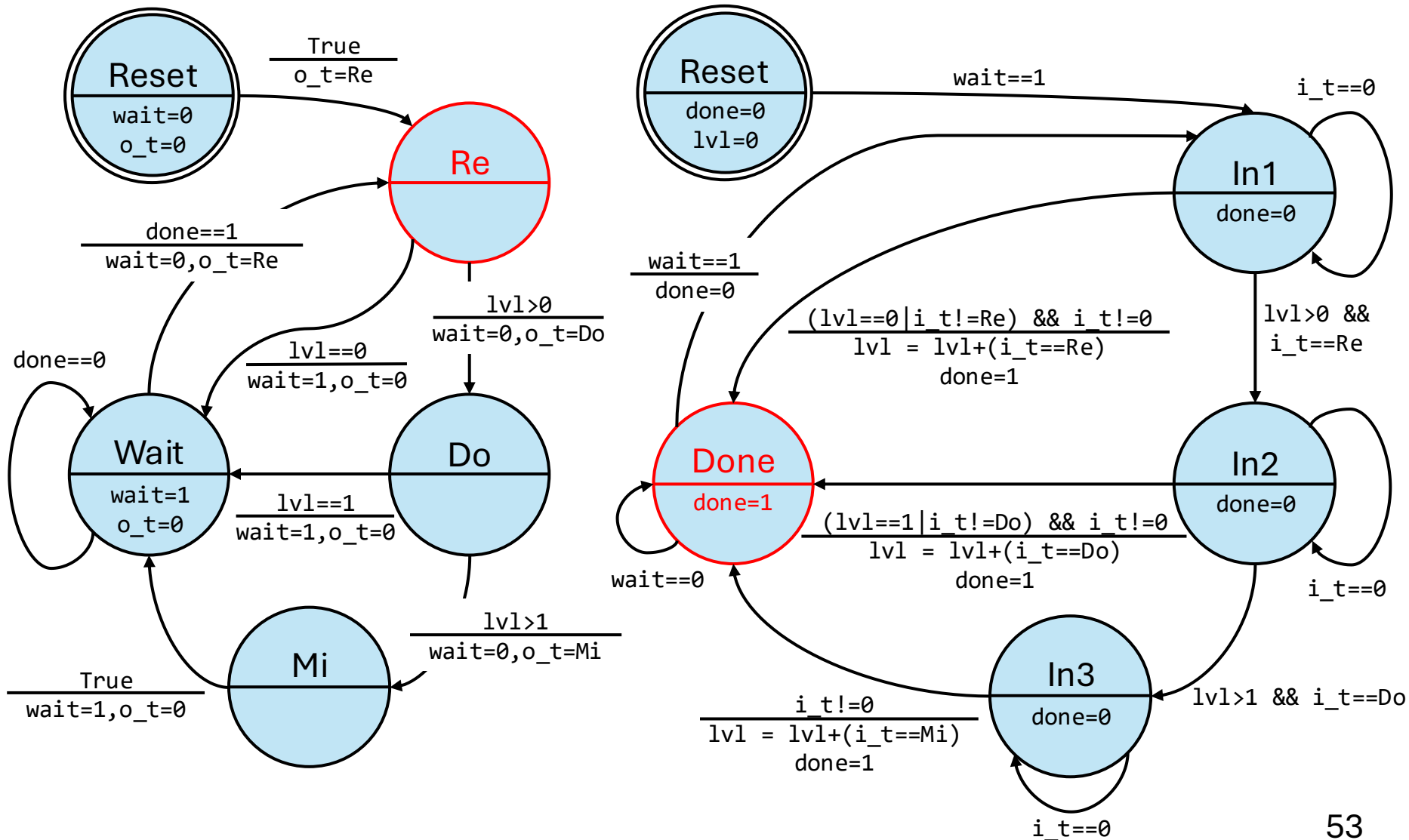
Example: Music Toy (Prompt + Response FSMs)



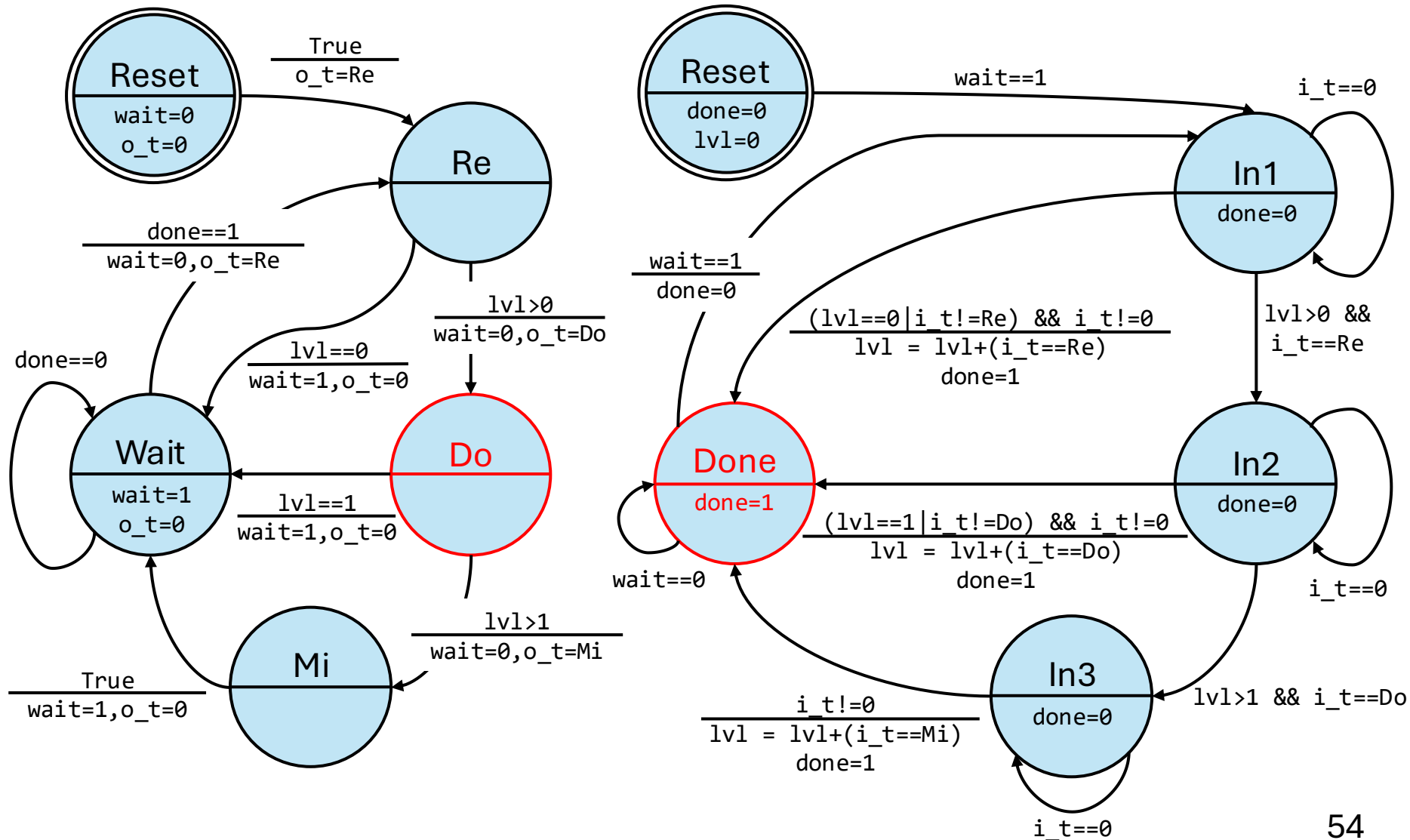
Example: Music Toy (Prompt + Response FSMs)



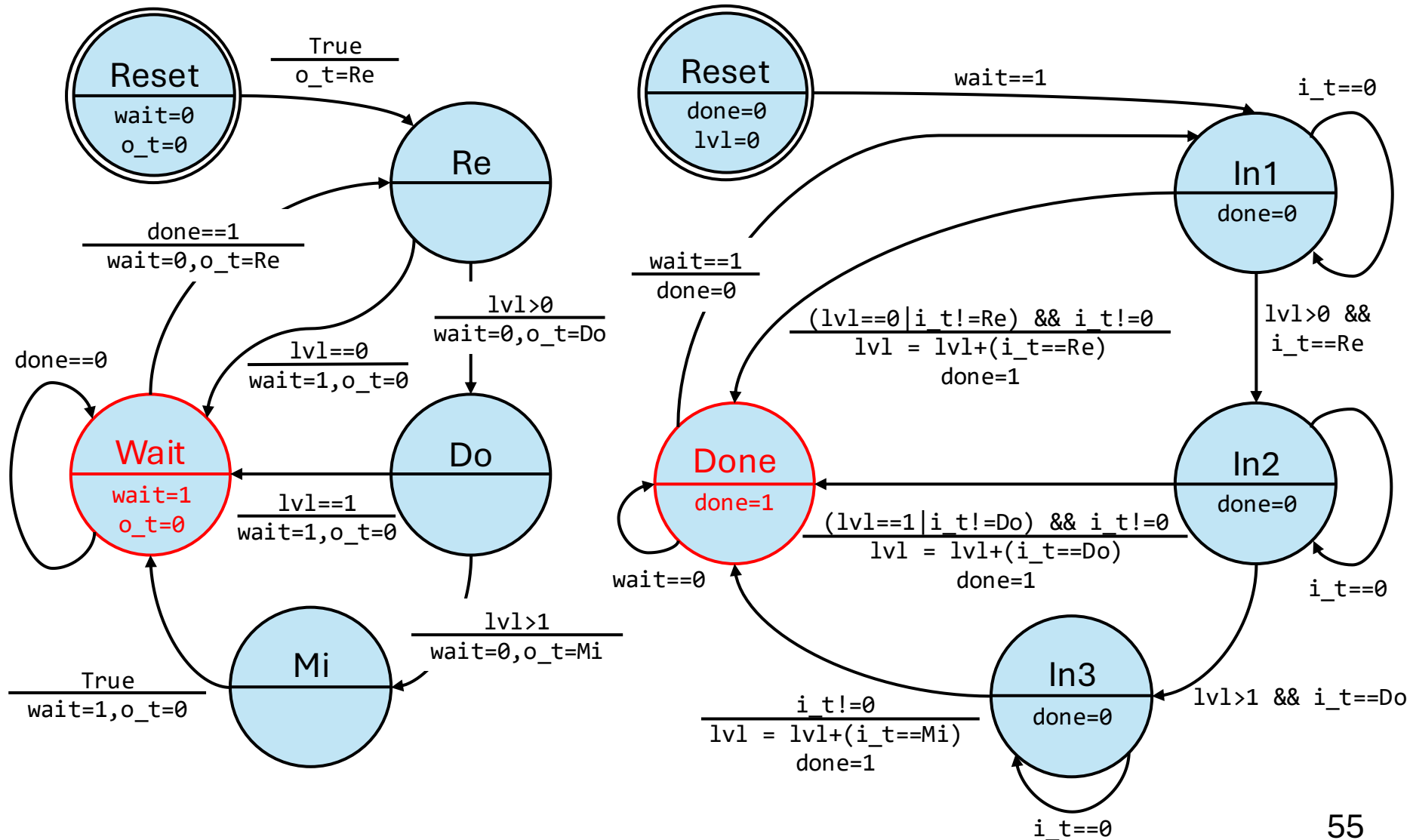
Example: Music Toy (Prompt + Response FSMs)



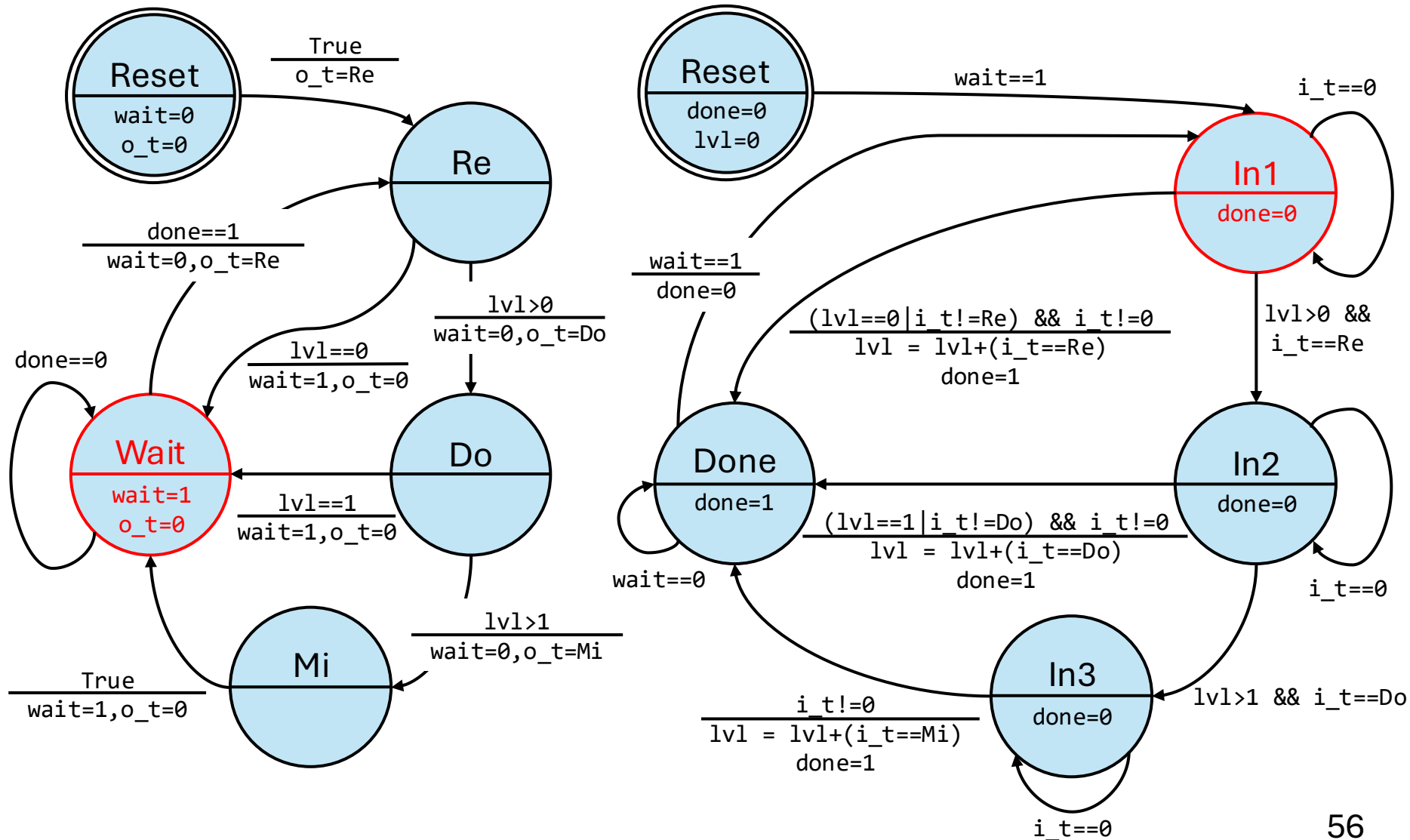
Example: Music Toy (Prompt + Response FSMs)



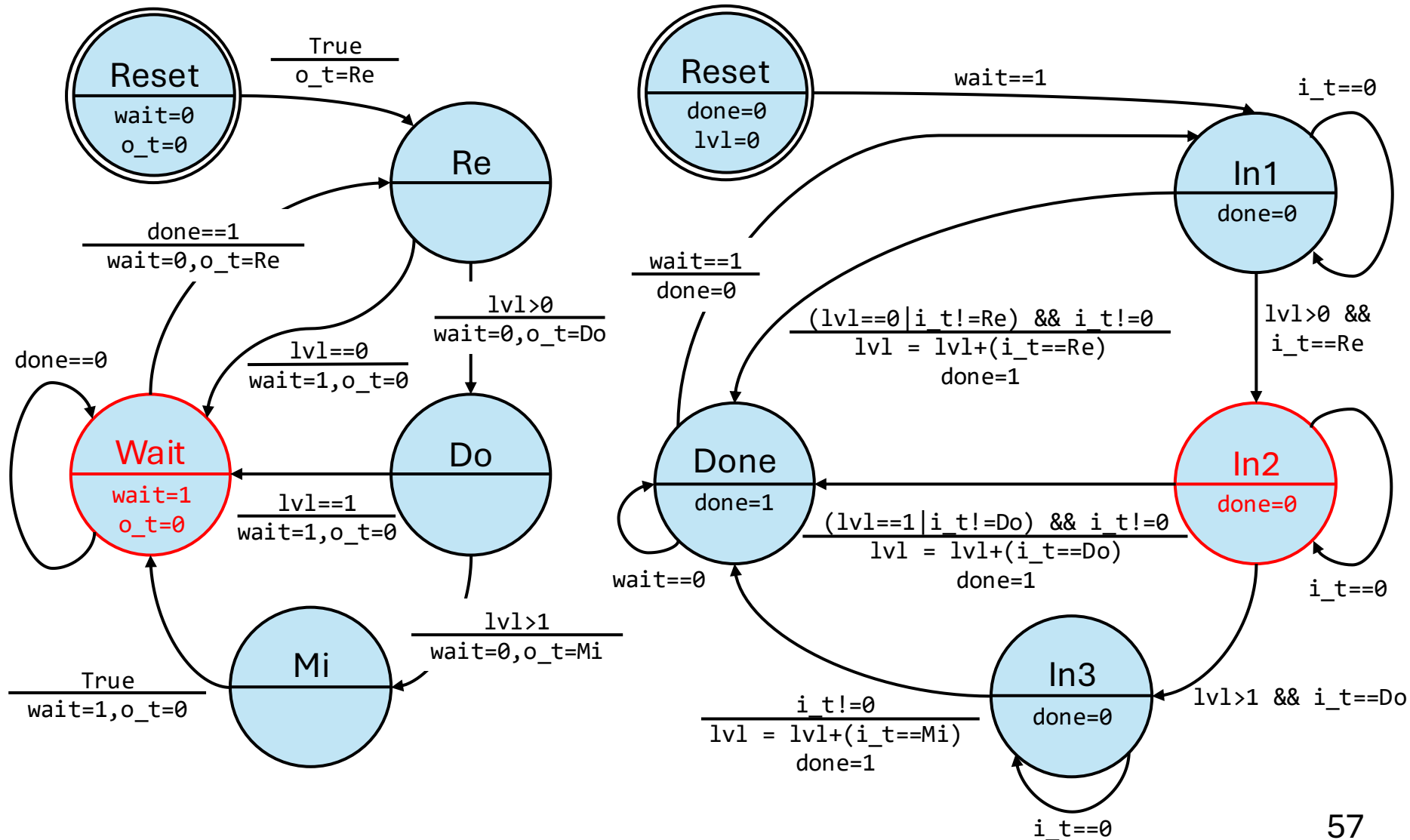
Example: Music Toy (Prompt + Response FSMs)



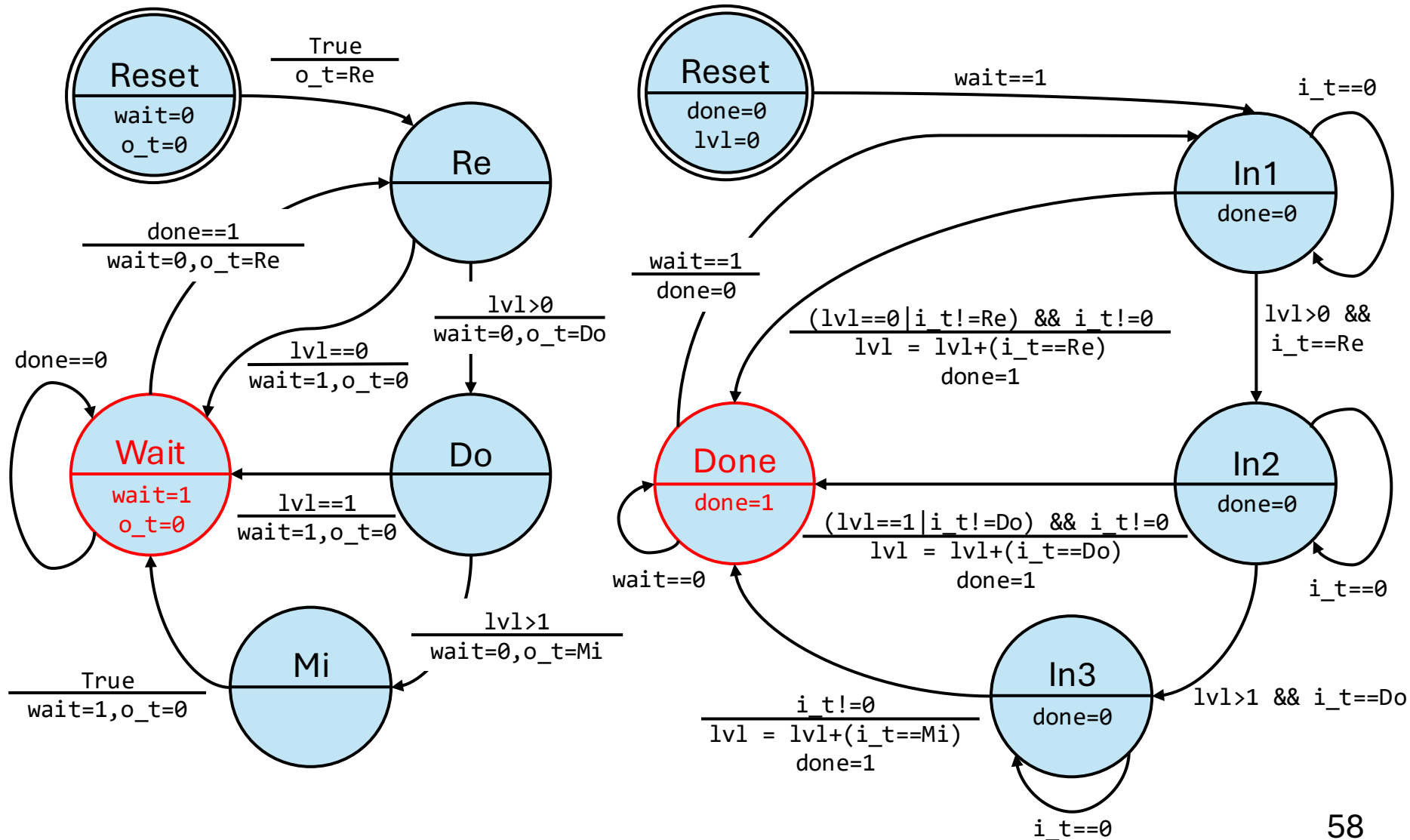Example: Music Toy (Prompt + Response FSMs)



Example: Music Toy (Waveform)

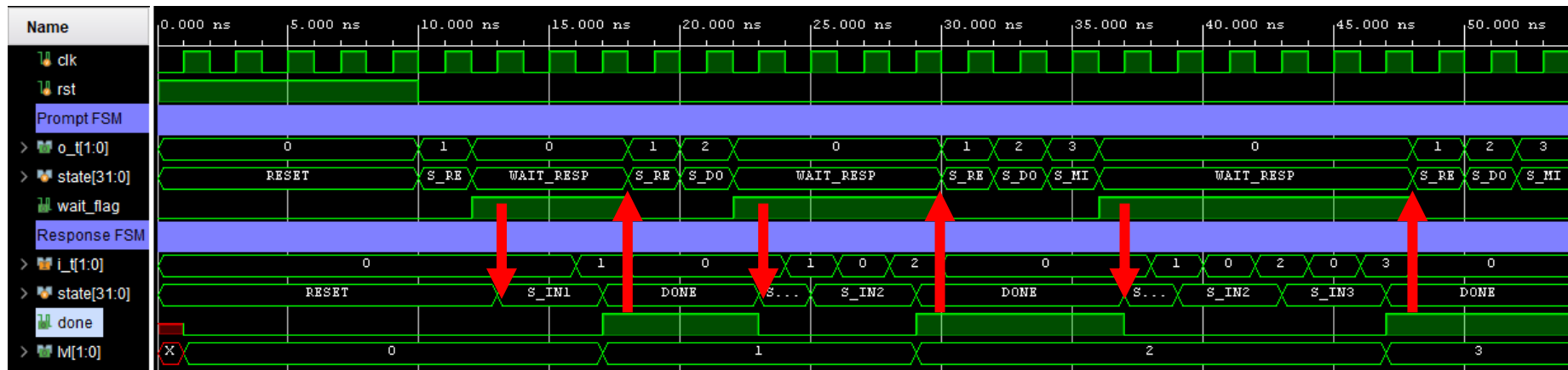


Finite State Machine + Datapath (FSMD)

- In many cases, FSMs are used to control a **time-multiplexed datapath** to perform a specific sequence of operations
 - Datapath can perform different operations (e.g., ALU from your lab 1)
 - FSM orchestrates the use of datapath in each clock cycle
- Example: In a processor ...
 - FSM is the instruction decode + program counter
 - Datapath is ALU with multiplexers and bypass logic
- In FSMD, the FSM generates multiplexer select lines

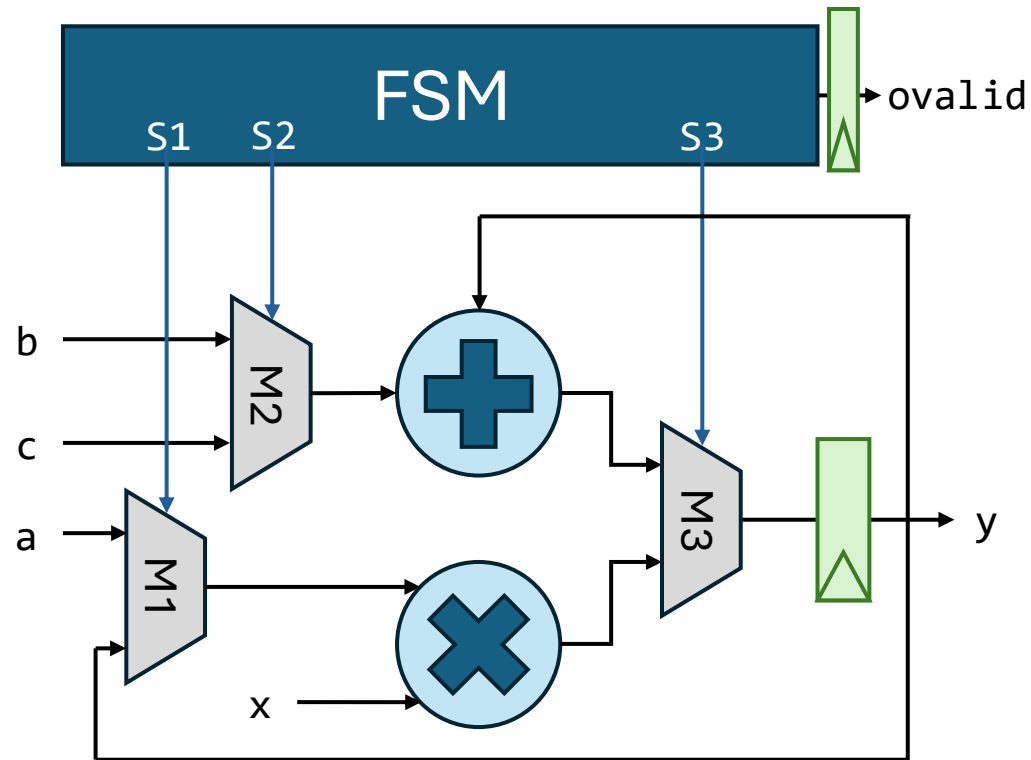
Example: Polynomial Revisited

- Compute $y = ax^2 + bx + c$ using only 1 multiplier & 1 adder
- Refactor computation as $y = [(ax+b)x] + c$ to perform over 4 steps:



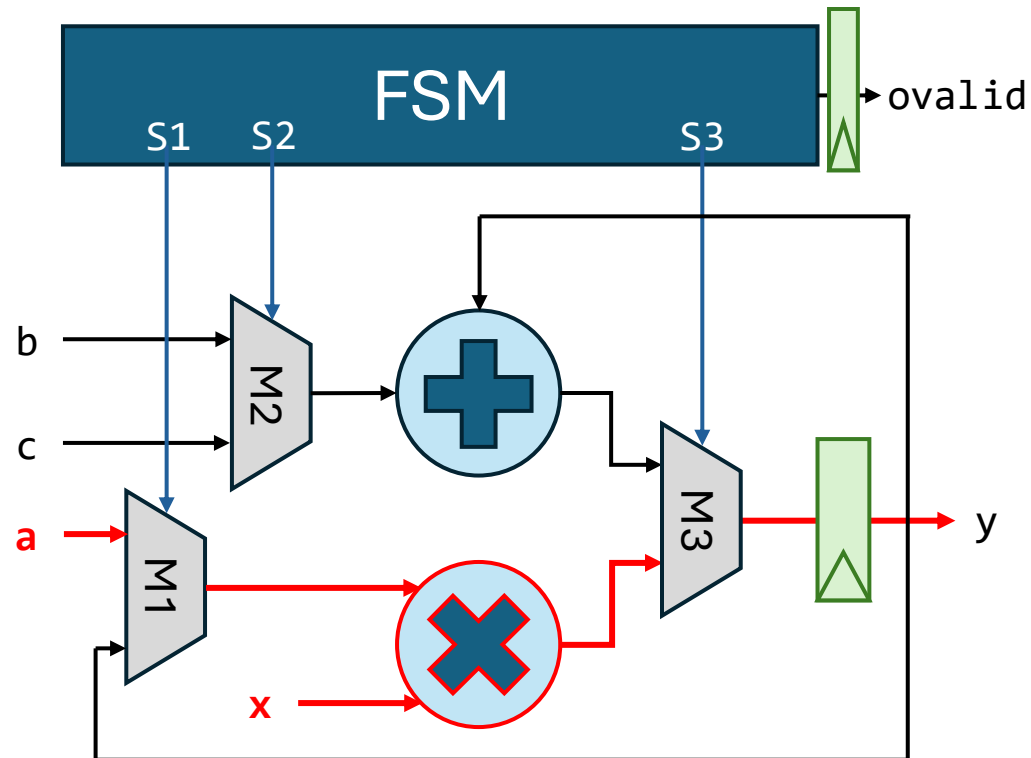
Example: Polynomial Revisited

- Compute $y = ax^2 + bx + c$ using only 1 multiplier & 1 adder
- Refactor computation as $y = [(ax+b)x] + c$ to perform over 4 steps:
 1. $tmp = a * x$



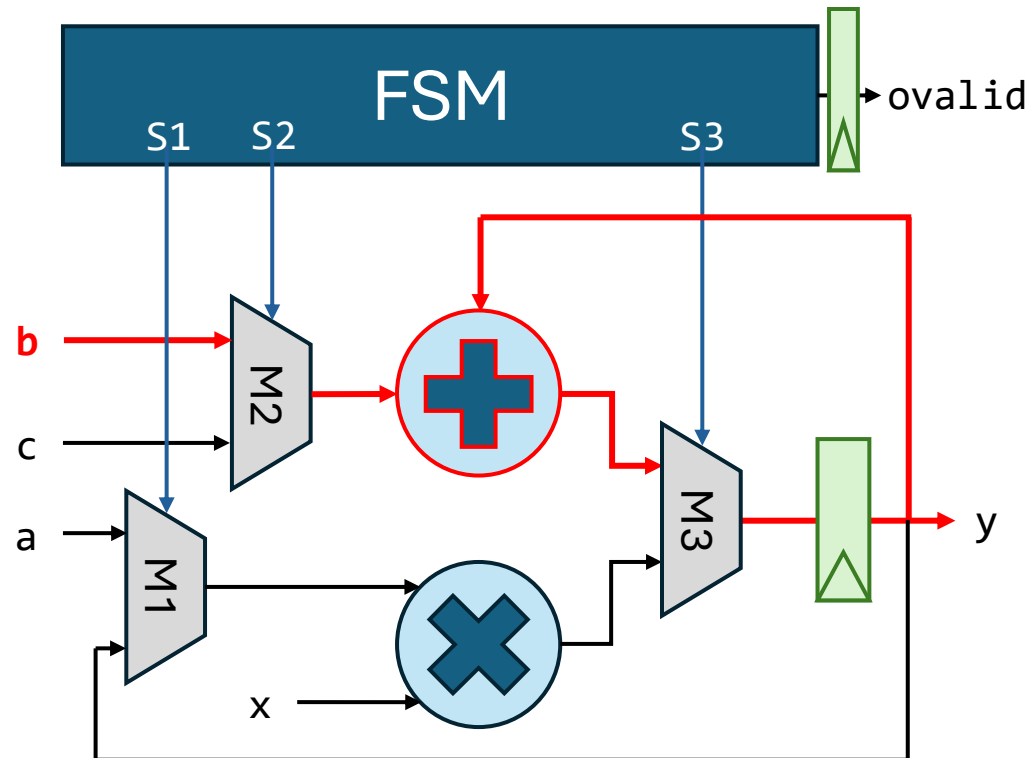
Example: Polynomial Revisited

- Compute $y = ax^2 + bx + c$ using only 1 multiplier & 1 adder
- Refactor computation as $y = [(ax+b)x] + c$ to perform over 4 steps:
 1. $tmp = a * x$
 2. $tmp = tmp + b$



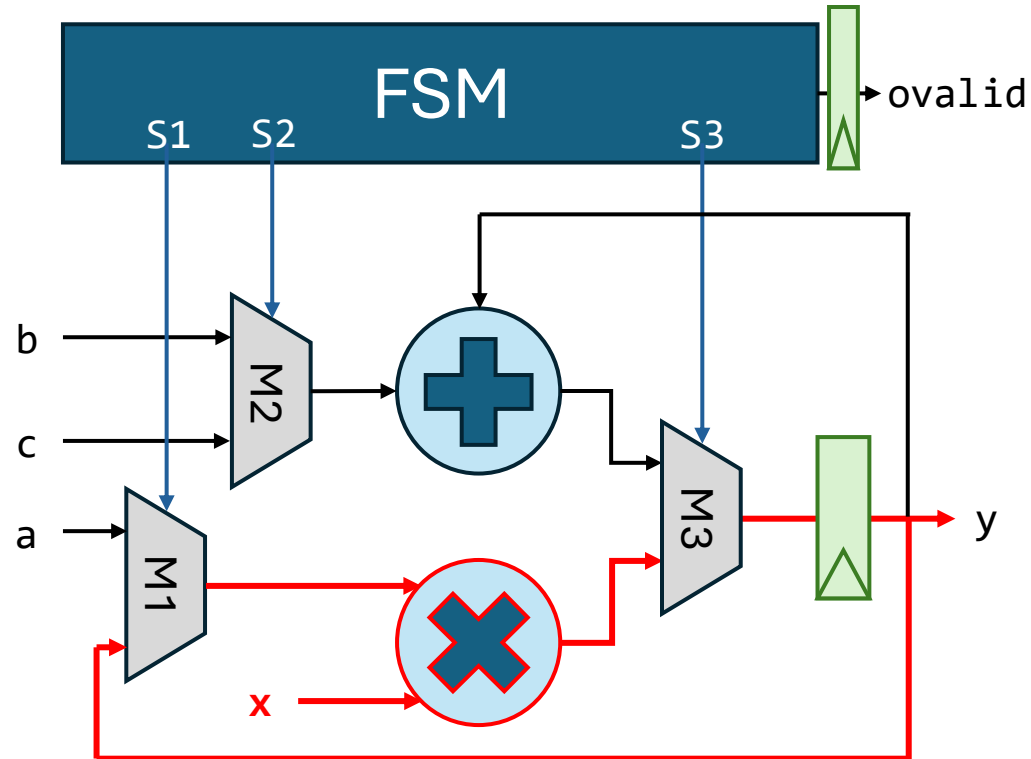
Example: Polynomial Revisited

- Compute $y = ax^2 + bx + c$ using only 1 multiplier & 1 adder
- Refactor computation as $y = [(ax+b)x] + c$ to perform over 4 steps:
 1. $tmp = a * x$
 2. $tmp = tmp + b$
 3. $tmp = tmp * x$



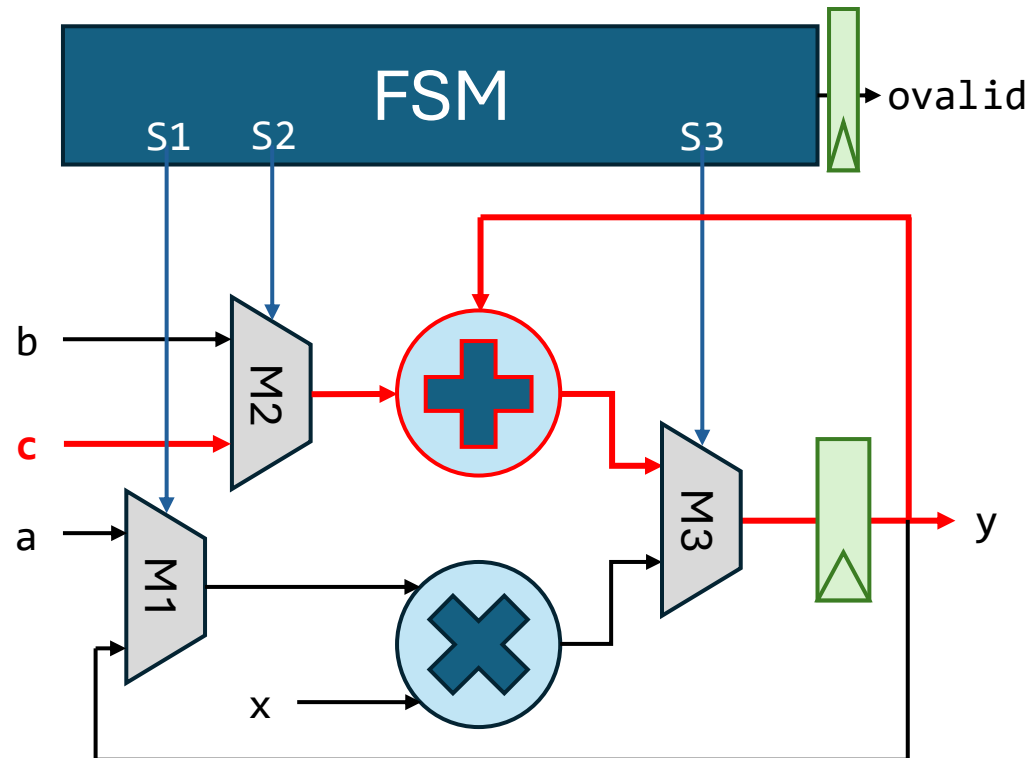
Example: Polynomial Revisited

- Compute $y = ax^2 + bx + c$ using only 1 multiplier & 1 adder
- Refactor computation as $y = [(ax+b)x] + c$ to perform over 4 steps:
 1. $tmp = a * x$
 2. $tmp = tmp + b$
 3. $tmp = tmp * x$
 4. $y = tmp + c$





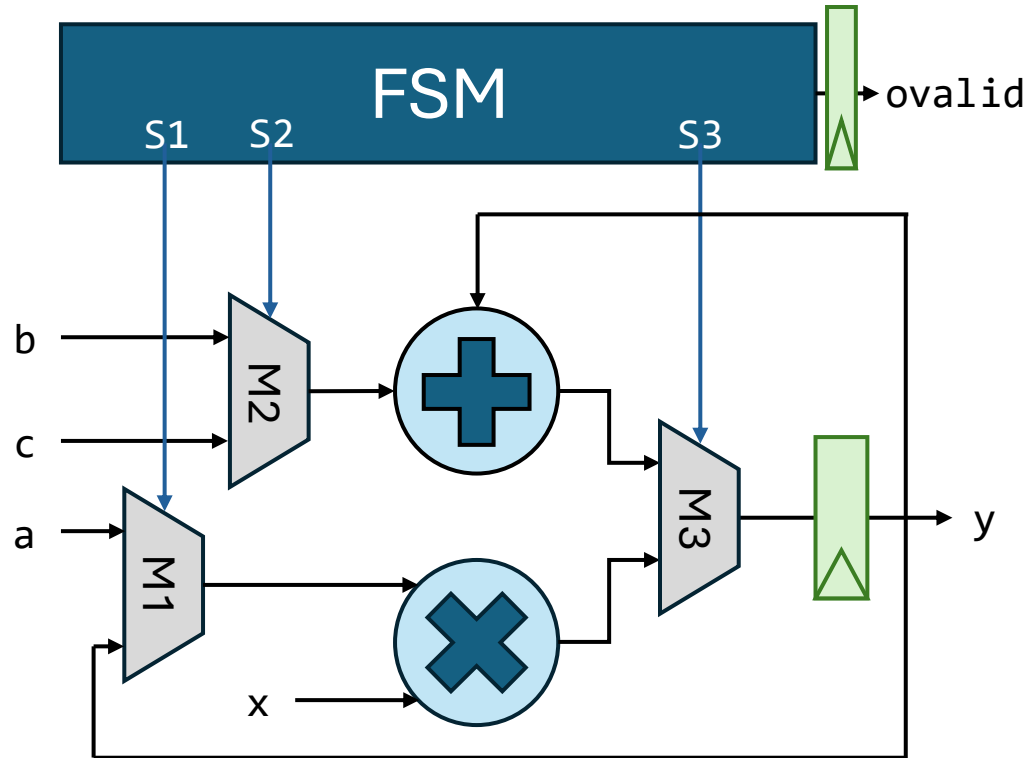Example: Polynomial Revisited (Datapath Code)



```
module poly_datapath (  
    input clk,  
    input rst,  
    input signed [7:0] a,  
    input signed [7:0] b,  
    input signed [7:0] c,  
    input signed [7:0] x,  
    input s1,  
    input s2,  
    input s3,  
    output logic signed [31:0] y  
);  
  
    logic signed [7:0] m1_out, m2_out, m3_out;  
  
    assign m1_out = (s1)? y : a;  
    assign m2_out = (s2)? c : b;  
    assign m3_out = (s3)? m1_out*x : m2_out+y;  
  
    always_ff @ (posedge clk) begin  
        if (rst) y <= 'd0;  
        else y <= m3_out;  
    end  
  
endmodule
```



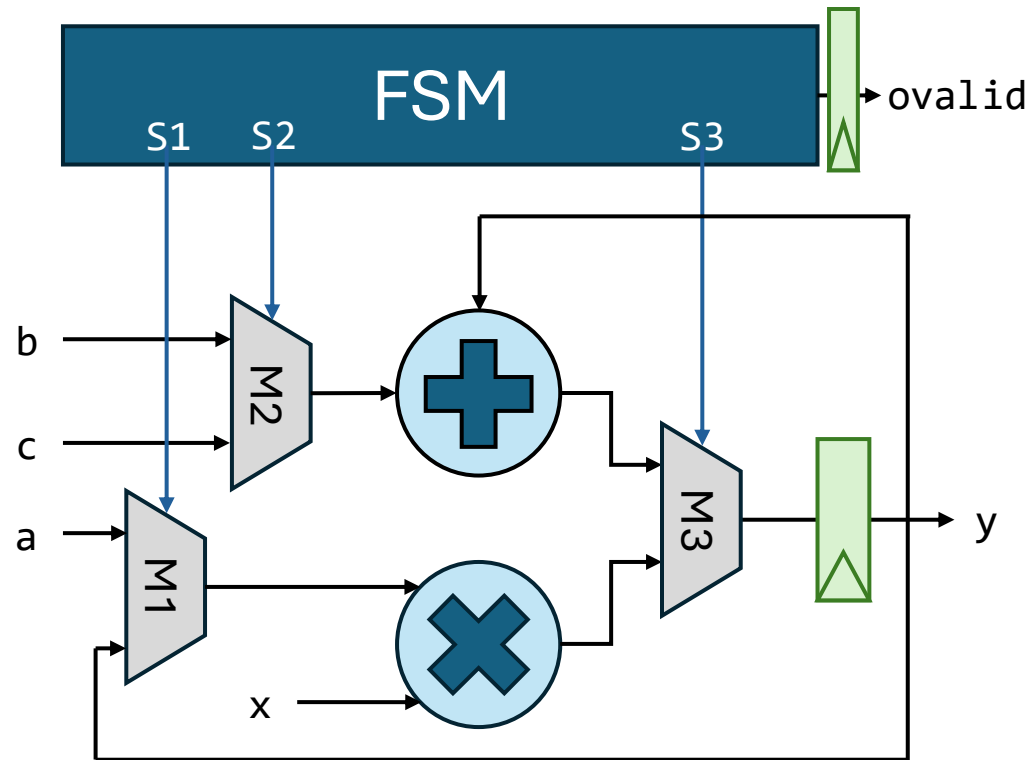
 
Example: Polynomial Revisited (FSM Design)



 
 
Example: Polynomial Revisited (FSM Design)



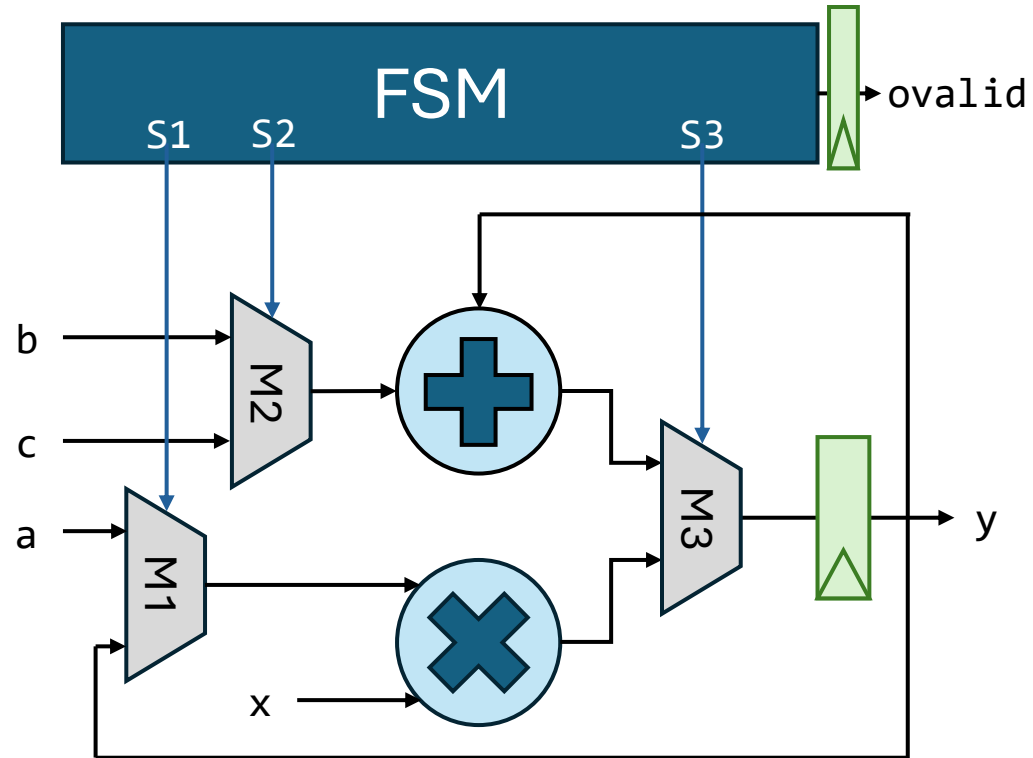
 
Example: Polynomial Revisited (FSM Design)



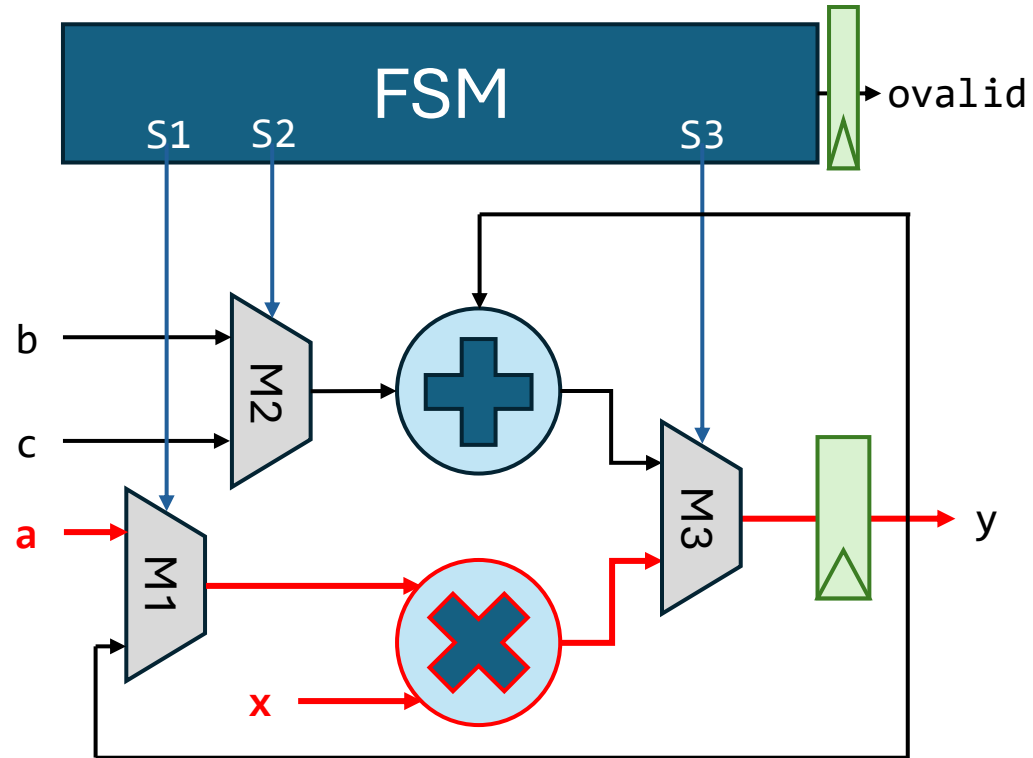
 
Example: Polynomial Revisited (FSM Design)



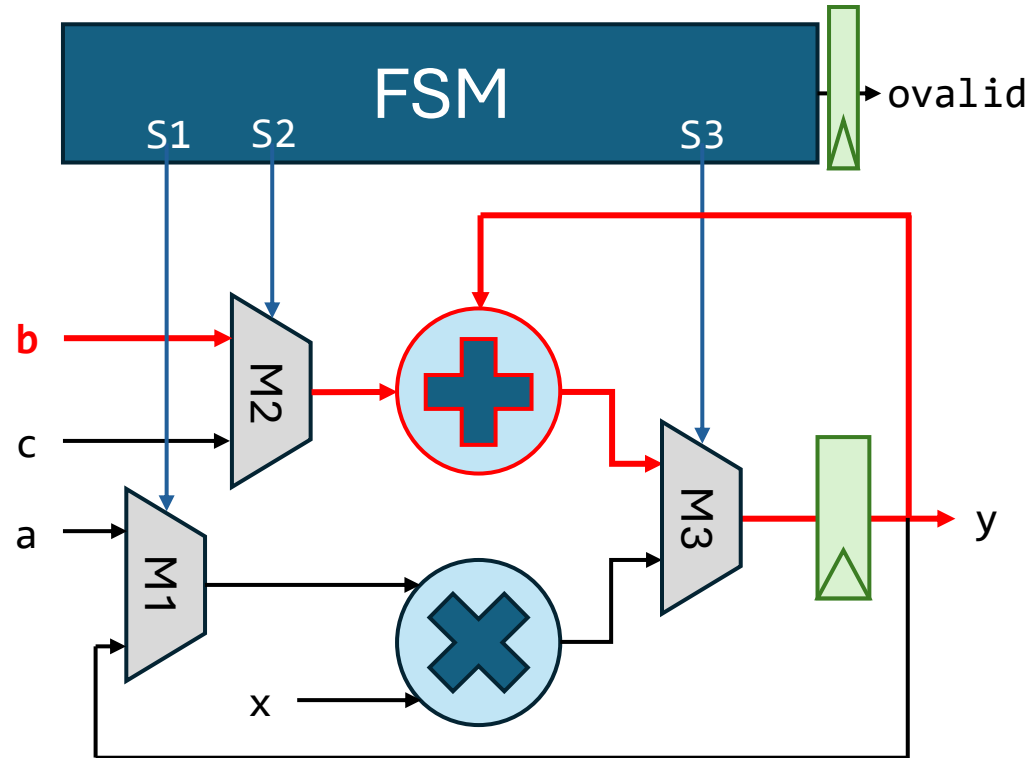
 
Example: Polynomial Revisited (FSM Design)



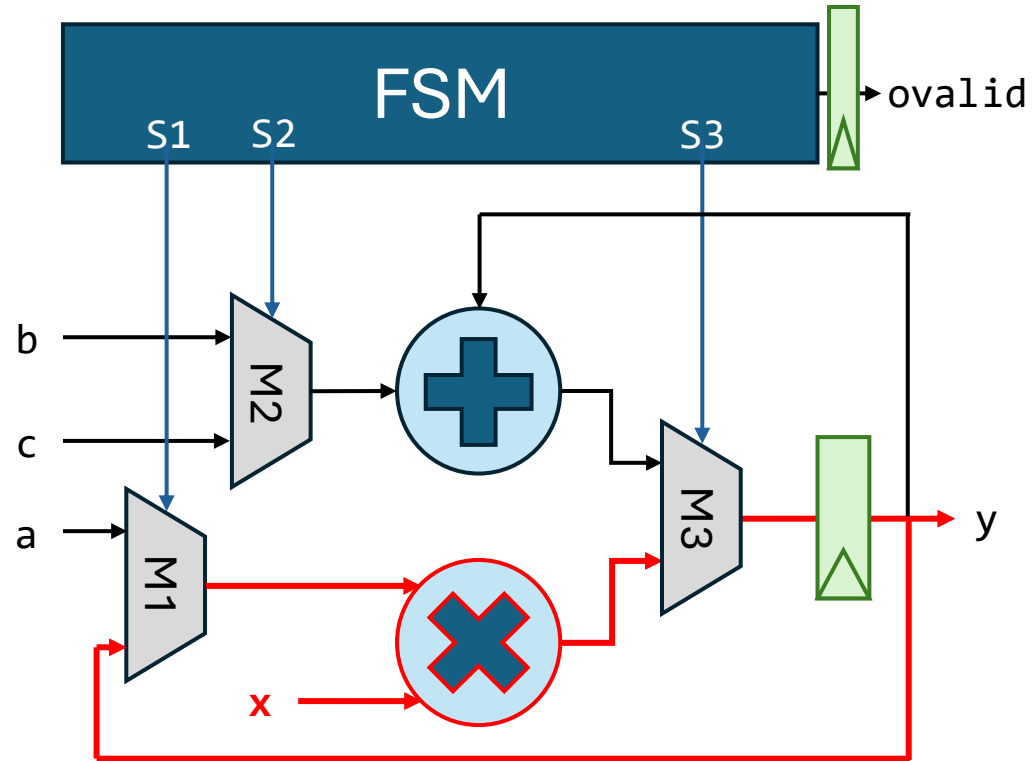 Example: Polynomial Revisited (FSM Design)



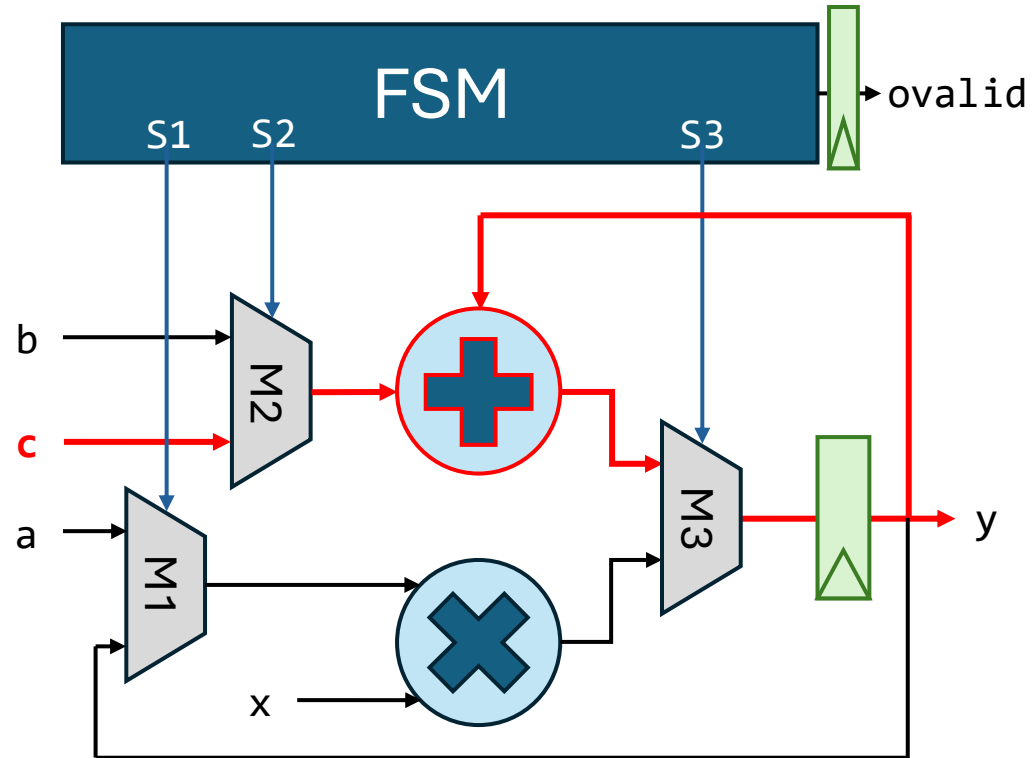 Example: Polynomial Revisited (FSM Design)



Example: Polynomial Revisited (FSM Code)

```
module poly_fsm (  
    input clk,  
    input rst,  
    output logic s1,  
    output logic s2,  
    output logic s3,  
    output logic ovalid  
);
```

```
endmodule
```

Example: Polynomial Revisited (FSM Code)

```
module poly_fsm (  
    input clk,  
    input rst,  
    output logic s1,  
    output logic s2,  
    output logic s3,  
    output logic ovalid  
);  
  
enum {R,S0,S1,S2,S3} state, next_state;  
logic s1_w, s2_w, s3_w, ovalid_w;
```

```
endmodule
```

Example: Polynomial Revisited (FSM Code)

```
module poly_fsm (  
    input clk,  
    input rst,  
    output logic s1,  
    output logic s2,  
    output logic s3,  
    output logic ovalid  
);  
  
enum {R,S0,S1,S2,S3} state, next_state;  
logic s1_w, s2_w, s3_w, ovalid_w;  
  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        s1 <= 1'b0; s2 <= 1'b0; s3 <= 1'b0;  
        state <= R; ovalid <= 1'b0;  
    end else begin  
        s1 <= s1_w; s2 <= s2_w; s3 <= s3_w;  
        state <= next_state; ovalid <= ovalid_w;  
    end  
end
```

```
endmodule
```

Example: Polynomial Revisited (FSM Code)

```
module poly_fsm (  
    input clk,  
    input rst,  
    output logic s1,  
    output logic s2,  
    output logic s3,  
    output logic ovalid  
);  
  
enum {R,S0,S1,S2,S3} state, next_state;  
logic s1_w, s2_w, s3_w, ovalid_w;  
  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        s1 <= 1'b0; s2 <= 1'b0; s3 <= 1'b0;  
        state <= R; ovalid <= 1'b0;  
    end else begin  
        s1 <= s1_w; s2 <= s2_w; s3 <= s3_w;  
        state <= next_state; ovalid <= ovalid_w;  
    end  
end  
  
always_comb begin: state_decoder  
    case (state)  
        R : next_state = S0;  
        S0: next_state = S1;  
        S1: next_state = S2;  
        S2: next_state = S3;  
        S3: next_state = S0;  
        default: next_state = R;  
    endcase  
end
```

```
endmodule
```


Example: Polynomial Revisited (FSM Code)

```
module poly_fsm (  
    input clk,  
    input rst,  
    output logic s1,  
    output logic s2,  
    output logic s3,  
    output logic ovalid  
);  
  
enum {R,S0,S1,S2,S3} state, next_state;  
logic s1_w, s2_w, s3_w, ovalid_w;  
  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        s1 <= 1'b0; s2 <= 1'b0; s3 <= 1'b0;  
        state <= R; ovalid <= 1'b0;  
    end else begin  
        s1 <= s1_w; s2 <= s2_w; s3 <= s3_w;  
        state <= next_state; ovalid <= ovalid_w;  
    end  
end  
  
always_comb begin: state_decoder  
    case (state)  
        R : next_state = S0;  
        S0: next_state = S1;  
        S1: next_state = S2;  
        S2: next_state = S3;  
        S3: next_state = S0;  
        default: next_state = R;  
    endcase  
end
```

```
always_comb begin: output_decoder  
    case (state)  
        R : begin  
            s1_w = 1'b0; s2_w = 1'b0; s3_w = 1'b0;  
            ovalid_w = 1'b0;  
        end  
        S0: begin  
            s1_w = 1'b0; s2_w = 1'b0; s3_w = 1'b1;  
            ovalid_w = 1'b0;  
        end  
        S1: begin  
            s1_w = 1'b0; s2_w = 1'b0; s3_w = 1'b0;  
            ovalid_w = 1'b0;  
        end  
        S2: begin  
            s1_w = 1'b1; s2_w = 1'b0; s3_w = 1'b1;  
            ovalid_w = 1'b0;  
        end  
        S3: begin  
            s1_w = 1'b0; s2_w = 1'b1; s3_w = 1'b0;  
            ovalid_w = 1'b1;  
        end  
        default: begin  
            s1_w = 1'b0; s2_w = 1'b0; s3_w = 1'b0;  
            ovalid_w = 1'b0;  
        end  
    endcase  
end  
  
endmodule
```

 
Example: Polynomial Revisited (Datapath Code)

```
module top_level (  
    input clk,  
    input rst,  
    input signed [7:0] a,  
    input signed [7:0] b,  
    input signed [7:0] c,  
    input signed [7:0] x,  
    output signed [31:0] y,  
    output logic ovalid  
);  
  
logic s1, s2, s3, fsm_ovalid;  
  
poly_datapath dp_inst(  
    clk, rst, a, b, c, x, s1, s2, s3, y  
);  
  
poly_fsm fsm_inst(  
    clk, rst, s1, s2, s3, fsm_ovalid  
);  
  
always_ff @ (posedge clk) begin  
    if (rst) ovalid <= 1'b0;  
    else ovalid <= fsm_ovalid;  
end  
  
endmodule
```



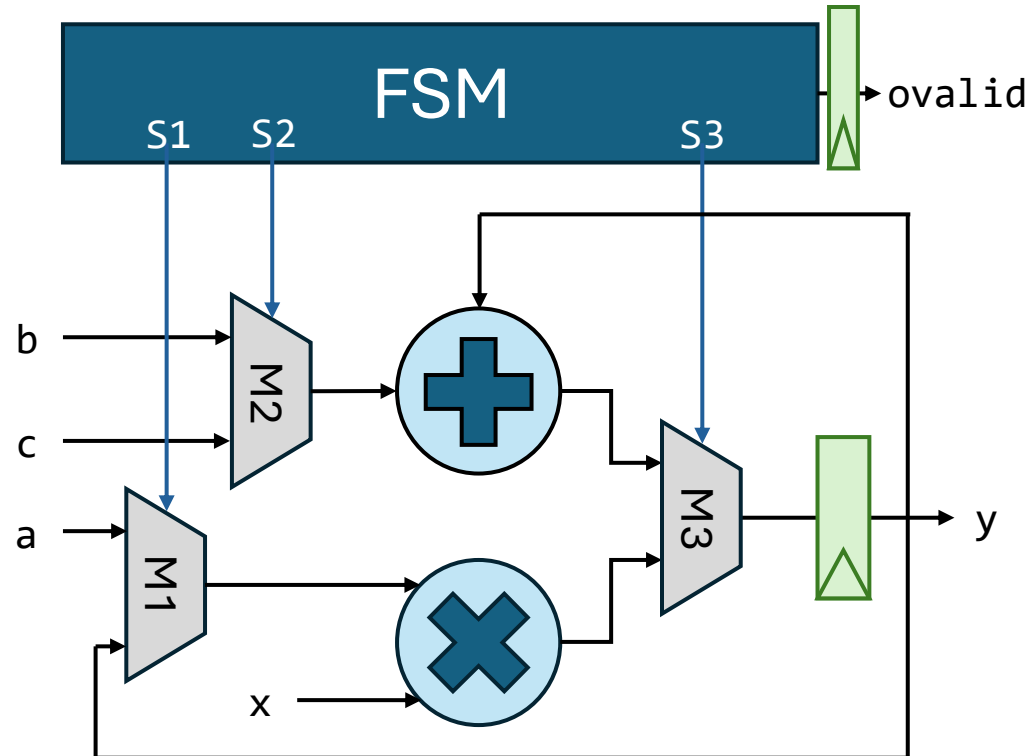Example: Polynomial Revisited (Datapath Code)

```
module top_level (  
    input clk,  
    input rst,  
    input signed [7:0] a,  
    input signed [7:0] b,  
    input signed [7:0] c,  
    input signed [7:0] x,  
    output signed [31:0] y,  
    output logic ovalid  
);  
  
logic s1, s2, s3, fsm_ovalid;  
  
poly_datapath dp_inst(  
    clk, rst, a, b, c, x, s1, s2, s3, y  
);  
  
poly_fsm fsm_inst(  
    clk, rst, s1, s2, s3, fsm_ovalid  
);  
  
always_ff @ (posedge clk) begin  
    if (rst) ovalid <= 1'b0;  
    else ovalid <= fsm_ovalid;  
end  
  
endmodule
```



Why do we need this?



Summary

- FSMs can have complex control flow with multiple possible transitions from each state
 - Carefully defined state transition conditions guarantee mutual exclusivity and preserved priority
- FSMs can interact with each other
 - Must pay attention to cycle/timing of interacting signals
- FSMs can be used to control datapath (FSMD design style)
 - Decouple compute datapath from control logic

Next Lecture

Improving circuit throughput via pipelining ...