

# **ECE 327/627**

# **Digital Hardware Systems**

## **Lecture 10: FIFO-Based Dataflow Design**

Andrew Boutros

[andrew.boutros@uwaterloo.ca](mailto:andrew.boutros@uwaterloo.ca)

# Some Logistics


- Lab 3 was released on Friday
  - Worth **8%** of the ECE 327 total course grade
  - Worth **4%** of the ECE 327 total course grade
  - Deadline **March 6 @ 11:59 pm**
- ECE 627 Course Project handout posted last night
  - Project selection and approval due in a week (**Feb 16 @ 11:59 pm**)
- Lab 1 grades were released yesterday
  - Class average is **89%**
- Lab 2 individual assessment in this week's lab sessions
  - Worth **40%** of the lab 2 grade
  - Special schedule due to sharing the quiz room with another course – check Piazza and be on time
- You will not be tested on this lecture's content in the midterm
- No new content next lecture → midterm review

# In the Previous Lecture ...


- Latency-insensitive design
  - Wire delays are becoming problematic in newer process technologies
  - Pipelining wires is not very straightforward if modules are latency-sensitive (i.e., expect inputs exactly at specific cycles)
  - Ready-valid handshakes
    - Sender produces data tagged with a valid bit
    - Receiver indicates whether ready to accept data or not
    - Transaction happens when valid & ready are both asserted
    - Regardless when that happens, functionality doesn't break
  - This allows pipelining data & valid signals, but ready must remain combinational to freeze the entire pipeline if not ready → did not solve the wire delay issue
  - Simple pipeline regs are not enough → Relay Stations (Skid Buffers)
    - Pipeline ready signal going in opposite direction
    - Have auxiliary registers to hold 1 extra piece of data until ready is communicated to the upstream module
 
# Throughput Balancing Revisited

- Many designs in practice have several cascaded modules processing data that flows from one module to the next → streaming architectures




 **Throughput of the entire structure = Lowest throughput of all stages**


 
# Throughput Balancing Revisited

- Many designs in practice have several cascaded modules processing data that flows from one module to the next → streaming architectures



**Throughput of the entire structure = Lowest throughput of all stages**

*Ideally, want throughput of all stages of the structure to be balanced*

# Throughput Balancing Revisited






M1

M2




# Throughput Balancing Revisited

   ***Produces 5 elements every 10 cycles!***



# Throughput Balancing Revisited

   ***Produces 5 elements every 10 cycles!***






*Can consume an input  
every other cycle*

***Consumes 5 elements every 10 cycles!***



# Throughput Balancing Revisited

   
***Produces 5 elements every 10 cycles!***




*Can consume an input  
every other cycle*

***Consumes 5 elements every 10 cycles!***


# Throughput Balancing Revisited

 

# Throughput Balancing Revisited

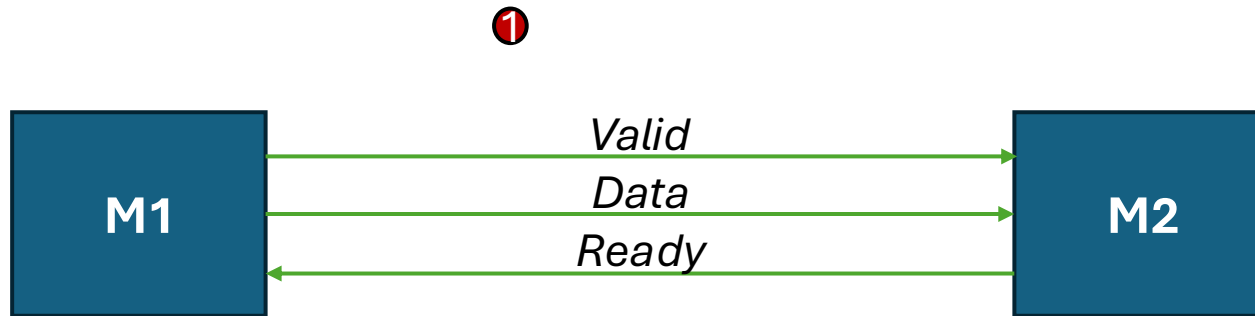


# Throughput Balancing Revisited

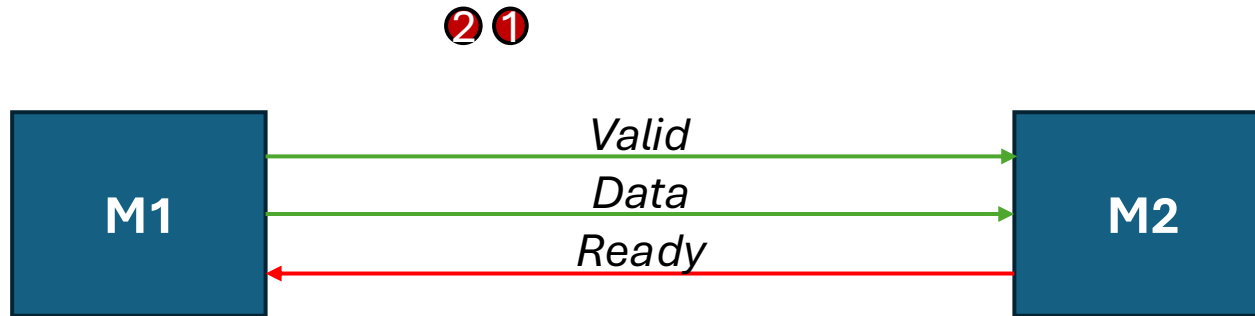


○ 1


# Throughput Balancing Revisited

 


# Throughput Balancing Revisited

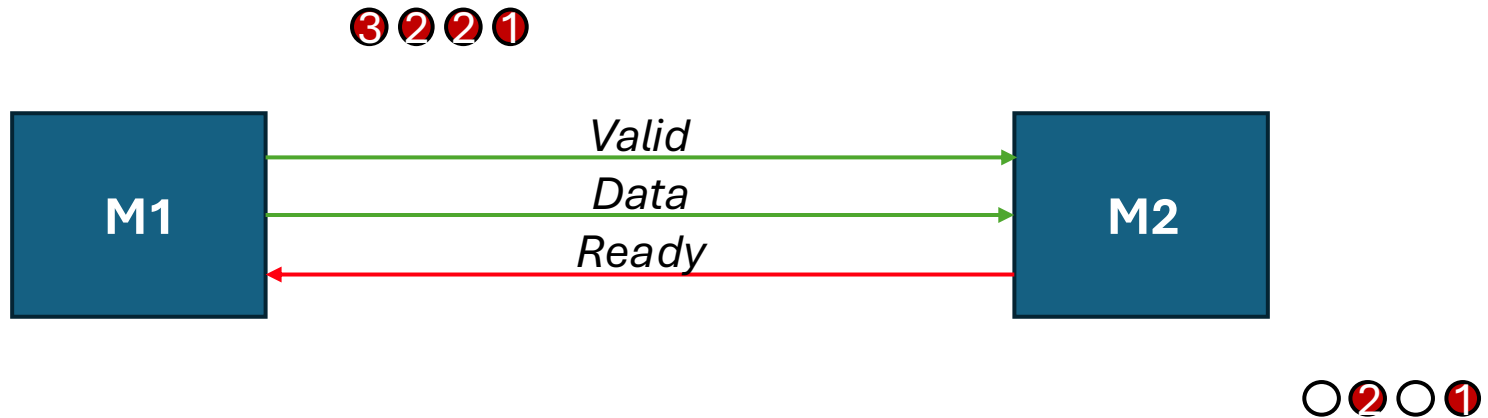

# Throughput Balancing Revisited

 


# Throughput Balancing Revisited

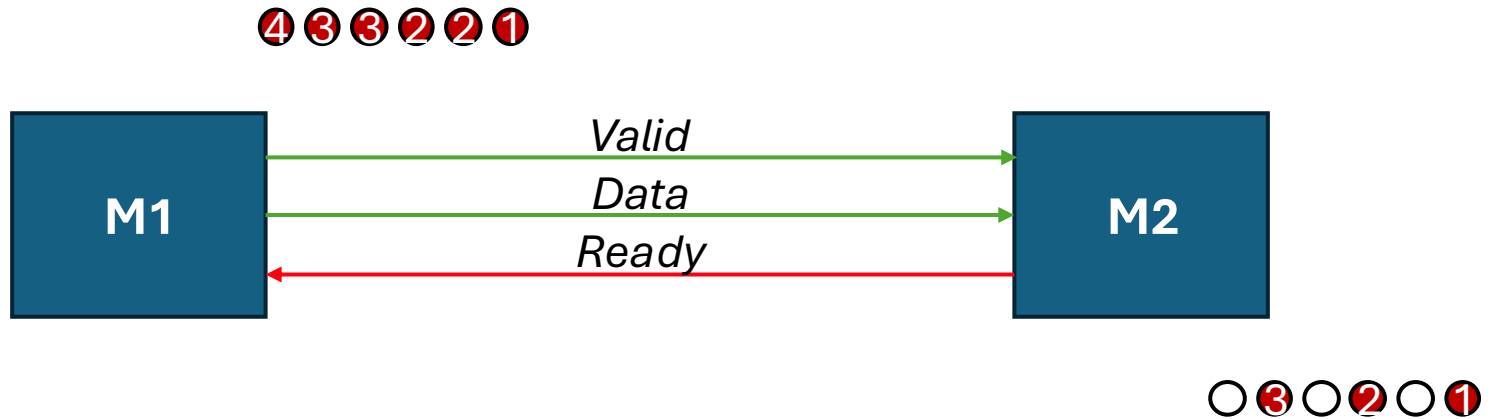





# Throughput Balancing Revisited

 

# Throughput Balancing Revisited

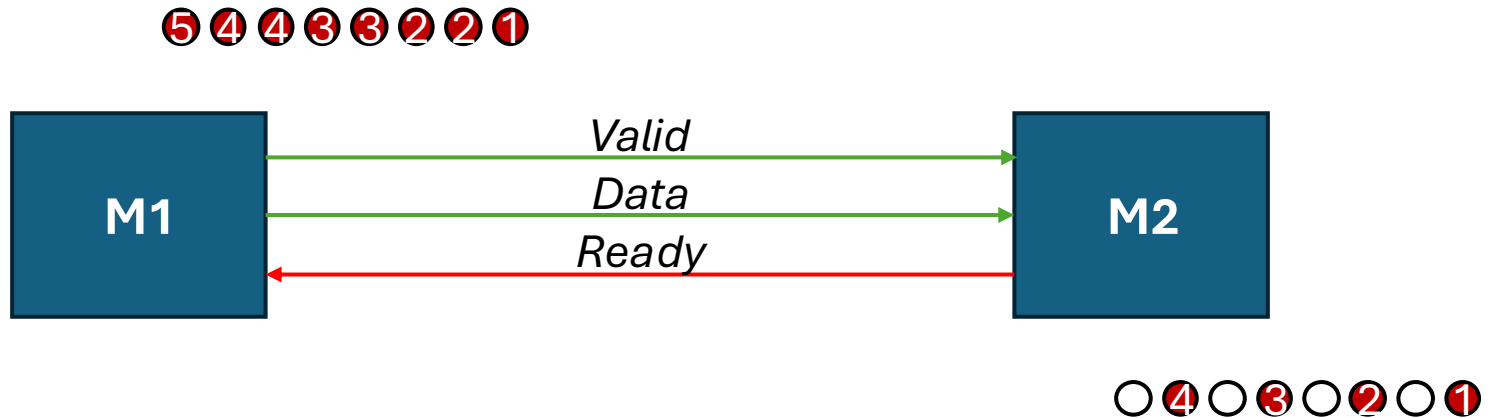


# Throughput Balancing Revisited

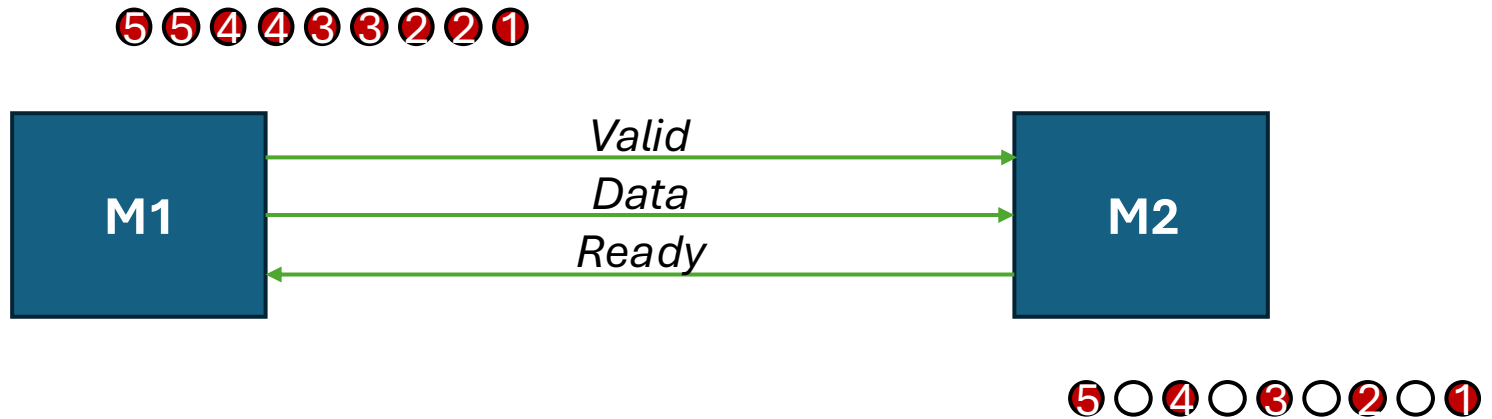


# Throughput Balancing Revisited

*Busy Doing  
Compute*

 


*Valid  
Data  
Ready*

 

*Ready to accept  
new inputs but  
no valid data*

# Throughput Balancing Revisited



*M1 in isolation*

 


*M2 in isolation*

# Throughput Balancing Revisited

*M1 in isolation*

  


 
*M1 & M2 affect each other  
and overall throughput is  
reduced!!*




*M2 in isolation*

# Throughput Balancing Revisited

*M1 in isolation*

  

 *M1 & M2 affect each other  
and overall throughput is  
reduced!!*



*M2 in isolation*

If only we could keep 2 3 4 5 somewhere until M2 is ready to consume them, M1 can proceed to the next compute in the meantime!

# FIFOs can help!

- A **FIFO** is a **first-in first-out** buffer with a push/pop interface
  - Has status output signals (e.g., empty and full)
  - As long as not full → can push data into it
  - As long as not empty → can pop data from it
  - Similar to a queue data structure in software
  - Bitwidth of input/output data & FIFO depth are design parameters






# FIFOs can help!

- A **FIFO** is a **first-in first-out** buffer with a push/pop interface
  - Has status output signals (e.g., empty and full)
  - As long as not full → can push data into it
  - As long as not empty → can pop data from it
  - Similar to a queue data structure in software
  - Bitwidth of input/output data & FIFO depth are design parameters




Can be wrapped to present  
a latency-insensitive  
ready-valid interface


# FIFO-Based Design

 

# FIFO-Based Design

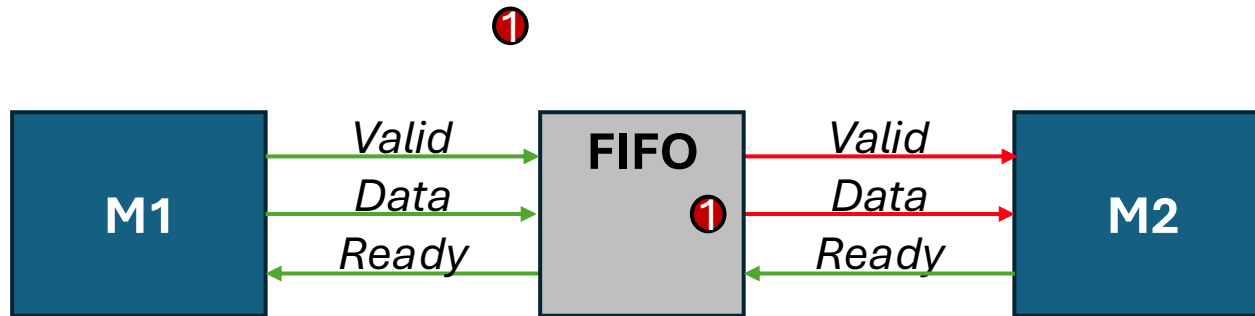


# FIFO-Based Design

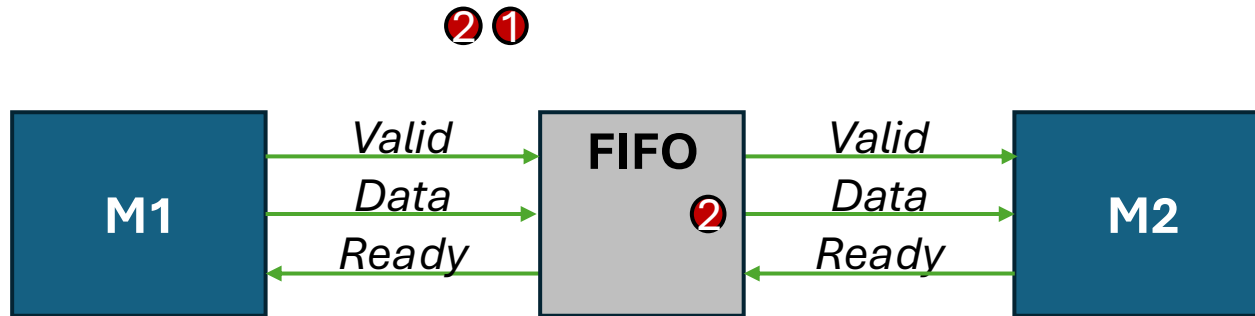


1

# FIFO-Based Design

 


○ 1


# FIFO-Based Design

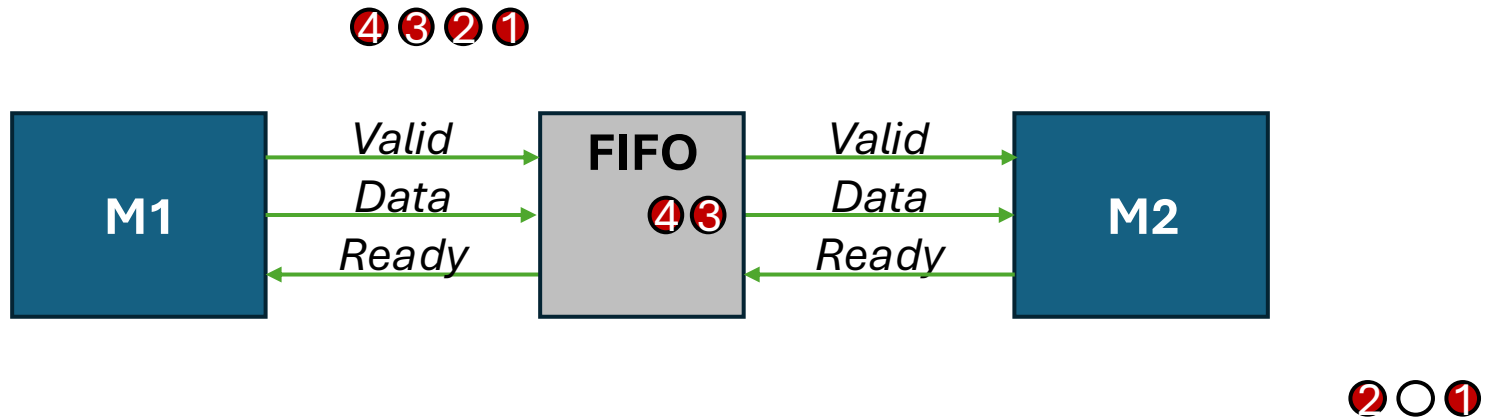

# FIFO-Based Design

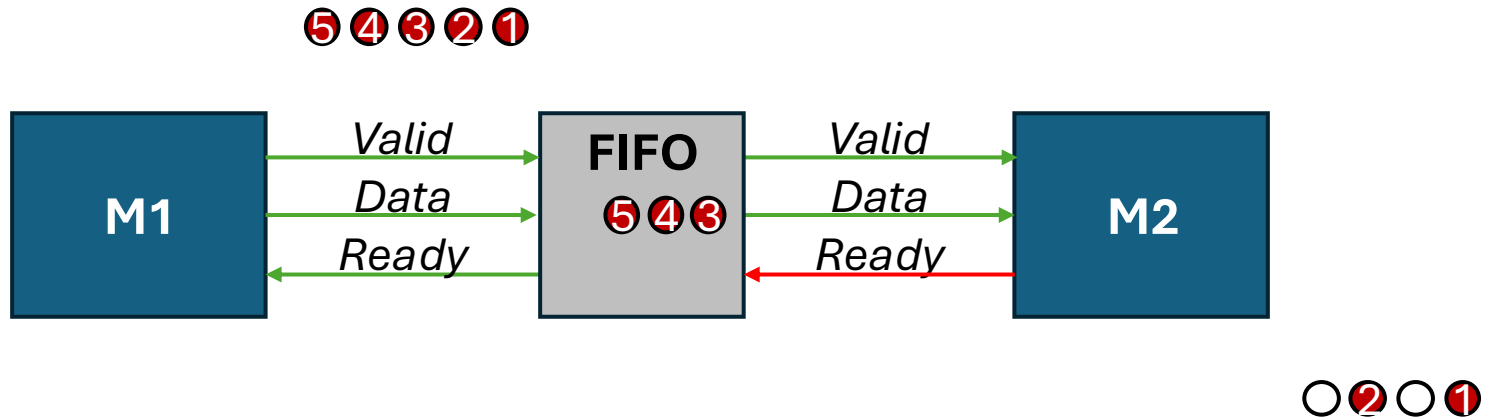


# FIFO-Based Design

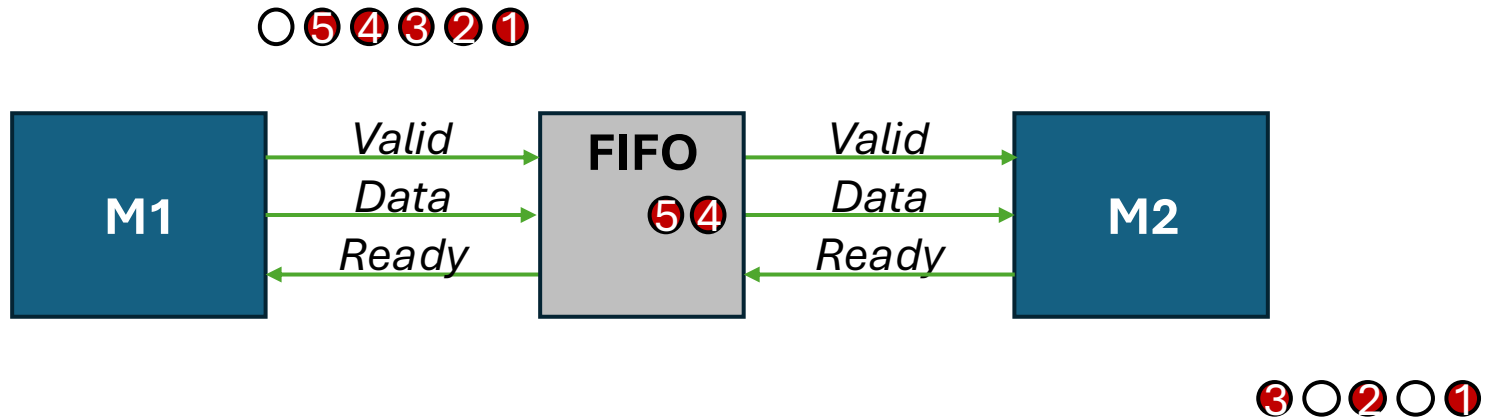





# FIFO-Based Design

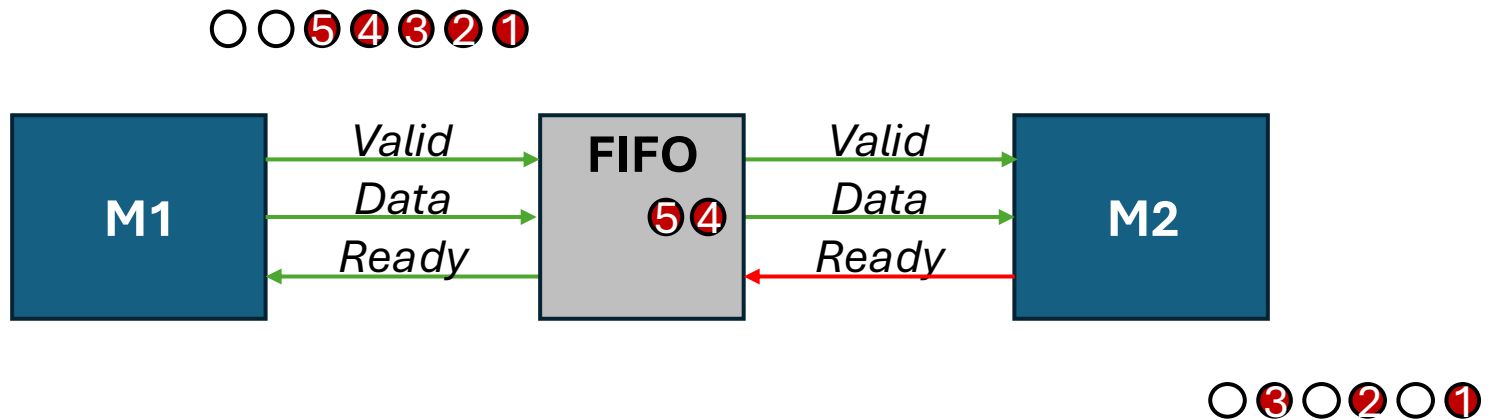


# FIFO-Based Design

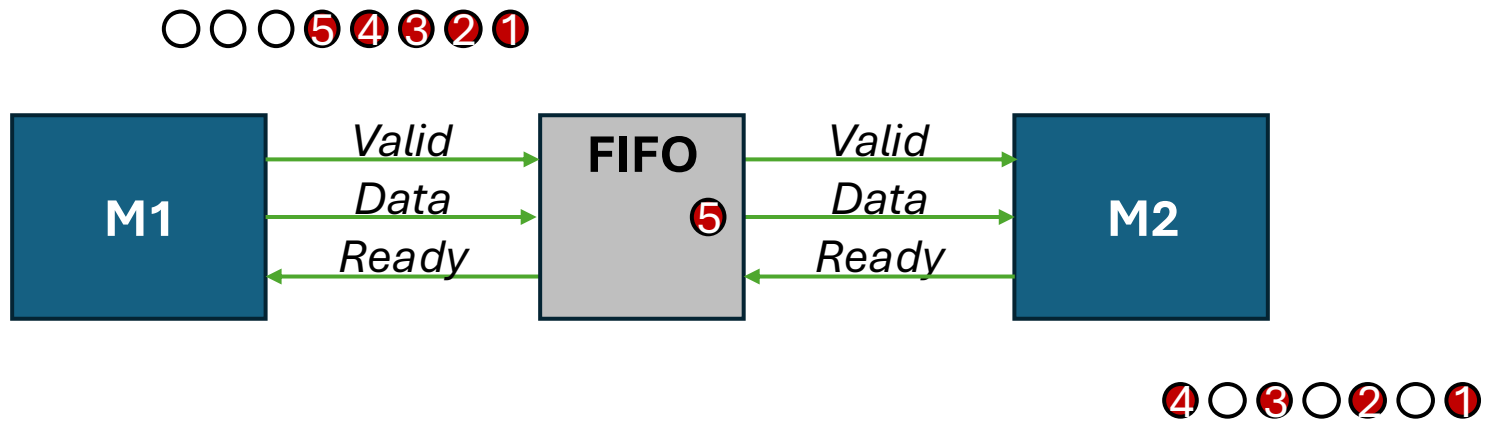

# FIFO-Based Design

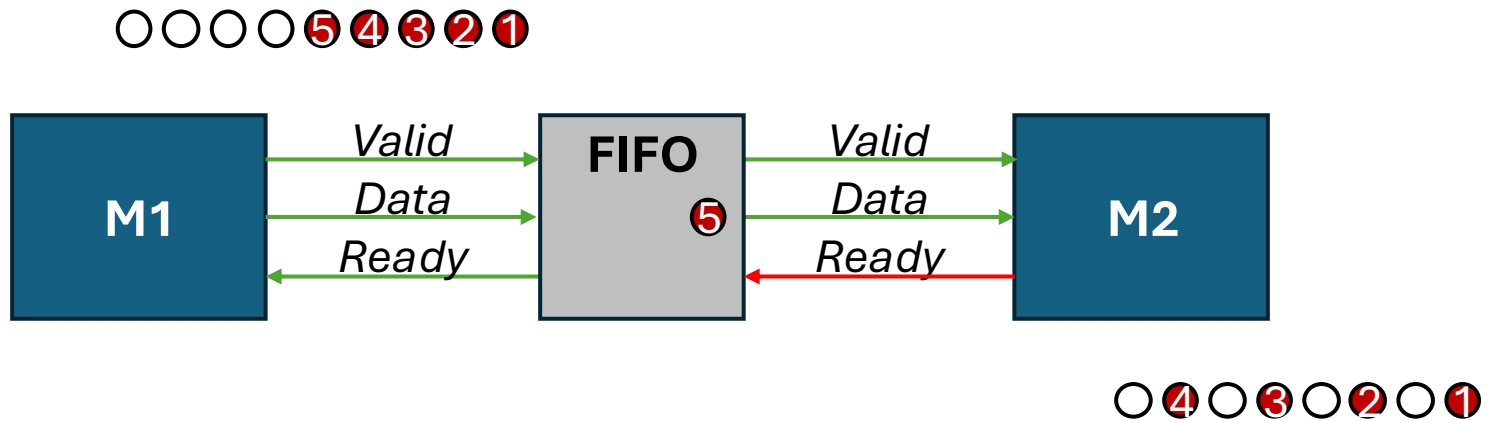


# FIFO-Based Design

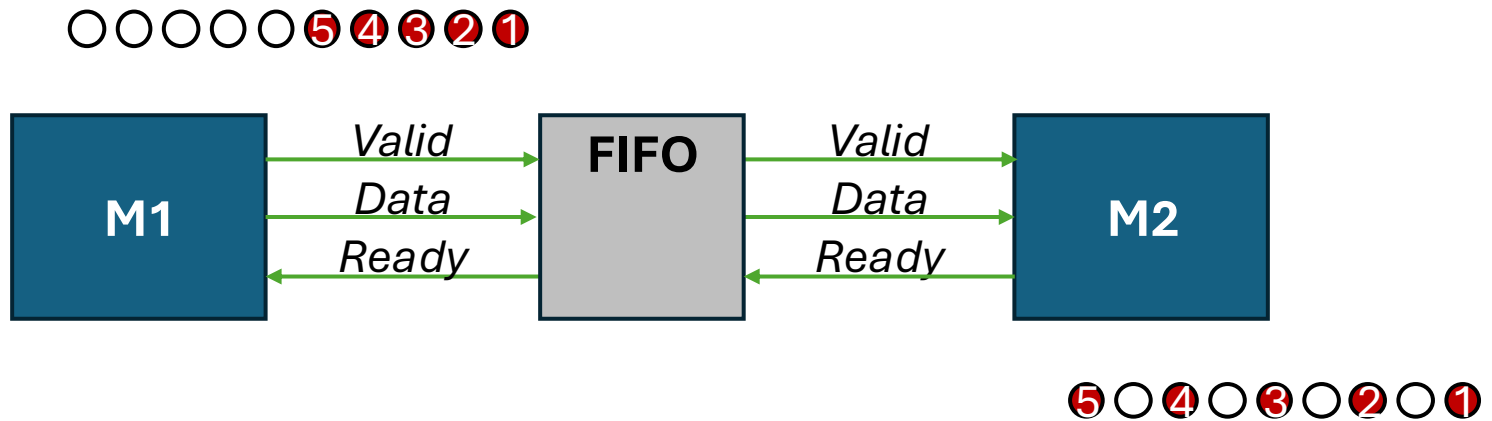

# FIFO-Based Design

... 5 4 3 2 1 ○ ○ ○ ○ ○ ○ 5 4 3 2 1

 


... ○ 2 ○ 1 ○ ○ 5 ○ 4 ○ 3 ○ 2 ○ 1
 
# FIFO-Based Design

*M1 in isolation*



... 5 4 3 2 1 followed by five empty circles, then 5 4 3 2 1



... followed by five empty circles, then 5 4 3 2 1




*M2 in isolation*
 
# FIFO-Based Design

*M1 in isolation*



*M1 & M2 don't affect each other  
and full throughput is maintained  
because of the elasticity  
provided by the FIFO in-between*



*M2 in isolation*

# FIFO Implementation (Vanilla Interface)





# FIFO Implementation (Vanilla Interface)

```
module fifo # (
```

```
) (
```

```
);
```

```
endmodule
```



# FIFO Implementation (Vanilla Interface)

[illegible]

endmodule



# FIFO Implementation (Vanilla Interface)

```
module fifo # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512,  
    parameter ADDRW = $clog2(DEPTH)  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_push,  
    output o_full,  
    output logic [DATAW-1:0] o_data,  
    input  i_pop,  
    output o_empty  
);
```

```
endmodule
```



# FIFO Implementation (Vanilla Interface)

```
module fifo # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512,  
    parameter ADDRW = $clog2(DEPTH)  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_push,  
    output o_full,  
    output logic [DATAW-1:0] o_data,  
    input  i_pop,  
    output o_empty  
);
```

```
logic [DATAW-1:0] mem [0:DEPTH-1];  
logic [ADDRW-1:0] rd_ptr, wr_ptr;
```

```
endmodule
```



# FIFO Implementation (Vanilla Interface)

```
module fifo # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512,  
    parameter ADDRW = $clog2(DEPTH)  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_push,  
    output o_full,  
    output logic [DATAW-1:0] o_data,  
    input  i_pop,  
    output o_empty  
);  
  
logic [DATAW-1:0] mem [0:DEPTH-1];  
logic [ADDRW-1:0] rd_ptr, wr_ptr;
```

```
always_ff @ (posedge clk) begin  
    if (rst) begin  
        rd_ptr <= 'd0;  
        wr_ptr <= 'd0;  
    end else begin  
        if (~o_empty && i_pop) begin  
            o_data <= mem[rd_ptr];  
            rd_ptr <= rd_ptr + 1;  
        end  
  
        if (~o_full && i_push) begin  
            mem[wr_ptr] <= i_data;  
            wr_ptr <= wr_ptr + 1;  
        end  
    end  
end  
  
endmodule
```



# FIFO Implementation (Vanilla Interface)

```
module fifo # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512,  
    parameter ADDRW = $clog2(DEPTH)  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_push,  
    output o_full,  
    output logic [DATAW-1:0] o_data,  
    input  i_pop,  
    output o_empty  
);  
  
logic [DATAW-1:0] mem [0:DEPTH-1];  
logic [ADDRW-1:0] rd_ptr, wr_ptr;
```

```
always_ff @ (posedge clk) begin  
    if (rst) begin  
        rd_ptr <= 'd0;  
        wr_ptr <= 'd0;  
    end else begin  
        if (~o_empty && i_pop) begin  
            o_data <= mem[rd_ptr];  
            rd_ptr <= rd_ptr + 1;  
        end  
  
        if (~o_full && i_push) begin  
            mem[wr_ptr] <= i_data;  
            wr_ptr <= wr_ptr + 1;  
        end  
    end  
end  
  
assign o_full = (wr_ptr + 1) == rd_ptr;  
assign o_empty = wr_ptr == rd_ptr;  
  
endmodule
```



# FIFO Implementation (Ready-Valid Interface)

```
module fifo_ready_valid # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_valid,  
    output o_ready,  
    output logic [DATAW-1:0] o_data,  
    output o_valid,  
    input  i_ready  
);  
  
logic fifo_full, fifo_empty, fifo_push, fifo_pop;
```

```
fifo # (  
    .DATAW(DATAW),  
    .DEPTH(DEPTH)  
) fifo_inst (  
    .clk(clk),  
    .rst(rst),  
    .i_data(i_data),  
    .i_push(fifo_push),  
    .o_full(fifo_full),  
    .o_data(o_data),  
    .i_pop(fifo_pop),  
    .o_empty(fifo_empty)  
);  
  
assign fifo_push = i_valid && o_ready;  
assign fifo_pop  = o_valid && i_ready;  
assign o_ready  = ~fifo_full;  
assign o_valid  = ~fifo_empty;  
  
endmodule
```




# Design Considerations




- FIFO depth is a key design choice ...
  - A very shallow FIFO would backpressure frequently affecting overall throughput negatively
  - A very deep FIFO is more expensive in terms of silicon area footprint
  - **Goal:** minimize FIFO size and provide enough elasticity to maintain full throughput




# Design Considerations

 

 
- FIFO depth is a key design choice ...
  - A very shallow FIFO would backpressure frequently affecting overall throughput negatively
  - A very deep FIFO is more expensive in terms of silicon area footprint
  - **Goal:** minimize FIFO size and provide enough elasticity to maintain full throughput
- FIFOs have to be carefully sized to avoid deadlocks!



# Design Considerations

 


 - FIFO depth is a key design choice ...
  - A very shallow FIFO would backpressure frequently affecting overall throughput negatively
  - A very deep FIFO is more expensive in terms of silicon area footprint
  - **Goal:** minimize FIFO size and provide enough elasticity to maintain full throughput
- FIFOs have to be carefully sized to avoid deadlocks!




*If this FIFO gets full, M1 will be stalled.  
If this happens before M2 gets enough data elements from M1 to produce  
outputs, the design will deadlock!*
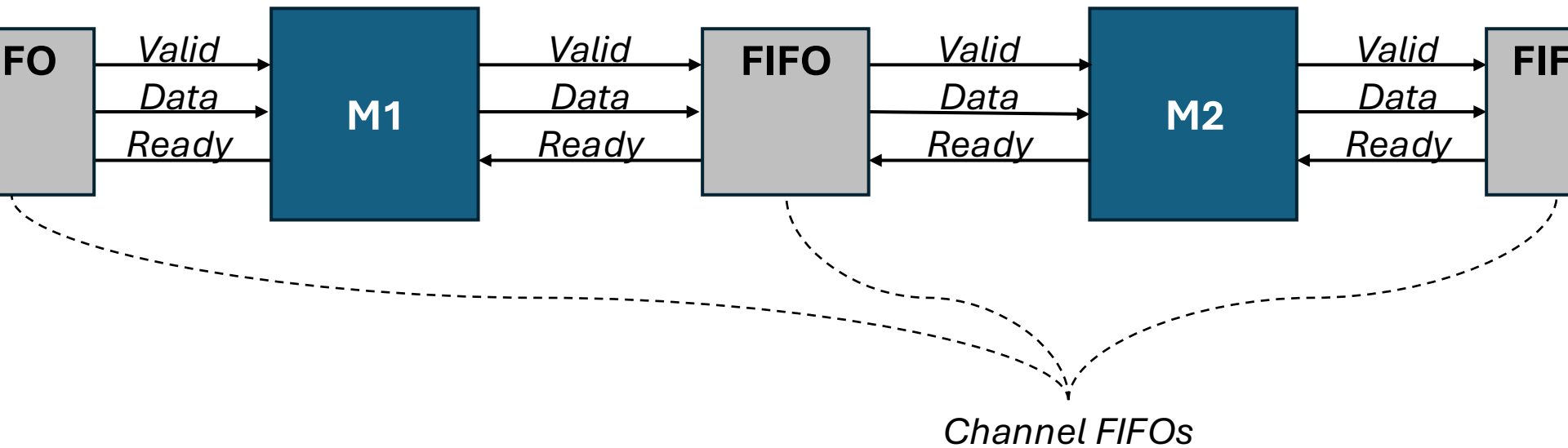
# Coming Full Circle: FIFOs & LI Channels



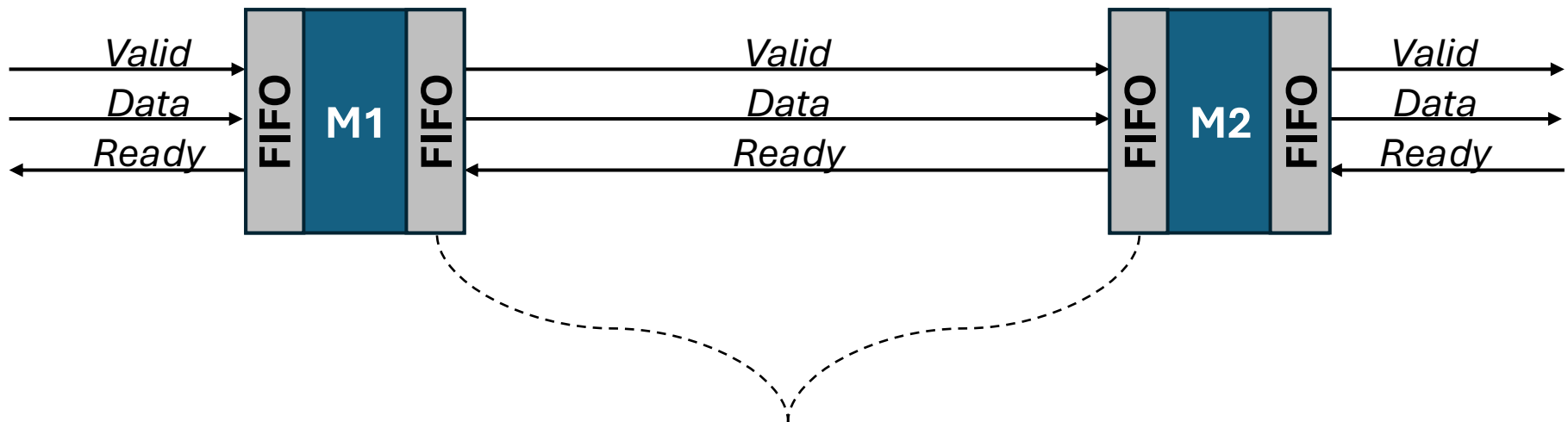
# Coming Full Circle: FIFOs & LI Channels



*Can split channel FIFOs such that each of the modules has FIFOs on its inputs and outputs*

***Depths of split FIFOs combined = Depth of channel FIFO  
FIFO control logic replicated (not very expensive)***

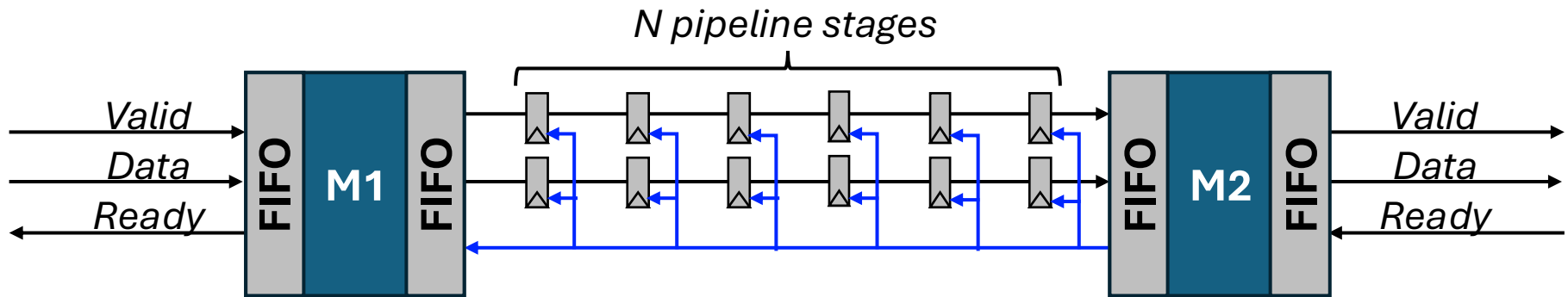
# Coming Full Circle: FIFOs & LI Channels



*If we want to pipeline the latency-insensitive channel to optimize timing, ready signal has to stay combinational to ...*

- (1) Freeze the pipeline*
- (2) Stall the sender module*
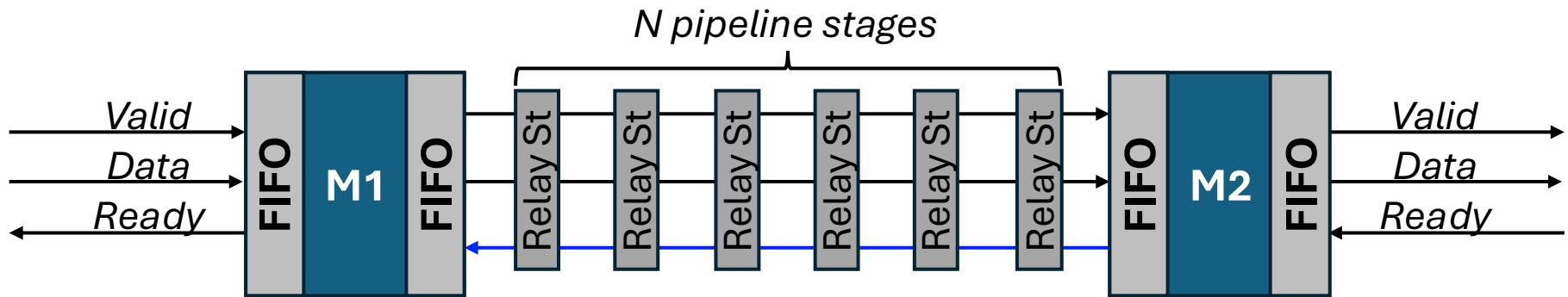
# Coming Full Circle: FIFOs & LI Channels



*If we want to pipeline the latency-insensitive channel to optimize timing, ready signal has to stay combinational to ...*


- (1) Freeze the pipeline*
- (2) Stall the sender module*

*Or use relay stations instead of simple registers*

**→ higher cost (2x the registers + control FSM per stage)**
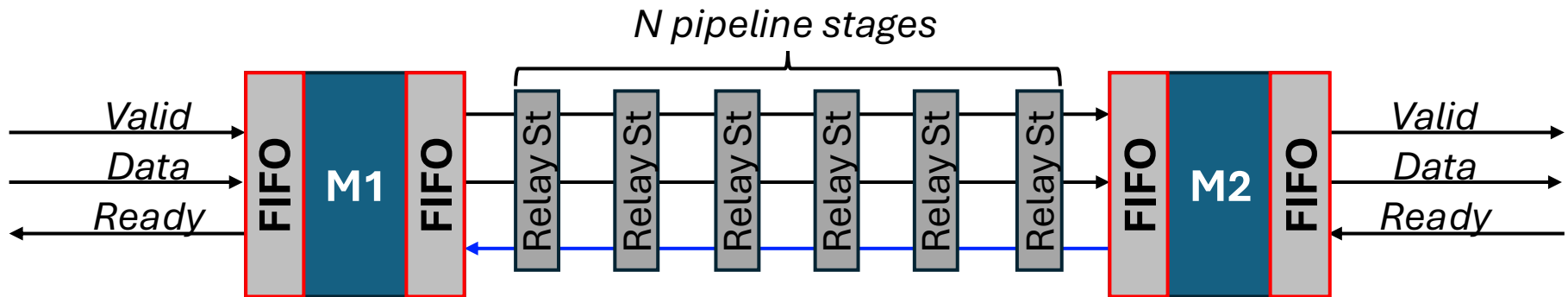
# Coming Full Circle: FIFOs & LI Channels

*These FIFOs can provide a different solution!*




*If we want to pipeline the latency-insensitive channel to optimize timing, ready signal had to stay combinational to ...*

- (1) Freeze the pipeline*
- (2) Stall the sender module*

*Or use relay stations instead of simple registers*


*→ higher cost (2x the registers + control FSM per stage)*
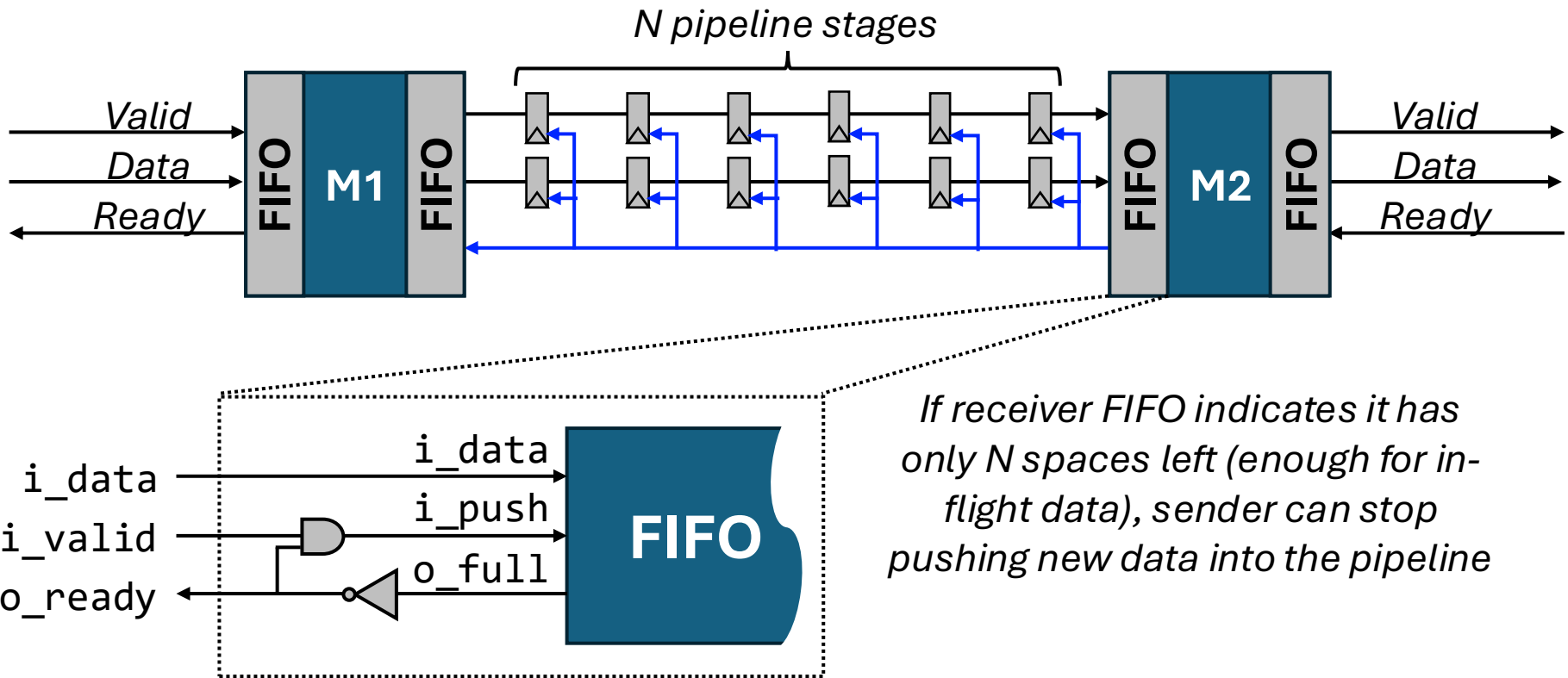
# Coming Full Circle: FIFOs & LI Channels






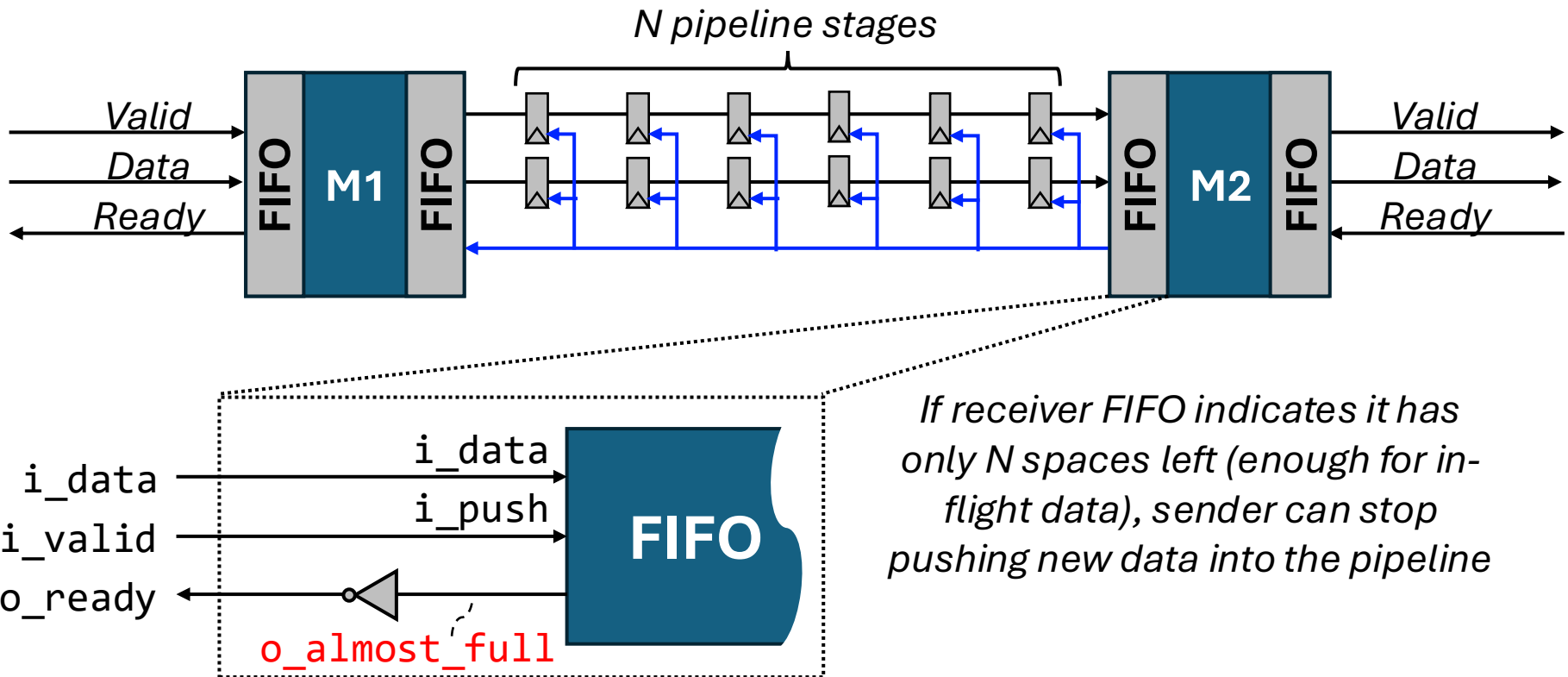
# Coming Full Circle: FIFOs & LI Channels



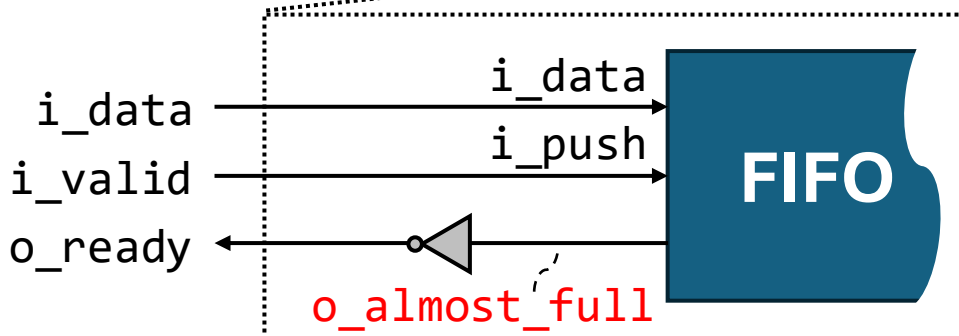 
# Coming Full Circle: FIFOs & LI Channels




*If receiver FIFO indicates it has only N spaces left (enough for in-flight data), sender can stop pushing new data into the pipeline*  
**→ No need to freeze the pipeline – let it drain!**
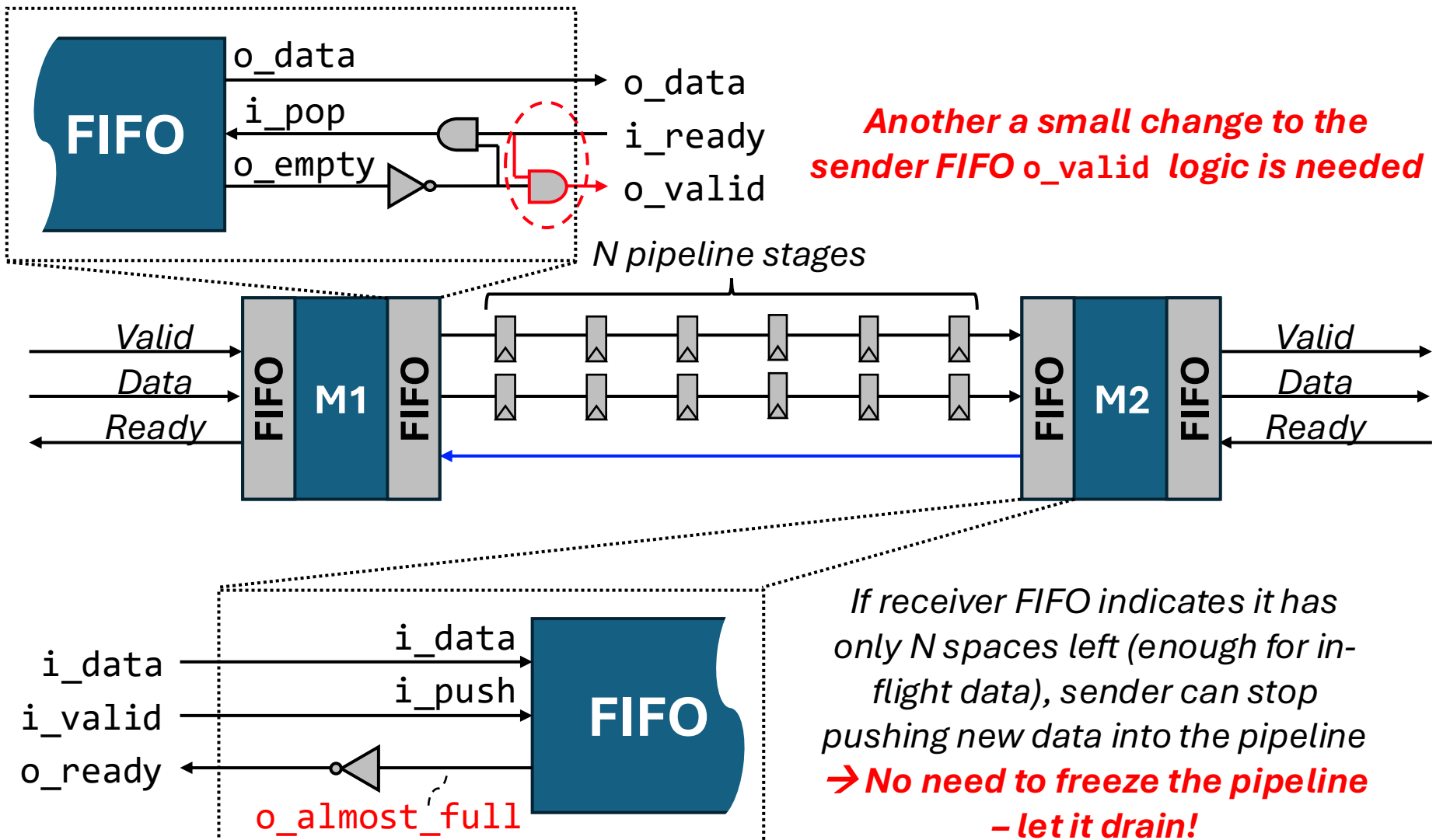
# Coming Full Circle: FIFOs & LI Channels



 
# Coming Full Circle: FIFOs & LI Channels



*Now if we pipeline the ready signal, it takes another  $N$  cycles to reach the sender*

 
# Coming Full Circle: FIFOs & LI Channels



Now if we pipeline the ready signal, it takes another  $N$  cycles to reach the sender

→ **If receiver FIFO indicates it is almost full when it has  $2N$  spaces left, works fine!**
 
# Coming Full Circle: FIFOs & LI Channels



Now if we pipeline the ready signal, it takes another  $N$  cycles to reach the sender

→ If receiver FIFO indicates it is almost full when it has  $2N$  spaces left, works fine!

There is one subtle catch ... Any idea?



# FIFO Implementation with almost\_full Status

```
module fifo # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512,  
    parameter ADDRW = $clog2(DEPTH)  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_push,  
    output o_full,  
    output logic [DATAW-1:0] o_data,  
    input  i_pop,  
    output o_empty  
);  
  
logic [DATAW-1:0] mem [0:DEPTH-1];  
logic [ADDRW-1:0] rd_ptr, wr_ptr;
```

```
always_ff @ (posedge clk) begin  
    if (rst) begin  
        rd_ptr <= 'd0;  
        wr_ptr <= 'd0;  
    end else begin  
        if (~o_empty && i_pop) begin  
            o_data <= mem[rd_ptr];  
            rd_ptr <= rd_ptr + 1;  
        end  
  
        if (~o_full && i_push) begin  
            mem[wr_ptr] <= i_data;  
            wr_ptr <= wr_ptr + 1;  
        end  
    end  
end  
  
assign o_full = (wr_ptr + 1) == rd_ptr;  
assign o_empty = wr_ptr == rd_ptr;  
  
endmodule
```

***What needs to change in the FIFO  
implementation to support almost\_full?***



# FIFO Implementation with almost\_full Status

```
module fifo_ready_valid # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_valid,  
    output o_ready,  
    output logic [DATAW-1:0] o_data,  
    output logic o_valid,  
    input  i_ready  
);  
  
logic fifo_full, fifo_empty, fifo_push, fifo_pop;
```

```
    fifo # (  
        .DATAW(DATAW),  
        .DEPTH(DEPTH)  
    ) fifo_inst (  
        .clk(clk),  
        .rst(rst),  
        .i_data(i_data),  
        .i_push(fifo_push),  
        .o_full(fifo_full),  
        .o_data(o_data),  
        .i_pop(fifo_pop),  
        .o_empty(fifo_empty)  
    );  
  
    assign fifo_push = i_valid && o_ready;  
    assign fifo_pop = o_valid && i_ready;  
    assign o_ready = ~fifo_full;  
    assign o_valid = ~fifo_empty;  
  
endmodule
```




# FIFO Implementation with almost\_full Status

```
module fifo_ready_valid # (  
    parameter DATAW = 32,  
    parameter DEPTH = 512,  
    parameter ALMOST_FULL_DEPTH = DEPTH - 2  
)(  
    input  clk,  
    input  rst,  
    input  [DATAW-1:0] i_data,  
    input  i_valid,  
    output o_ready,  
    output logic [DATAW-1:0] o_data,  
    output logic o_valid,  
    input  i_ready  
);  
  
logic fifo_full, fifo_empty, fifo_push, fifo_pop;  
logic fifo_almost_full;
```


```
fifo # (  
    .DATAW(DATAW),  
    .DEPTH(DEPTH),  
    .ALMOST_FULL_DEPTH(ALMOST_FULL_DEPTH)  
) fifo_inst (  
    .clk(clk),  
    .rst(rst),  
    .i_data(i_data),  
    .i_push(fifo_push),  
    .o_full(fifo_full),  
    .o_almost_full(fifo_almost_full),  
    .o_data(o_data),  
    .i_pop(fifo_pop),  
    .o_empty(fifo_empty)  
);  
  
assign fifo_push = i_valid;  
assign fifo_pop = o_valid && i_ready;  
assign o_ready = ~fifo_almost_full;  
assign o_valid = ~fifo_empty && i_ready;  
  
endmodule
```
 
# Data Width Adaptation

- In many cases, sender/receiver modules produce/consume data words that have different bitwidths



 
*M1 produces a 1024-bit data word every other cycle*



*M2 can consume a 512-bit data word every cycle*

 
# Data Width Adaptation

- In many cases, sender/receiver modules produce/consume data words that have different bitwidths
- An asymmetric FIFO can be used to perform width adaptation


 
# Data Width Adaptation

- In many cases, sender/receiver modules produce/consume data words that have different bitwidths
- An asymmetric FIFO can be used to perform width adaptation



*M1 produces a 1024-bit data word every other cycle*

*M2 can consume a 512-bit data word every cycle*

- An asymmetric FIFO has different data bitwidth for the push and pop interfaces (usually integer multiples of each other)
- Can be implemented using multiple narrower FIFOs
  - **Wide to Narrow Conversion:** Push in parallel and pop sequentially
  - **Narrow to Wide Conversion:** Push sequentially and pop in parallel


# Asym. FIFO Implementation (Wide to Narrow)

```
module asym_fifo # (  
    parameter IDATAW = 32,  
    parameter ODATAW = 8,  
    parameter DEPTH = 512,  
    parameter NUM_FIFOS = IDATAW / ODATAW  
)(  
    input clk,  
    input rst,  
    input [IDATAW-1:0] i_data,  
    input i_valid,  
    output o_ready,  
    output logic [ODATAW-1:0] o_data,  
    output o_valid,  
    input i_ready  
);  
  
logic fifo_full, fifo_almost_full, fifo_empty;  
logic fifo_push, fifo_pop;  
logic [IDATAW-1:0] fifo_odata;  
logic [$clog2(NUM_FIFOS)-1:0] cntr;  
  
fifo # (  
    .DATAW(IDATAW),  
    .DEPTH(DEPTH)  
) fifo_inst (  
    .clk(clk),  
    .rst(rst),  
    .i_data(i_data),  
    .i_push(fifo_push),  
    .o_full(fifo_full),  
    .o_almost_full(fifo_almost_full),  
    .o_data(fifo_odata),  
    .i_pop(fifo_pop),  
    .o_empty(fifo_empty)  
);
```

```
always_ff @ (posedge clk) begin  
    if (rst) begin  
        cntr <= 0;  
    end else begin  
        if (o_valid && i_ready) begin  
            if (cntr == NUM_FIFOS-1) cntr <= 0;  
            else cntr <= cntr + 1;  
        end  
    end  
end  
  
always_comb begin  
    o_data = fifo_odata[cntr * ODATAW +: ODATAW];  
end  
  
assign fifo_push = i_valid && o_ready;  
assign fifo_pop = o_valid && i_ready  
                && (cntr==NUM_FIFOS-1);  
assign o_ready = ~fifo_almost_full;  
assign o_valid = ~fifo_empty;  
  
endmodule
```


# FIFO-Based Design in Practice

- In network-on-chip (NoC) router ports

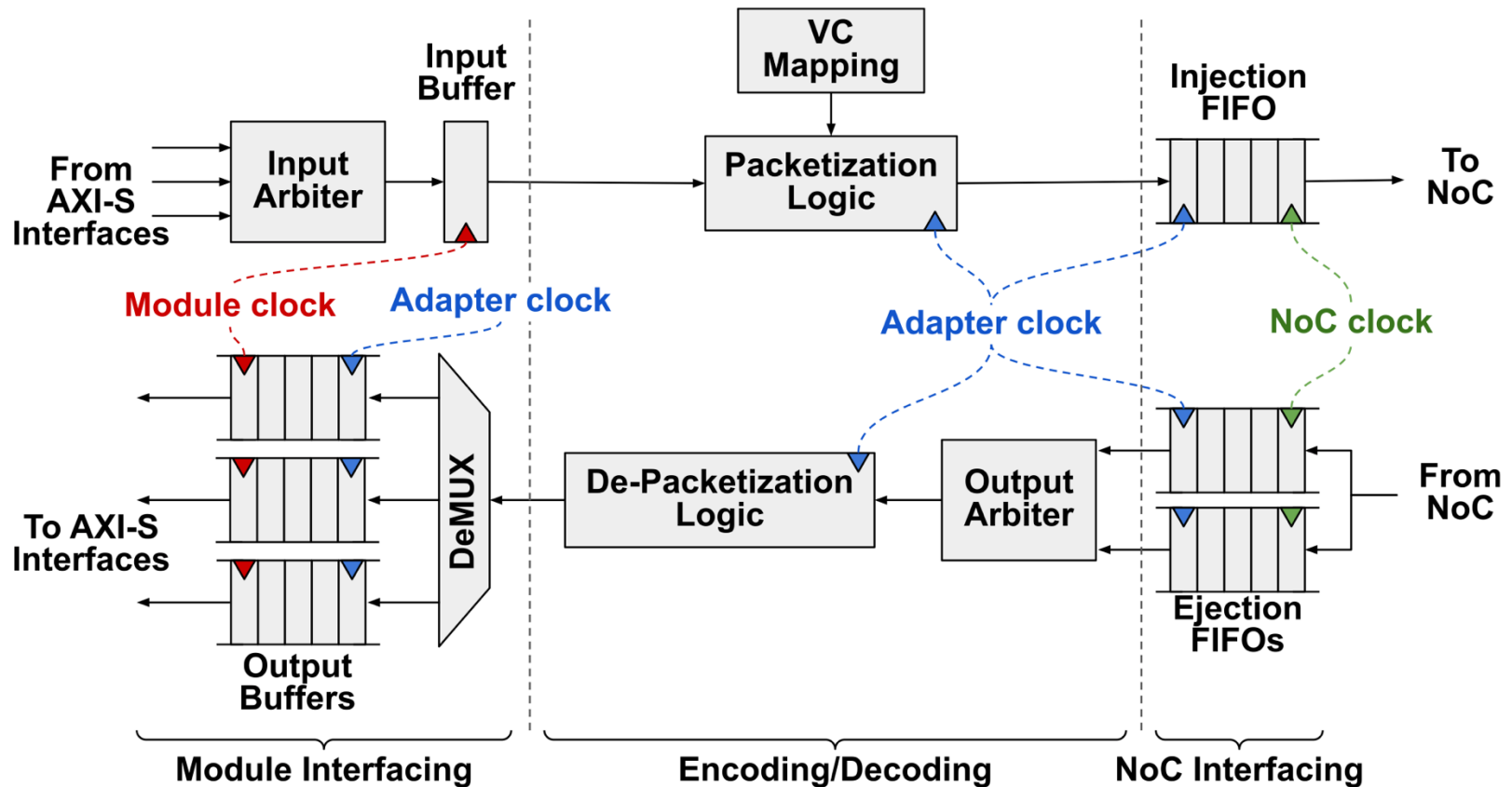

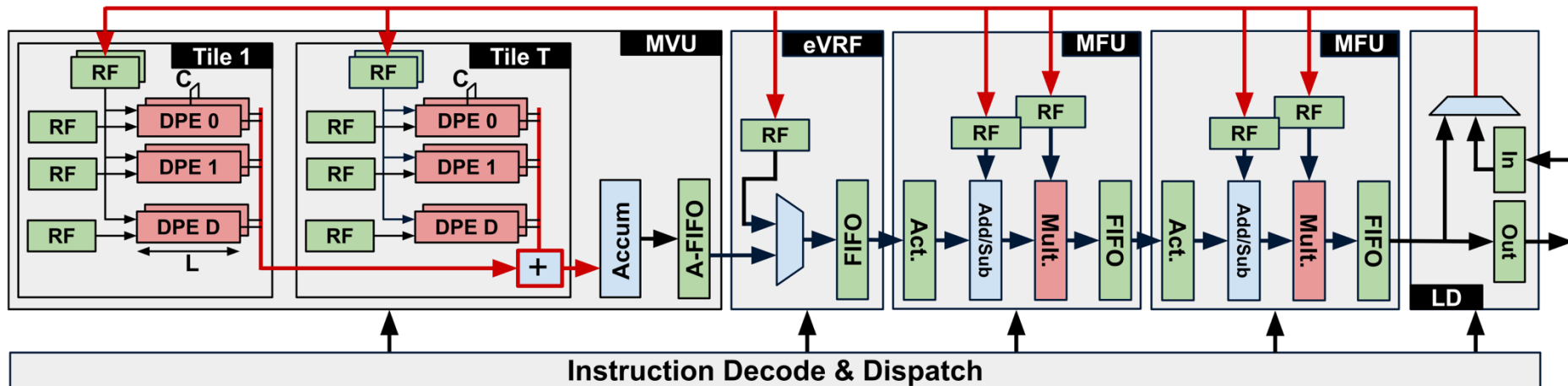
# FIFO-Based Design in Practice

- In many accelerator designs (e.g., Microsoft Brainwave)


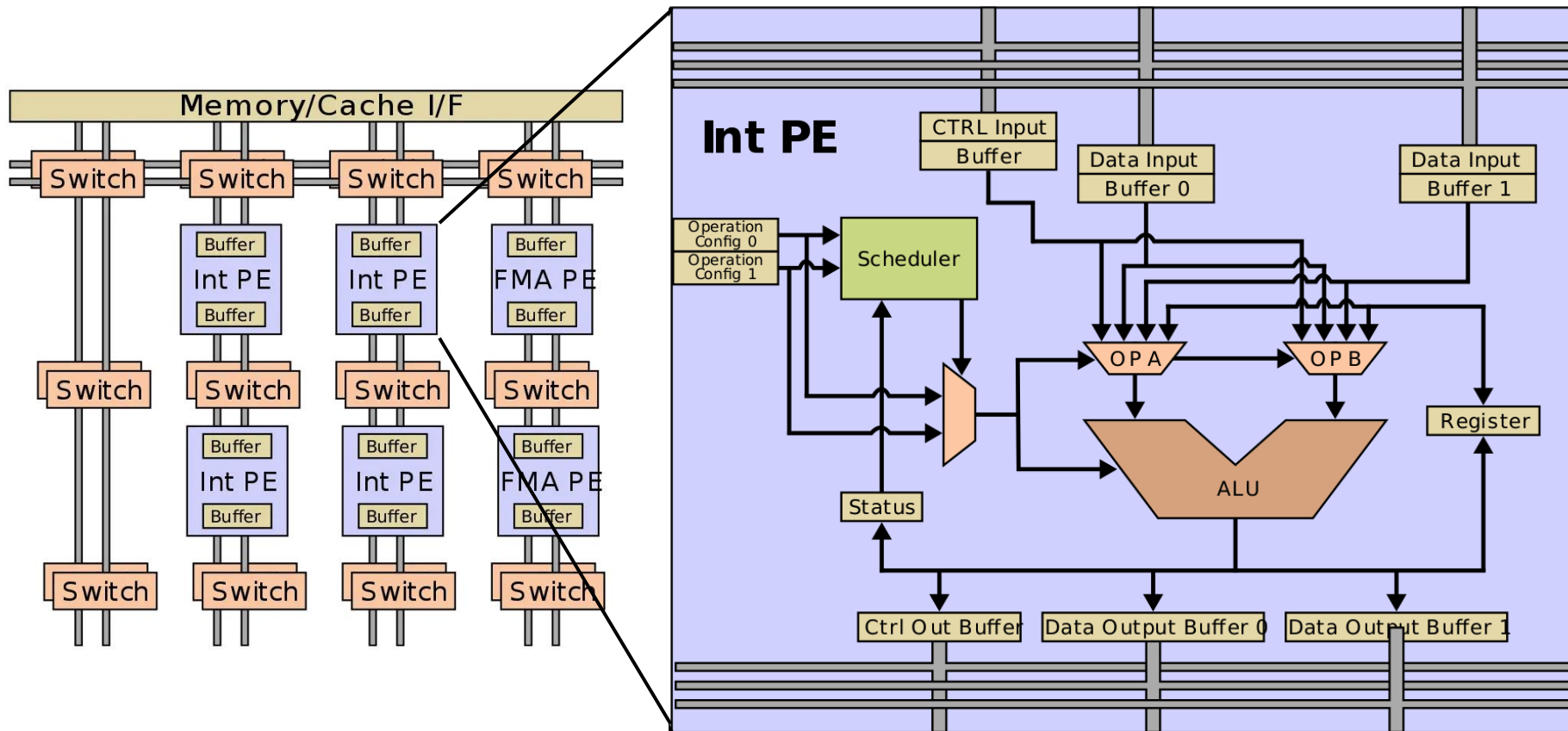
# FIFO-Based Design in Practice

- Dataflow architectures (e.g., Intel Configurable Spatial Array)



Source: [https://en.wikichip.org/wiki/intel/configurable\\_spatial\\_accelerator](https://en.wikichip.org/wiki/intel/configurable_spatial_accelerator)



# FIFO-Based Design in Practice

- SambaNova architecture

