

ECE 327/627

Digital Hardware Systems

Lecture 3: SystemVerilog Basics II

Andrew Boutros

andrew.boutros@uwaterloo.ca

Some Logistics

- Lab group registration is open on LEARN
 - Connect > Groups > View Available Groups
 - Deadline is **January 16 @ 11:59 pm**
- Lab 1 is released
 - Worth **5%** of the total course grade for ECE 327 students
 - Worth **3%** of the total course grade for ECE 627 students
 - Deadline **January 23 @ 11:59 pm**
- Tutorial session will be held this week
 - Wednesday 12:30 - 1:20 pm @ PSE-4053
 - More SystemVerilog examples

In Previous Lecture ...

- SystemVerilog basics
 - Typical module skeleton
 - Ports
 - Continuous assignment
 - Signals (`logic`)
 - Module parameterization
 - Hierarchical instantiation
 - Procedural blocks
 - `initial` – behavior happens only once at beginning of time
 - `always_comb` – behavior happens every time a RHS signal changes
 - `always_ff` – behavior happens every pos/neg clock edge
 - Blocking (`=`) vs. non-blocking (`<=`) assignments
 - Blocking → “sequential” description of the behavior
 - Non-blocking → “concurrent” description of the behavior

One More Example: Blocking vs. Non-Blocking

```
module poly1 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 = a * x;  
    y1 = y0 + b;  
    y2 = y1 * x;  
    y3 = y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```


```
module poly2 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 <= a * x;  
    y1 <= y0 + b;  
    y2 <= y1 * x;  
    y3 <= y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```

One More Example: Blocking vs. Non-Blocking

```
module poly1 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 = a * x;  
    y1 = y0 + b;  
    y2 = y1 * x;  
    y3 = y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```

One More Example: Blocking vs. Non-Blocking
 
```
module poly1 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 = a * x;  
    y1 = y0 + b;  
    y2 = y1 * x;  
    y3 = y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```



Blocking assignments mean that this behavior is described sequentially. You can substitute dependencies:

$$y3 = (((a * x) + b) * x) + c;$$

y0


y1

y2

One More Example: Blocking vs. Non-Blocking

```
module poly1 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 = a * x;  
    y1 = y0 + b;  
    y2 = y1 * x;  
    y3 = y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```
 
`always_ff` means that final results of the procedural block are registered



Blocking assignments mean that this behavior is described sequentially. You can substitute dependencies:

$$y3 = (((a * x) + b) * x) + c;$$

y0

y1

y2


One More Example: Blocking vs. Non-Blocking

```
module poly1 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 = a * x;  
    y1 = y0 + b;  
    y2 = y1 * x;  
    y3 = y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```



What if we change
always_ff to always_comb?

 always_ff means that final results of
the procedural block are registered



Blocking assignments mean that this
behavior is described sequentially. You can
substitute dependencies:


$$y3 = (((a * x) + b) * x) + c;$$

y0
y1
y2

One More Example: Blocking vs. Non-Blocking

```
module poly2 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
    logic [15:0] y0;  
    logic [15:0] y1;  
    logic [23:0] y2;  
    logic [23:0] y3;  
  
    always_ff @ (posedge clk) begin  
        y0 <= a * x;  
        y1 <= y0 + b;  
        y2 <= y1 * x;  
        y3 <= y2 + c;  
    end  
  
    assign y = y3;  
  
endmodule
```

 
One More Example: Blocking vs. Non-Blocking



Concurrent non-blocking assignments
(i.e., The LHS of all non-blocking assignments in
an `always_ff` translate to registers)

```
module poly2 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
logic [15:0] y0;  
logic [15:0] y1;  
logic [23:0] y2;  
logic [23:0] y3;  
  
always_ff @ (posedge clk) begin  
    y0 <= a * x;  
    y1 <= y0 + b;  
    y2 <= y1 * x;  
    y3 <= y2 + c;  
end  
  
assign y = y3;  
  
endmodule
```

 One More Example: Blocking vs. Non-Blocking




Concurrent non-blocking assignments
(i.e., The LHS of all non-blocking assignments in
an `always_ff` translate to registers)



**Does this work correctly if the
inputs change every clock cycle?**

```
module poly2 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
    logic [15:0] y0;  
    logic [15:0] y1;  
    logic [23:0] y2;  
    logic [23:0] y3;  
  
    always_ff @ (posedge clk) begin  
        y0 <= a * x;  
        y1 <= y0 + b;  
        y2 <= y1 * x;  
        y3 <= y2 + c;  
    end  
  
    assign y = y3;  
  
endmodule
```

 One More Example: Blocking vs. Non-Blocking



Concurrent non-blocking assignments
(i.e., The LHS of all non-blocking assignments in
an `always_ff` translate to registers)



**Does this work correctly if the
inputs change every clock cycle?**

*More on this in the pipeline lecture
later in the course*


```
module poly2 (  
    input  clk,  
    input  [7:0] a,  
    input  [7:0] b,  
    input  [7:0] c,  
    input  [7:0] x,  
    output [23:0] y  
);  
  
    logic [15:0] y0;  
    logic [15:0] y1;  
    logic [23:0] y2;  
    logic [23:0] y3;  
  
    always_ff @ (posedge clk) begin  
        y0 <= a * x;  
        y1 <= y0 + b;  
        y2 <= y1 * x;  
        y3 <= y2 + c;  
    end  
  
    assign y = y3;  
  
endmodule
```

Recommended Best Practices for `<=` vs. `=`

- The language allows using blocking (`=`) or non-blocking (`<=`) assignments to describe sequential or combinational logic
- Can get really confusing and cause unintentional bugs if you don't know exactly what you are doing!
- Best practices and & guidelines to minimize sources of errors
 - Use non-blocking (`<=`) assignments only to describe sequential (i.e., clocked) logic in `always_ff` blocks
 - Use blocking (`=`) assignments only to describe combinational logic in `always_comb` blocks

Conditions in Always Blocks

 - In always blocks, condition branches instantiate distinct circuits + multiplexer
- The multiplexer select line is the condition logic
- Circuits corresponding to all conditions process inputs, but only one output is selected
 - Compare to software branches?



```
module add_mult (
    input  signed [7:0] a,
    input  signed [7:0] b,
    input  op,
    output signed [15:0] y
);

logic signed [15:0] res;

always_comb begin
    if (!op) begin
        res = a + b;
    end else begin
        res = a * b;
    end
end

assign y = res;

endmodule
```

=

```
module add_mult (...);


assign y = (!op)? a+b : a*b;

endmodule
```

Incomplete Conditions

- If a conditional statement is incomplete (missing else), this generates a feedback from the mux output to its input
 - In combinational circuit → latch
 - Initial value problem
 - Need to be very carefully designed to avoid metastability (feedback delay for the value to stabilize before select line changes)

 
```
module add_mult (  
    input  signed [7:0] a,  
    input  signed [7:0] b,  
    input  op,  
    output signed [15:0] y  
);  
  
logic signed [15:0] res;  
  
always_comb begin  
    if (!op) begin  
        res = a + b;  
    end  
end  
  
assign y = res;  
  
endmodule
```



Incomplete Conditions

- If a conditional statement is incomplete (missing else), this generates a feedback from the mux output to its input
 - In combinational circuit → latch
 - Initial value problem
 - Need to be very carefully designed to avoid metastability (feedback delay for the value to stabilize before select line changes)
 - In sequential circuit → feedback loop broken by a register stage
 
```
module add_mult (  
    input clk,  
    input signed [7:0] a,  
    input signed [7:0] b,  
    input op,  
    output signed [15:0] y  
);  
logic signed [15:0] res;  
  
always_ff @ (posedge clk) begin  
    if (!op) begin  
        res = a + b;  
    end  
end  
  
assign y = res;  
  
endmodule
```




Non-mutually Exclusive Conditions

```
...  
always_comb begin  
    if (x > 1000) begin  
        y = c;  
    end else if (x > 100) begin  
        y = b;  
    end else if (x > 10) begin  
        y = a;  
    end else if (x > 1) begin  
        y = x;  
    end else begin  
        y = 0;  
    end  
end  
...
```

Highest priority (points to the first `if` condition)

Lowest priority (points to the final `else` condition)

 
- If-else conditions can be non-mutually exclusive
 - e.g., $x = 1001$ satisfies all conditions)
- In this case, the order defines condition priority



Mutually Exclusive Conditions

```
...  
always_comb begin  
    case(x)  
        8'h00: begin  
            y = c;  
        end  
        8'h01: begin  
            y = b;  
        end  
        8'h02: begin  
            y = a;  
        end  
        8'h03: begin  
            y = x;  
        end  
        default: begin  
            y = 0;  
        end  
    endcase  
end  
...
```

 
- Can use if-else conditions or a case statement
- No notion of condition priority



Mutually Exclusive Conditions

```
...  
always_comb begin  
    case(x)  
        8'h00: begin  
            y = c;  
        end  
        8'h01: begin  
            y = b;  
        end  
        8'h02: begin  
            y = a;  
        end  
        8'h03: begin  
            y = x;  
        end  
    endcase  
end  
...
```

 
- Can use if-else conditions or a case statement
- No notion of condition priority
- Removing the **default** case infers a latch (same as missing else)



Default Condition in If-Else

```
...  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        x <= 0;  
    end else begin  
        x <= 4;  
        if (x < 4) begin  
            x <= x + 1;  
        end  
    end  
end  
...
```

 - In procedural blocks, the last non-blocking assignment of a signal wins!
 - Previous assignments are ignored
- This can be used to define a default condition and avoid inferring a feedback loop if there is a no else




Default Condition in If-Else

```
...  
always_ff @ (posedge clk) begin  
    if (rst) begin  
        x <= 0;  
    end else begin  
        if (x < 4) begin  
            x <= x + 1;  
        end  
        x <= 4;  
    end  
end  
...
```




What hardware will be generated if we flip the order?

 - In procedural blocks, the last non-blocking assignment of a signal wins!
 - Previous assignments are ignored
- This can be used to define a default condition and avoid inferring a feedback loop if there is a no else




Vector Summation Example

 

Behavioral description that synthesizes similar hardware to our hierarchical implementation from last lecture

```
module vector_sum (  
    input  clk,  
    input  rst,  
    input  signed [7:0] a [0:3],  
    output signed [31:0] sum  
);  
  
    logic signed [31:0] res;  
  
    always_ff @ (posedge clk) begin  
        if (rst) begin  
            res <= 0;  
        end else if  
            res <= a[0] + a[1] + a[2] + a[3];  
        end  
    end  
  
    assign sum = res;  
  
endmodule
```


Vector Summation Example

 

What if vector a had 100 elements?

```
module vector_sum (  
    input  clk,  
    input  rst,  
    input  signed [7:0] a [0:99],  
    output signed [31:0] sum  
);  
  
    logic signed [31:0] res;  
  
    always_ff @ (posedge clk) begin  
        if (rst) begin  
            res <= 0;  
        end else if  
            res <= a[0] + a[1] + ... + a[99];  
        end  
    end  
  
    assign sum = res;  
  
endmodule
```

Vector Summation Example

 

What if vector a had 100 elements?

Or what if I want to implement a parameterizable module?

```
module vector_sum #(
    parameter N = 128
)(
    input  clk,
    input  rst,
    input  signed [7:0] a [0:N-1],
    output signed [31:0] sum
);

    logic signed [31:0] res;

    always_ff @ (posedge clk) begin
        if (rst) begin
            res <= 0;
        end else if
            res <= ???
        end
    end

    assign sum = res;

endmodule
```


For Loops in Procedural Blocks

- For loops can be used to describe circuit behavior in procedural blocks
- Loop iterator variable is defined as an **integer**
 - This is not synthesized in hardware – just to describe the behavior of the circuit

```
module vector_sum #(
    parameter N = 128
)(
    input  clk,
    input  rst,
    input  signed [7:0] a [0:N-1],
    output signed [31:0] sum
);

    logic signed [31:0] res;
    integer i;

    always_ff @ (posedge clk) begin
        if (rst) begin
            res = 0;
        end else begin
            res = 0;
            for (i = 0; i < N; i = i + 1) begin
                res = res + a[i];
            end
        end
    end

    assign sum = res;

endmodule
```

For Loops in Procedural Blocks

- For loops can be used to describe circuit behavior in procedural blocks
- Loop iterator variable is defined as an **integer**
 - This is not synthesized in hardware – just to describe the behavior of the circuit
- This synthesizes into a large adder tree to sum up the elements of the vector
 - Remember that the loop is describing the behavior – **There are no iterations in the synthesized hardware**

```
module vector_sum #(
    parameter N = 128
)(
    input  clk,
    input  rst,
    input  signed [7:0] a [0:N-1],
    output signed [31:0] sum
);

    logic signed [31:0] res;
    integer i;

    always_ff @ (posedge clk) begin
        if (rst) begin
            res = 0;
        end else begin
            res = 0;
            for (i = 0; i < N; i = i + 1) begin
                res = res + a[i];
            end
        end
    end

    assign sum = res;

endmodule
```


Generate Blocks

- Circuits can instantiate many replicas of subcomponents
- Generate blocks allow you to instantiate modules in a loop to avoid doing it manually
- Keep in mind ...
 - For loops in procedural blocks → describe the behavior of the module
 - Generate for loops → instantiate sub-modules

```
module adder (  
    input  [7:0] a,  
    input  [7:0] b,  
    output [8:0] out  
);  
assign out = a + b;  
endmodule  
  
/*****/  
  
module vector_add #(  
    parameter N = 128  
)(  
    input  [7:0] a [0:N-1],  
    input  [7:0] b [0:N-1],  
    output [8:0] res [0:N-1]  
);  
  
    genvar i;  
    generate  
    for (i = 0; i < N; i = i + 1)  
    begin: gen_adders  
        adder add_inst(  
            .a(a[i]), .b(b[i]), .out(res[i])  
        );  
    end  
endgenerate  
  
endmodule
```


Implementing Simulation Testbenches

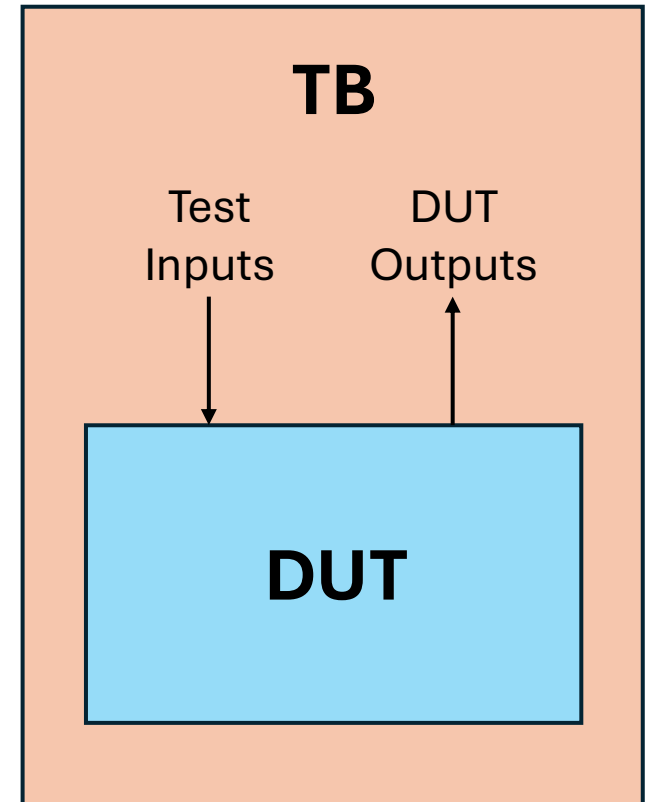- A simulation testbench is a wrapper around the module to be tested (design under test or DUT):
 - Instantiates DUT as a subcomponent
 - Provides test inputs & monitors the DUT outputs
 - (Optional) Compares to reference “golden” outputs to verify correctness



Implementing Simulation Testbenches

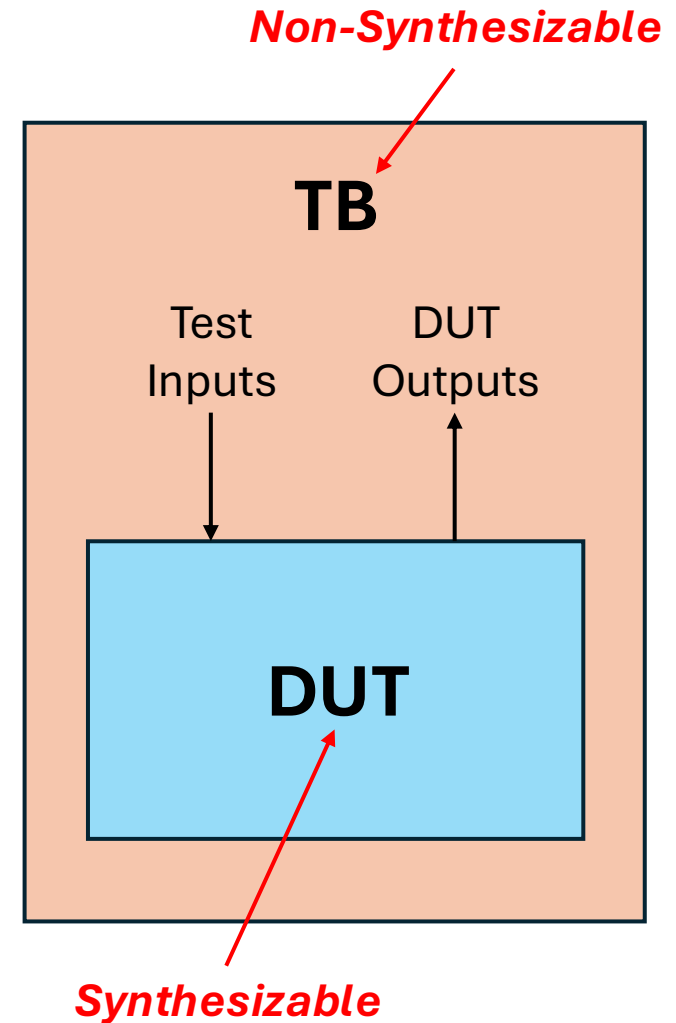- A simulation testbench is a wrapper around the module to be tested (design under test or DUT):
 - Instantiates DUT as a subcomponent
 - Provides test inputs & monitors the DUT outputs
 - (Optional) Compares to reference “golden” outputs to verify correctness
- The testbench is not synthesized to hardware – used to verify & simulate a synthesizable DUT



Simple Testbench Example

``timescale <unit>/<precision>`

- Directive that specifies the time unit and precision used for simulation
 - Delays and simulation time are measured in time unit
 - Delay values are rounded based on the time precision
- Quantities can be 1, 10, or 100
- Units can range from seconds (s) to femtoseconds (fs)

```
`timescale 1ns/1ps

module adder8b_tb ();

    logic [7:0] in1, in2;
    logic [8:0] out;

    adder8b dut (
        .in1(in1),
        .in2(in2),
        .out(out)
    );

    initial begin
        $monitor($time, "ns: in1=%d, in2=%d, out=%d", in1, in2, out);
        in1 = 8'd3; in2 = 8'd2;
        #10 in1 = 8'd10; in2 = 8'd34;
        #10 in1 = 8'd22; in2 = 8'd17;
        #10 in1 = 8'd13; in2 = 8'd85;
        #10 in1 = 8'd74; in2 = 8'd44;
        #10 $stop;
    end

endmodule
```

```
module adder8b (
    input [7:0] in1,
    input [7:0] in2,
    output [8:0] out
);
```

Simple Testbench Example

- A testbench typically has no external inputs or outputs (i.e., no port list)
- Self-contained testbenches
 - Generate test inputs internally and supply them to the DUT
 - Receive DUT outputs (can be investigated by “print” statements or in waveforms)
 - Can compare DUT outputs to reference “golden” solutions

```
`timescale 1ns/1ps

module adder8b_tb ();

    logic [7:0] in1, in2;
    logic [8:0] out;

    adder8b dut (
        .in1(in1),
        .in2(in2),
        .out(out)
    );

    initial begin
        $monitor($time, "ns: in1=%d, in2=%d, out=%d", in1, in2, out);
        in1 = 8'd3; in2 = 8'd2;
        #10 in1 = 8'd10; in2 = 8'd34;
        #10 in1 = 8'd22; in2 = 8'd17;
        #10 in1 = 8'd13; in2 = 8'd85;
        #10 in1 = 8'd74; in2 = 8'd44;
        #10 $stop;
    end

endmodule
```

```
module adder8b (
    input [7:0] in1,
    input [7:0] in2,
    output [8:0] out
);
```

Simple Testbench Example

- Declare signals corresponding to DUT inputs and outputs
- Instantiate DUT and connect its ports to the declared signals

```
`timescale 1ns/1ps

module adder8b_tb ();

    logic [7:0] in1, in2;
    logic [8:0] out;

    adder8b dut (
        .in1(in1),
        .in2(in2),
        .out(out)
    );

    initial begin
        $monitor($time, "ns: in1=%d, in2=%d, out=%d", in1, in2, out);
        in1 = 8'd3; in2 = 8'd2;
        #10 in1 = 8'd10; in2 = 8'd34;
        #10 in1 = 8'd22; in2 = 8'd17;
        #10 in1 = 8'd13; in2 = 8'd85;
        #10 in1 = 8'd74; in2 = 8'd44;
        #10 $stop;
    end

endmodule
```

```
module adder8b (
    input [7:0] in1,
    input [7:0] in2,
    output [8:0] out
);
```


Simple Testbench Example

- Set test input values in a procedural block (e.g., `initial`)

```
`timescale 1ns/1ps

module adder8b_tb ();

    logic [7:0] in1, in2;
    logic [8:0] out;

    adder8b dut (
        .in1(in1),
        .in2(in2),
        .out(out)
    );

    initial begin
        $monitor($time, "ns: in1=%d, in2=%d, out=%d", in1, in2, out);
        in1 = 8'd3; in2 = 8'd2;
        #10 in1 = 8'd10; in2 = 8'd34;
        #10 in1 = 8'd22; in2 = 8'd17;
        #10 in1 = 8'd13; in2 = 8'd85;
        #10 in1 = 8'd74; in2 = 8'd44;
        #10 $stop;
    end

endmodule
```

```
module adder8b (
    input [7:0] in1,
    input [7:0] in2,
    output [8:0] out
);
```

Simple Testbench Example

- Set test input values in a procedural block (e.g., `initial`)
- Use delay statements to specify when to set input signals to certain values
 - Delay statements are in the units specified by timescale directive
 - In this example, `#10` means 10 units of `1ns` → 10ns
 - Delay statements are not synthesizable – only used for modeling and simulation

```
`timescale 1ns/1ps

module adder8b_tb ();

    logic [7:0] in1, in2;
    logic [8:0] out;

    adder8b dut (
        .in1(in1),
        .in2(in2),
        .out(out)
    );

    initial begin
        $monitor($time, "ns: in1=%d, in2=%d, out=%d", in1, in2, out);
        in1 = 8'd3; in2 = 8'd2;
        #10 in1 = 8'd10; in2 = 8'd34;
        #10 in1 = 8'd22; in2 = 8'd17;
        #10 in1 = 8'd13; in2 = 8'd85;
        #10 in1 = 8'd74; in2 = 8'd44;
        #10 $stop;
    end

endmodule
```

```
module adder8b (
    input  [7:0] in1,
    input  [7:0] in2,
    output [8:0] out
);
```

Simple Testbench Example

- Some SystemVerilog system functions can be useful for simulation
 - **\$monitor**: continuously monitors the signals in its argument list and outputs a message when any of their values changes
 - **\$display**: outputs a message at any time (e.g., output simulation time during the execution of a procedural block)
 - **\$time**: outputs the current simulation time
 - **\$stop**: pauses the simulation (analogous to a breakpoint)
 - **\$finish**: terminates simulation

```
`timescale 1ns/1ps

module adder8b_tb ();

    logic [7:0] in1, in2;
    logic [8:0] out;

    adder8b dut (
        .in1(in1),
        .in2(in2),
        .out(out)
    );

    initial begin
        $monitor($time, "ns: in1=%d, in2=%d, out=%d", in1, in2, out);
        in1 = 8'd3; in2 = 8'd2;
        #10 in1 = 8'd10; in2 = 8'd34;
        #10 in1 = 8'd22; in2 = 8'd17;
        #10 in1 = 8'd13; in2 = 8'd85;
        #10 in1 = 8'd74; in2 = 8'd44;
        #10 $stop;
    end

endmodule
```

```
module adder8b (
    input  [7:0] in1,
    input  [7:0] in2,
    output [8:0] out
);
```

Generating a Clock Signal in the Testbench

- When simulating sequential circuits, the testbench needs to generate a periodic clock signal for the DUT
- Clock can be generated in an independent **initial** block
 - Set clock signal initially to 0
 - Use **forever** to repeat a behavior until end of time
 - The repeated behavior is to wait half a clock period & negate the clock signal → 50% duty cycle
- Remember this is generating a clock signal for simulation
 - Does not synthesize hardware that generates a clock

```
`timescale 1ns/1ps

module sequential_module_tb ();

    parameter CLK_PERIOD = 2; // 2ns clock

    // Declare logic signals
    logic clk;
    ...

    sequential_module dut (
        // Connect DUT ports
        .clk(clk),
        ...
    );

    initial begin
        clk = 1'b0;
        forever #(CLK_PERIOD/2) clk = ~clk;
    end

    initial begin
        // Testbench logic goes here
    end

endmodule
```

How does the Simulator Work?

- SystemVerilog simulation is event-driven

How does the Simulator Work?

- SystemVerilog simulation is event-driven
- Two types of events:
 - **Evaluation** events – RHS expressions of assignments are evaluated
 - **Update** events – LHS signals of assignments are updated

How does the Simulator Work?

- SystemVerilog simulation is event-driven
- Two types of events:
 - **Evaluation** events – RHS expressions of assignments are evaluated
 - **Update** events – LHS signals of assignments are updated
- Update events can happen at different times
 - Right after evaluation events (e.g., blocking & continuous assignments)
 - At the end of a physical time step (e.g., non-blocking assignments)

How does the Simulator Work?

- SystemVerilog simulation is event-driven
- Two types of events:
 - **Evaluation** events – RHS expressions of assignments are evaluated
 - **Update** events – LHS signals of assignments are updated
- Update events can happen at different times
 - Right after evaluation events (e.g., blocking & continuous assignments)
 - At the end of a physical time step (e.g., non-blocking assignments)
- Update events → Trigger evaluation events to be queued → Trigger update events → Trigger evaluation events → ...

How does the Simulator Work?

- SystemVerilog simulation is event-driven
- Two types of events:
 - **Evaluation** events – RHS expressions of assignments are evaluated
 - **Update** events – LHS signals of assignments are updated
- Update events can happen at different times
 - Right after evaluation events (e.g., blocking & continuous assignments)
 - At the end of a physical time step (e.g., non-blocking assignments)
- Update events → Trigger evaluation events to be queued → Trigger update events → Trigger evaluation events → ...
- Events enter a priority queue (“stratified event queue”) to be processed:
 - Earliest event first
 - Then first come first serve

How does the Simulator Work?

- SystemVerilog simulation is event-driven
- Two types of events:
 - **Evaluation** events – RHS expressions of assignments are evaluated
 - **Update** events – LHS signals of assignments are updated
- Update events can happen at different times
 - Right after evaluation events (e.g., blocking & continuous assignments)
 - At the end of a physical time step (e.g., non-blocking assignments)
- Update events → Trigger evaluation events to be queued → Trigger update events → Trigger evaluation events → ...
- Events enter a priority queue (“stratified event queue”) to be processed:
 - Earliest event first
 - Then first come first serve
- For concurrent blocks, events can be queued in any order

Simulation Example

```
module swap (  
    input  clk,  
    input  rst,  
    output logic out1,  
    output logic out2  
);  
  
always_ff @ (posedge clk)  
    if (rst) out1 = 0;  
    else out1 = out2;  
  
always_ff @ (posedge clk)  
    if (rst) out2 = 1;  
    else out2 = out1;  
  
endmodule
```

```
module swap_tb ();  
    logic clk, rst, out1, out2;  
    swap dut(clk, rst, out1, out2);  
  
    initial begin  
        clk = 1'b0;  
        forever #1 clk = ~clk;  
    end  
  
    initial begin  
        rst = 1;  
        #2 rst = 0;  
    end  
  
endmodule
```

Simulation Example

t = 0

clk_new = 0
clk = clk_new
rst_new = 1
rst = rst_new

← *Evaluation event*

← *Update event*

← *Evaluation event*

← *Update event*

clk				
rst				
out1				
out2				

Signal	Value	_new
clk	X	
rst	X	
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 0

clk_new = 0
clk = clk_new
rst_new = 1
rst = rst_new

clk					
rst					
out1					
out2					

Signal	Value	_new
clk	X	0
rst	X	
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 0

clk = clk_new
rst_new = 1
rst = rst_new

clk				
rst				
out1				
out2				

Signal	Value	_new
clk	0	0
rst	X	
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 0

rst_new = 1
rst = rst_new

clk					
rst					
out1					
out2					

Signal	Value	_new
clk	0	0
rst	X	1
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 0

rst = rst_new

clk				
rst				
out1				
out2				


Signal	Value	_new
clk	0	0
rst	1	1
out1	X	
out2	X	

```
module swap (  
    input  clk,  
    input  rst,  
    output logic out1,  
    output logic out2  
);  
  
always_ff @ (posedge clk)  
    if (rst) out1 = 0;  
    else out1 = out2;  
  
always_ff @ (posedge clk)  
    if (rst) out2 = 1;  
    else out2 = out1;  
  
endmodule
```

```
module swap_tb ();  
    logic clk, rst, out1, out2;  
    swap dut(clk, rst, out1, out2);  
  
    initial begin  
        clk = 1'b0;  
        forever #1 clk = ~clk;  
    end  
  
    initial begin  
        rst = 1;  
        #2 rst = 0;  
    end  
  
endmodule
```


Simulation Example

t = 0

 

Signal	Value	_new
clk	0	0
rst	1	1
out1	X	
out2	X	


```
module swap (  
    input  clk,  
    input  rst,  
    output logic out1,  
    output logic out2  
);  
  
always_ff @ (posedge clk)  
    if (rst) out1 = 0;  
    else out1 = out2;  
  
always_ff @ (posedge clk)  
    if (rst) out2 = 1;  
    else out2 = out1;  
  
endmodule
```

```
module swap_tb ();  
    logic clk, rst, out1, out2;  
    swap dut(clk, rst, out1, out2);  
  
    initial begin  
        clk = 1'b0;  
        forever #1 clk = ~clk;  
    end  
  
    initial begin  
        rst = 1;  
        #2 rst = 0;  
    end  
  
endmodule
```

Simulation Example

t = 1

clk_new = ~clk
clk = clk_new

 

Signal	Value	_new
clk	0	0
rst	1	1
out1	X	
out2	X	

```
module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule
```

```
module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule
```

Simulation Example

t = 1

clk_new = ~clk

clk = clk_new

 

Signal	Value	_new
clk	0	1
rst	1	1
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 1

clk = clk_new

*Clock posedge queues
more events*

 

Signal	Value	_new
clk	1	1
rst	1	1
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 1

out1_new = 0
out1 = out1_new
out2_new = 1
out2 = out2_new

***Clock posedge queues
more events***

 

Signal	Value	_new
clk	1	1
rst	1	1
out1	X	
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 1

 out1_new = 0
out1 = out1_new
out2_new = 1
out2 = out2_new



Signal	Value	_new
clk	1	1
rst	1	1
out1	X	0
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 1

 out1 = out1_new
out2_new = 1
out2 = out2_new



Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	X	

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 1

out2_new = 1
out2 = out2_new

 

Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	X	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```


Simulation Example

t = 1

out2 = out2_new

 

Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 1

 

Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 2

 clk_new = ~clk
clk = clk_new
rst_new = 0
rst = rst_new



Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 2

 clk_new = ~clk
clk = clk_new
rst_new = 0
rst = rst_new



Signal	Value	_new
clk	1	0
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 2

clk = clk_new
rst_new = 0
rst = rst_new

 

Signal	Value	_new
clk	0	0
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 2

rst_new = 0
rst = rst_new

 

Signal	Value	_new
clk	0	0
rst	1	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 2

rst = rst_new

 

Signal	Value	_new
clk	0	0
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 2

 

Signal	Value	_new
clk	0	0
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```


Simulation Example

t = 3

clk_new = ~clk
clk = clk_new

 

Signal	Value	_new
clk	0	0
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 3

clk_new = ~clk
clk = clk_new

 

Signal	Value	_new
clk	0	1
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 3

clk = clk_new

*Clock posedge queues
more events*

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 3

out1_new = out2
out1 = out1_new
out2_new = out1
out2 = out2_new

***Clock posedge queues
more events***

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 3

 out1_new = out2
out1 = out1_new
out2_new = out1
out2 = out2_new



Signal	Value	_new
clk	1	1
rst	0	0
out1	0	1
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 3

 out1 = out1_new
out2_new = out1
out2 = out2_new



Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 3

out2_new = out1

out2 = out2_new

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```

Simulation Example

t = 3

out2 = out2_new

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```


Simulation Example

t = 3

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 5

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 = 0;
    else out1 = out2;

always_ff @ (posedge clk)
    if (rst) out2 = 1;
    else out2 = out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

Now let's see
what happens
when we use
non-blocking
assignments

clk					
rst					
out1					
out2					

Signal	Value	_new
clk	X	
rst	X	
out1	X	
out2	X	

```
module swap (  
    input  clk,  
    input  rst,  
    output logic out1,  
    output logic out2  
);  
  
always_ff @ (posedge clk)  
    if (rst) out1 <= 0;  
    else out1 <= out2;  
  
always_ff @ (posedge clk)  
    if (rst) out2 <= 1;  
    else out2 <= out1;  
  
endmodule
```

```
module swap_tb ();  
    logic clk, rst, out1, out2;  
    swap dut(clk, rst, out1, out2);  
  
    initial begin  
        clk = 1'b0;  
        forever #1 clk = ~clk;  
    end  
  
    initial begin  
        rst = 1;  
        #2 rst = 0;  
    end  
  
endmodule
```


Simulation Example

t = 1

out1_new = 0
out2_new = 1

out1 = out1_new
out2 = out2_new

 Updates to be
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	1	1
out1	X	0
out2	X	

```
module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule
```

```
module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule
```

Simulation Example


t = 1

out2_new = 1

out1 = out1_new

out2 = out2_new

 Updates to be
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	1	1
out1	X	0
out2	X	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 1

out1 = out1_new
out2 = out2_new

 Updates to be
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 1

 

Signal	Value	_new
clk	1	1
rst	1	1
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 2

 

Signal	Value	_new
clk	0	0
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule

```


Simulation Example

t = 3

clk_new = ~clk
clk = clk_new

 

Signal	Value	_new
clk	0	0
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 3

clk_new = ~clk

clk = clk_new

 

Signal	Value	_new
clk	0	1
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule


```

Simulation Example

t = 3

clk = clk_new

*Clock posedge queues
more events*

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```


Simulation Example

t = 3

out1_new = out2
out2_new = out1

out1 = out1_new
out2 = out2_new

 Updates are
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	0	0
out1	0	0
out2	1	1

```
module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule
```

```
module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule
```


Simulation Example

t = 3

out1_new = out2
out2_new = out1

out1 = out1_new
out2 = out2_new

 Updates are
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	0	0
out1	0	1
out2	1	1

```
module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule
```

```
module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule
```

Simulation Example


t = 3

out2_new = out1

out1 = out1_new

out2 = out2_new

 Updates are
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	0	0
out1	0	1
out2	1	0

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule
    
```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end


endmodule
    
```

Simulation Example

t = 3

out1 = out1_new
out2 = out2_new

 Updates are
processed at
end of time step



Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	0	0

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```

Simulation Example

t = 3

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	1	1
out2	0	0

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end


    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```


Simulation Example

t = 5

 

Signal	Value	_new
clk	1	1
rst	0	0
out1	0	0
out2	1	1

```

module swap (
    input  clk,
    input  rst,
    output logic out1,
    output logic out2
);

always_ff @ (posedge clk)
    if (rst) out1 <= 0;
    else out1 <= out2;

always_ff @ (posedge clk)
    if (rst) out2 <= 1;
    else out2 <= out1;

endmodule

```

```

module swap_tb ();
    logic clk, rst, out1, out2;
    swap dut(clk, rst, out1, out2);

    initial begin
        clk = 1'b0;
        forever #1 clk = ~clk;
    end

    initial begin
        rst = 1;
        #2 rst = 0;
    end

endmodule

```